

Equivalent


$$\frac{1}{Z_A} = \frac{1}{1/sC} + \frac{1}{R} = sC + \frac{1}{R} = \frac{sRC + 1}{R} ; Z_A = \frac{R}{sRC + 1}$$

For the gyrator

$$\begin{bmatrix} v_1 \\ f_1 \end{bmatrix} = \begin{bmatrix} 0 & 1/p \\ p & 0 \end{bmatrix} \begin{bmatrix} v_2 \\ f_2 \end{bmatrix} ; GY \equiv \frac{1}{p}$$


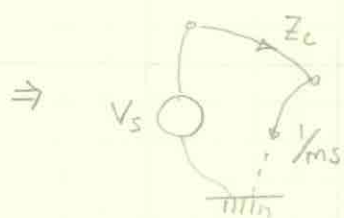
$$\text{where } Z_B = (GY)^2 / Z_A(s) = \frac{1}{p^2} \cdot \frac{sRC + 1}{R}$$



$$\begin{aligned} \frac{1}{Z_C} &= \frac{1}{s/k} + \frac{1}{Z_B} \\ &= \frac{k}{s} + \frac{p^2 R}{1 + sRC} = \frac{k(1 + sRC) + p^2 R s}{s(1 + sRC)} \end{aligned}$$

$$\text{OR } Z_C = \frac{s(1 + sRC)}{k + R(kC + p^2)s}$$

Driving point impedance

$$Z(s) = \frac{1}{ms} + Z_C(s) = \frac{1}{ms} + \frac{s(1 + sRC)}{k + R(kC + p^2)s}$$