

SUMMARY OF COMBINATIONAL LOGIC

I. Logic Variables

Logic variables take on only two states. The two states are represented by a 1 (logic one) or a 0 (logic zero), although TRUE and FALSE, ON and OFF, HIGH and LOW, are also names given to the two states. The states are exclusive. That is:

If $A \neq 0$, then $A = 1$
 If $A \neq 1$, then $A = 0$

II. Three Basic Boolean Operations

A. "OR"

Expression: $F = A + B$


Read: "F is equal to A or B"

Meaning: F is true (1) if either A or B is true.

Truth Table:

F	A	B
0	0	0
1	0	1
1	1	0
1	1	1

Logic Symbol:

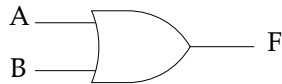

B. "AND"

Expression: $F = A \cdot B = AB$


Read: "F is equal to A and B"

Meaning: F is true (1) if A and B are true.

Truth Table:

F	A	B
0	0	0
0	0	1
0	1	0
1	1	1

Logic Symbol:

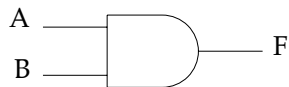

C. "NOT"

Expression: $F = \overline{A}$


Read: "F is equal to not A"

Meaning: F is true (1) if A is not true.

Truth Table:

F	A
1	0
0	1

Logic Symbol:

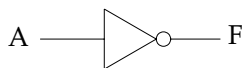

III. Derived Logic Operations

A. "NOR"

Expression: $F = \overline{A + B}$


Read: "F is equal to A nor B"

Meaning: Combined OR and NOT operations.
 F is true (1) if the quantity $A + B$ is not true.

Truth Table:

F	A	B
1	0	0
0	0	1
0	1	0
0	1	1

Logic Symbol:

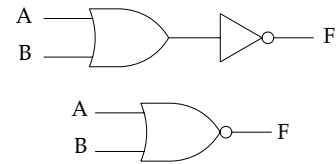

B. "NAND"

Expression: $F = \overline{AB}$


Meaning: Combined AND and NOT operations.

F is true (1) if the quantity AB is not true.

Truth Table:

F	A	B
1	0	0
1	0	1
1	1	0
0	1	1

Logic Symbol:

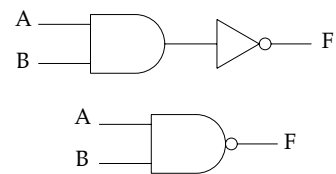

IV. Basic Theorems

With the basic logic operations it is possible to deduce a set of basic theorems.

$$1 + A = 1$$

$$0 + A = A$$

$$A + A = A$$

$$A + \overline{A} = 1$$

$$\overline{\overline{A}} = A$$

$$0A = 0$$

$$1A = A$$

$$AA = A$$

$$A \overline{A} = 0$$

$$A + B = B + A$$

$$A + (B + C) = (A + B) + C$$

$$A(B + C) = AB + AC$$

$$AB = BA$$

$$A(BC) = (AB)C$$

$$(A+B)(A+C) = A + BC$$

V. DeMorgan's Theorem's

$$\overline{A + B} = \overline{A} \overline{B}$$

$$\overline{AB} = \overline{A} + \overline{B}$$

Once expressions or logic symbol diagrams are written for a logic system, they can be manipulated (simplified) using the above rules.