## Homework #2, ME/MSE 485, due on Jan. 27, 2011

- 1. Consider the thermal composite composed of two kinds of conductors,  $K_{f1}=100W/(Km)$  and  $K_{f2}=50W/(Km)$ , and one insulator,  $K_m=0.2W/(Km)$ , see the following figure. Under applied heat at the top, Q=100W, we would like to calculate the temperature at top,  $T_1$ , and the temperature at mid-points,  $T_2$ - $T_4$ , where the temperature at the bottom,  $T_5$  is set to  $T_5=0$ . Answer the following questions. Please note that you do not need to solve for all unknowns.
  - (a) Calculate all thermal resistances, R<sub>ij</sub> defined in the figure, assuming the thickness perpendicular to this paper sheet is 1mm.
  - (b) Set the algebraic equations at nodal points (1-5) by using Kirchoff Current Law: all currents (or thermal flow in this problem) coming to i-th nodal point if they are summed up, it is equal to zero.
  - (c) Solve for temperatures,  $T_1$ ,  $T_2$ ,  $T_3$  and  $T_4$



