

**Transient on TL for ME485**  
**Important Subjects in Time-Domain Responses**

1/25/11

- (1) Unit step function responses
- (2) Delta-I noise
- (3) Finite rise-time pulse and Laplace transform technique
- (4) Pulse on lossy transmission lines and dispersion
- (5) Forward and backward coupled noise (To be covered in the coupled line)
- (6) Time-domain measurement techniques

Ref: HP application note 1304-2 (Web page)


**Time-domain Experiments**

-Requires a very fast unit step function generator

-Requires a very fast oscilloscope

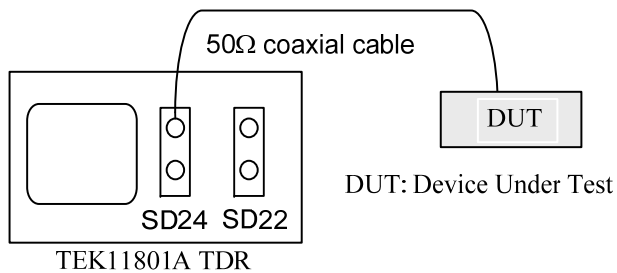
**Lab Equipment:**

TEK11801A TDR with SD24 (TDR head) and SD22 (Sampling head)



Experimental Setup for the Time Domain Analysis of Devices

**Pictures of devices under test (DUT)**

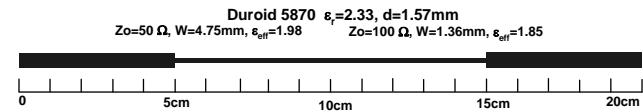

Test PCB



Unknown device 1




Unknown device 2




Unknown device 3

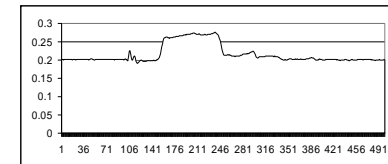**Expected responses (different TDR is used for these case)**




a) Unmatched Transmission Line

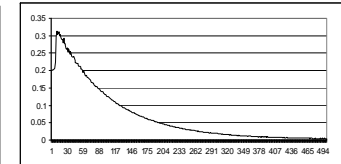


(b) Unknown 1

(1 data point = 10ps)

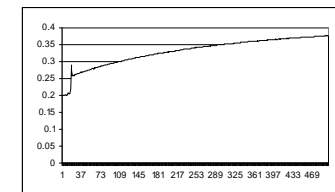

(c) Unknown 2

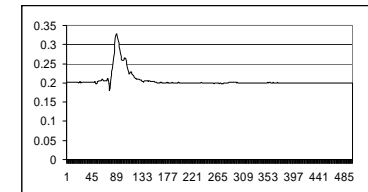

(d) Unknown 3

# 1. Unit Step Function Response from a Resistive Load

A digital signal on PCB (microstrip or stripline TL) is not a continuous wave. Rather it is a square (or pseudo square) pulse train which contains many frequency components. In this section, we will study the responses of matched and unmatched TL in time-domain. This is called "Transient Response".


### Applications:

-TDR is an instrument which combines a high speed step function generator and fast oscilloscope scope. The reflection from an unmatched impedance can be detected. Example: Computer network.


-Optical TDR is similar to TDR but it uses a short pulse to find a faulty optical fiber cable.
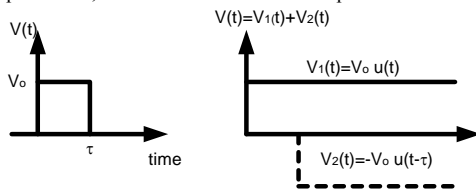
### Rectangular Pulse:

Assume the input signal is a pulse of duration  $\tau$  which can be expressed as a sum of two unit step functions as shown below. Therefore, once we find the circuit response to a unit step function, we can obtain the circuit response to a rectangular pulse.



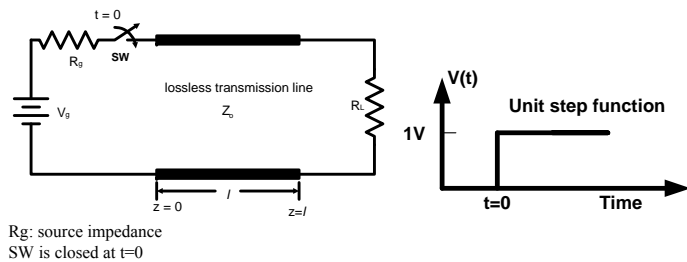
The unit step function can be created by closing and opening a switch at the source side as shown below.



# TL Response to a Unit Step Function
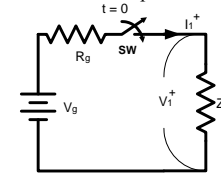
### Initial Condition

Let us assume the SW is closed at t=0. First, we need to find a initial voltage and current which propagate into the TL from the source. When the rise-time (voltage step) arrives at a TL, it does not see the load (R<sub>L</sub>). Instead, it sees the TL which has a characteristic impedance of Z<sub>o</sub>. Therefore, the voltage going into the TL is given by a voltage divider between the source impedance and Z<sub>o</sub>.



$$R_g = 4 Z_o$$


$$Z_L = 2 Z_o$$

$$V_g = 1V$$


$$V_1^+ = I_1^+ Z_o, \quad I_1^+ = \frac{V_g}{R_g + Z_o}, \quad V_1^+ = \frac{V_g Z_o}{R_g + Z_o} = \frac{1}{5} V_g = 0.2V$$
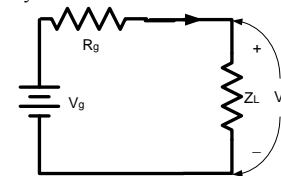
### Final Condition

We also need to take a look at a final condition. If the SW is ON for a long time, this corresponds to the DC voltage. The TL has no effect. The voltage on the load is given by


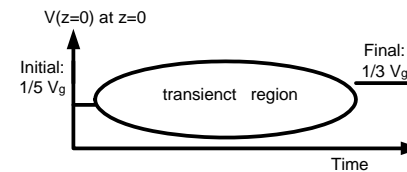
$$V_o = \left( \frac{Z_L}{R_g + Z_L} \right) V_g = 0.33V$$



The transient response is, therefore, a time response from the initial condition to the final condition.

**Between Initial and Final Conditions (Transient)**

The incident voltage reaches the load  $Z_L$  at  $t=T=l/U_p$  where  $U_p$  is the phase velocity on a TL. If the load impedance is not matched to the TL characteristic impedance, part of the incident voltage will be reflected. The polarity (positive or negative) of the reflected voltage depends on the load  $Z_L$ . It is positive for  $Z_L > Z_0$  and negative for  $Z_L < Z_0$ . Although we calculate the reflected voltage using the reflection coefficient, what we can observe is the total voltage. The total voltage on a TL is the sum of all incident and reflected voltages which occur up to the observation time.

$$\text{Load side } \Gamma_L = \frac{2Z_0 - Z_0}{2Z_0 + Z_0} = \frac{1}{3}$$

$$\text{Source side } \Gamma_g = \frac{4Z_0 - Z_0}{4Z_0 + Z_0} = \frac{3}{5}$$

The first reflected voltage from the load

$$V_1^- = \Gamma_L V_1^+ = \left(\frac{1}{3}\right)\left(\frac{1}{5}\right)V_g = \left(\frac{1}{15}\right)V_g$$

Total voltage is

$$V = V_1^+ + V_1^- = \left(\frac{1}{5} + \frac{1}{15}\right)V_g = \frac{4}{15}V_g \quad (= 0.267V)$$

If the source impedance  $R_g$  is matched to a TL ( $R_g=Z_0$ ), the reflected voltage will be absorbed by the source impedance and no signal will be reflected back to the TL when the reflected voltage arrives to the source. However, the reflected voltage which arrives to the source may also see an unmatched impedance ( $R_g \neq Z_0$ ). This will create a secondary reflection from the source side which becomes a new incident voltage.

Reflected voltage from the source

$$V_2^+ = \Gamma_g V_1^- = \Gamma_g \Gamma_L V_1^+ = \left(\frac{3}{5}\right)\left(\frac{1}{3}\right)V_1^+ = \left(\frac{3}{15}\right)\left(\frac{1}{5}\right)V_g$$

Total voltage

$$\begin{aligned} V &= V_1^+ + V_1^- + V_2^+ = (1 + \Gamma_L + \Gamma_L \Gamma_g) V_1^+ \\ &= \left(1 + \frac{1}{3} + \frac{3}{15}\right)\left(\frac{1}{5}\right)V_g \\ &= \left(\frac{23}{15}\right)\left(\frac{1}{5}\right)V_g \\ &= \frac{23}{75}V_g \quad (0.306V) \end{aligned}$$

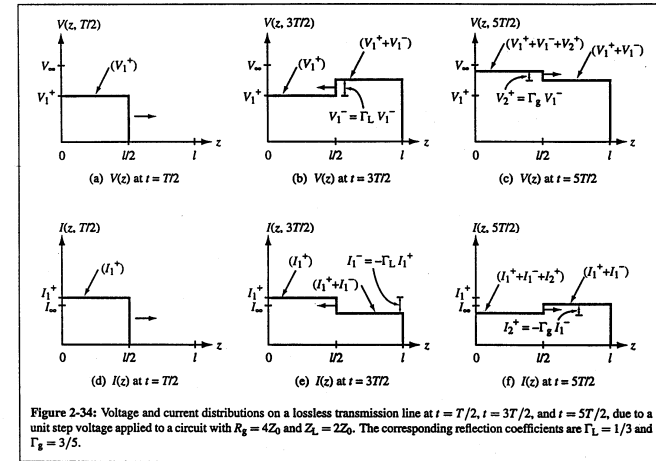


Figure 2-34: Voltage and current distributions on a lossless transmission line at  $t = T/2$ ,  $t = 3T/2$ , and  $t = 5T/2$ , due to a unit step voltage applied to a circuit with  $R_g = 4Z_0$  and  $Z_L = 2Z_0$ . The corresponding reflection coefficients are  $\Gamma_L = 1/3$  and  $\Gamma_g = 3/5$ .

This multiple reflection can be shown using the bounce diagrams.

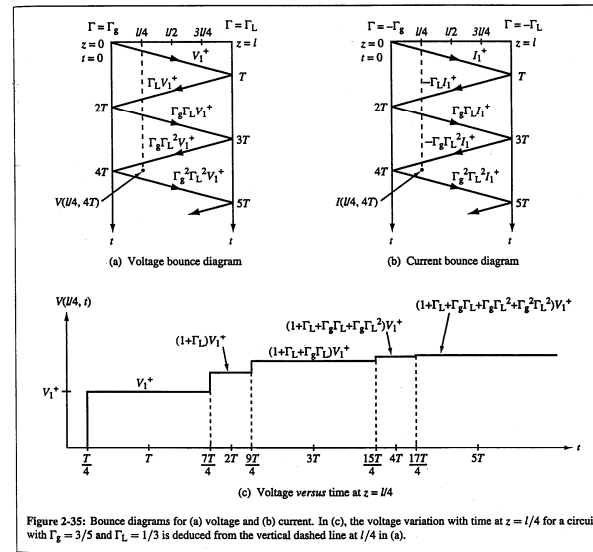


Figure 2-35: Bounce diagrams for (a) voltage and (b) current. In (c), the voltage variation with time at  $z = l/4$  for a circuit with  $\Gamma_g = 3/5$  and  $\Gamma_L = 1/3$  is deduced from the vertical dashed line at  $l/4$  in (a).

**Useful formula for a infinite series**

$$1 + x + x^2 + x^3 + \dots = \frac{1}{1-x} \quad |x| < 1$$

$$1 + \Gamma_L + \Gamma_g \Gamma_L + \Gamma_g \Gamma_L^2 + (\Gamma_g \Gamma_L)^2 + \dots = [1 + \Gamma_g \Gamma_L + (\Gamma_g \Gamma_L)^2 + \dots] + [\Gamma_L + \Gamma_g \Gamma_L^2 + \dots]$$

$$= [1 + \Gamma_L][1 + \Gamma_g \Gamma_L + (\Gamma_g \Gamma_L)^2 \dots]$$

Using this we can get

$$V_\infty = V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ + V_3^- \dots$$

$$= V_1^+ [(1 + \Gamma_L)(1 + \Gamma_L \Gamma_g + \Gamma_L^2 \Gamma_g^2 + \dots)]$$


$$= V_1^+ (1 + \Gamma_L)(1 + x + x^2 + \dots), \quad x = \Gamma_L \Gamma_g$$

$$V_\infty = V_1^+ \left( \frac{1 + \Gamma_L}{1 - \Gamma_L \Gamma_g} \right) = \frac{V_g Z_L}{R_g + Z_L}, \quad 1 + x + x^2 + \dots = \frac{1}{1-x}$$


**Another Reference Material**

**Modeling signal propagation between ICs using transmission line**

Modern ICs are usually mounted on PCB and interconnected by conducting line of very high conductivity (loss characteristics can be therefore neglected). We start our study with the following example: two ICs are connected in series, with one being master (the *driving* IC – IC<sub>1</sub>) and the other slave (the driven IC – IC<sub>2</sub>). This typical configuration can be modeled using this transmission line model:

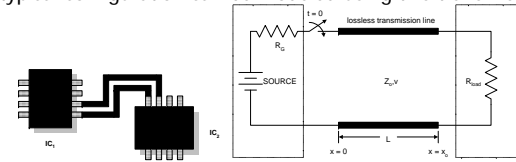

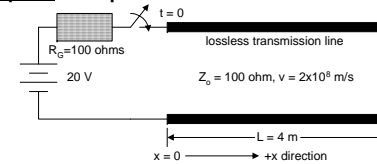**Example 1: An open-circuited transmission line (Zload → ∞)**



Describe in words and space-diagrams what happens as signal propagates from voltage source to the far-end of the transmission line.

Solution:

Consider the case of a 20 V battery with  $R_G = 100$  ohms connected to an open-circuited, lossless transmission line. This situation, with specific values of  $L$ ,  $v$  and  $Z_0$ , is shown in the figure above. With the initially open switch closed at  $t = 0$ , the voltage at the input to the line immediately becomes 10 V. This occurs because at the first instant, the dc source has no indication that the line is not infinite in length and hence “sees” an input impedance  $Z_0 = 100$  ohms. Thus at  $t = 0^+$  (that is, immediately after closing the switch), the current and voltage at the input to the line are  $20/(R_G + Z_0) = 0.10$  A and 10 V, respectively. These values remain constant until the battery has some indication (via a reflected wave) that the line is not infinite in length. With the velocity given as  $2 \times 10^8$  m/s, it takes 10 ns for  $V$  and  $I$  to travel halfway down the 4 m line. This situation is shown in part (a) of Fig. 1. Part (b) shows the waves at  $t = 20^-$  ns (that is, slightly less than 20 ns). When the waves arrive at the open circuit, something must happen since two contradictory impedance requirements exist. First, the  $V/I$  ratio for the traveling wave must be  $Z_0 = 100$  ohms. On the other hand, Ohm’s law at the open-circuited end of the line

requires an infinite impedance since current must be zero. The creation of reflected waves ( $V_-$ ,  $I_-$ ) allows both of these requirements to be satisfied. Thus at the load end ( $x = 4$  m, corresponding  $t = 20$  ns),

$$V_{load} = V_+ + V_-$$

$$I_{load} = I_+ - I_-$$

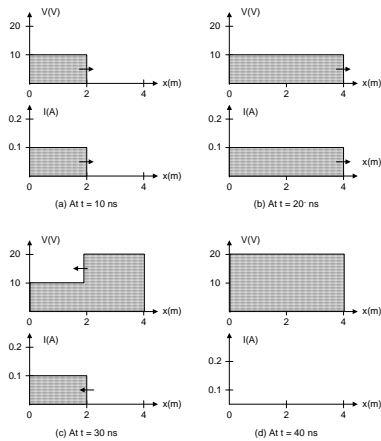



Fig. 1

The condition  $I_{load} = 0$  requires  $I_-$  and  $I_+ = 0.10$  A. Also, with  $V_+ = I_+ Z_0$  and  $V_- = I_- Z_0$ ,  $V_- = V_+ = 10$  V. Therefore,  $I_{load} = 0$  A and  $V_{load} = 20$  V at the load end.

The open-circuit condition at the load end creates reflected voltage and current waves of 10 V and 0.10 A, respectively. These waves travel in the negative  $x$  direction with the same velocity as the incident (transmitted) waves. Part (c) and (d) of Fig. 1 show the resultant voltage and current (due to the sum of + and - waves) at  $t = 30$  ns and 40 ns. As the wavefront of the 10 V, 0.10 A reflected waves moves to the left, it leaves behind a net voltage of 20 V and a net current of zero. Since  $R_G = 100$  ohms, both Ohm's law and the condition that  $V_-/I_- = 100$  ohms are satisfied at  $t = 40$  ns, and hence no reflections are required at the generator end. The process thus ends and a steady state is achieved with  $V = 20$  V and  $I = 0$  A everywhere on the transmission line. The time-flow

plots of these incident and reflected signals as a function of distance and time are shown on the next page.

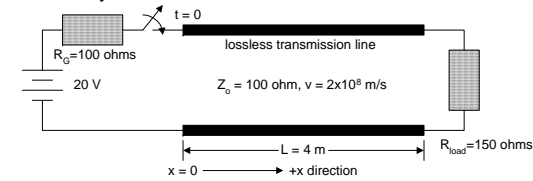**Example 2: A resistively terminated transmission line ( $Z_{load}$  : real number)**



Describe in words and space-diagrams what happens as signal propagates from voltage source to the far-end of the transmission line.

**Solution:**

Consider now the case of a finite length transmission line terminated with a pure resistance. This situation is shown above, where  $R_{load} (= 150$  ohms) is the terminating or load resistance. As before, closing the switch initiates a 10 V, 0.10 A forward traveling wave. At  $t = 20$  ns, the wave arrives at the load end. Since  $R_{load} \neq Z_0$ , Ohm's law can only be satisfied by assuming reflected waves. Thus at  $z = 4$  m,  $V_{load} = V_+ + V_-$  and  $I_{load} = I_+ - I_- = (V_+ - V_-)/Z_0$ . Ohm's law requires  $V_{load}/I_{load} = R_{load}$  and hence

$$\begin{aligned} R_{load} &= Z_0(V_+ + V_-) / (I_+ - I_-) = Z_0[ 1 + (V_-/V_+) ] / [ 1 - (V_-/V_+) ] \\ &= Z_0(1 + \Gamma_{load}) / (1 - \Gamma_{load}) \end{aligned}$$

Solving for the load reflection coefficient yields

$$\Gamma_{load} = (R_{load} - Z_0) / (R_{load} + Z_0)$$

(compare this with  $\Gamma_{load} = (Z_{load} - Z_0) / (Z_{load} + Z_0) = V_-(x=0) / V_+(x=0)$  on page 3 of this handout).

For resistively terminations,  $\Gamma_{load}$  is real and can take on any value between  $-1$  and  $+1$ . If  $R_{load} = 0$  (short circuit),  $\Gamma_{load} = -1$ , while if  $R_{load} = \infty$  (open circuit, the previous case),  $\Gamma_{load} = +1$ .

In the present case for  $R_{load} = 150$  ohms,  $\Gamma_{load} = 0.2$ . With the forward wave equal to 10 V and 0.10 A, the reflected voltage and current are 10 V  $\times 0.2 = 2$  V and 0.10 A  $\times 0.2 = 0.02$  A, respectively. Parts (a) and (b) of Fig. 2 shows the voltage and current along the line at  $t = 10$  ns and 30 ns. At  $t = 10$  ns, only the forward traveling waves exist, having arrived only at the halfway point of the 4 m line. At  $t = 30$  ns, the reflected waves have been generated and have traveled halfway back toward the generator end of the line. At  $t = 40$  ns (not shown), the reflected waves arrive at the input and the resultant voltage and current everywhere along the line become 12 V and 0.08 A. Since  $R_G = Z_0$ , no reflection is required at the generator end and the steady state is achieved after 40 ns. Note that the final values (12 V and 0.08 A) are those expected from a dc analysis of the circuit.

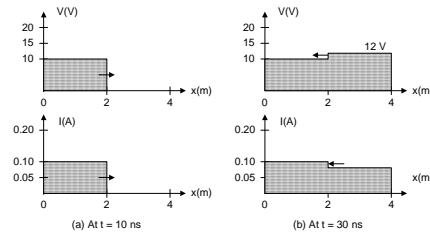


Fig. 2

### Example 3: Multiple reflections on a transmission line

From the above cases, it is clear that when  $R_G = Z_0$ , the steady state is achieved after one round trip (40 ns, in our example). On the other hand, if  $R_{load} = Z_0$ , the steady state occurs after an *one-way* trip (20 ns, in our example). Let us now explore the situation when neither  $R_G$  nor  $R_{load}$  is equal to the characteristic impedance  $Z_0$ . The analysis will show that reflections occur at both ends of the line and the steady state values are approached only as  $t$  becomes *infinite*!

Describe in words and space-diagrams what happens as signal propagates from voltage source to the far-end of the transmission line.

#### Solution:

As a specific example, consider the circuit above, where  $R_G = 200$  ohms,  $R_{load} = 25$  ohms, and  $Z_0 = 100$  ohms. When the switch is closed at  $t = 0$ , the 90 V source sees 200 ohms in series with the characteristic impedance of the line. Therefore, the current and voltage at the input end of the line

( $x = 0$ ) are initially  $I_+ = 90/300 = 0.3$  A and  $V_+ = I_+ Z_0 = 30$  V. After 20 ns, the  $V_+$  and  $I_+$  waves arrive at the load end where the reflection coefficient  $\Gamma_{load} = (25 - 100)/(25 + 100) = -75/125 = -0.6$  and hence  $V_- = \Gamma_{load} \times V_+ = -18$  V and  $I_- = \Gamma_{load} \times I_+ = -0.18$  A. At the end of 30 ns, the voltage between  $x = 2$  m and  $x = 4$  m is reduced to  $30 - 18 = 12$  V, while the current has increased to  $0.3 + 0.18 = 0.48$  A. The progress of the voltage wave along the line is shown in Fig. 3 for  $t = 30, 50, 70,$  and 90 ns.

Let us observe the voltage wave as time marches on. At the end of 40 ns, the  $-18$  V wave arrives at the input where it sees an impedance  $R_G = 200$  ohms. Since  $R_G \neq Z_0$ , a reflection occurs at the generator end. By analogy with  $\Gamma_{load}$ , the generator reflection coefficient  $\Gamma_G$  is given by

$$\Gamma_G = (R_G - Z_0) / (R_G + Z_0)$$

For  $R_G = 200$  ohms,  $\Gamma_G = 1/3$  and hence a  $-6$  V wave is reflected towards the load end. At  $t = 50$  ns, it has progressed halfway down the line, leaving behind it a voltage of  $(30 - 18 - 6) = 6$  V. This is shown in part (b) of the figure. At  $t = 60$  ns, the  $-6$  V wave arrives at the load which generates a reflected wave of value  $(-6) \times \Gamma_{load} = +3.6$  V. The situations at 70 and 90 ns are also shown in the figure. Note that at  $t = 90$  ns, another forward traveling wave exists having a value  $(+3.6) \times \Gamma_G = +1.2$  V. This process continues indefinitely with the amplitude of the re-reflected waves getting smaller and smaller (due to energy dissipation of the resistors). A plot of voltage versus time at any fixed point on the line would show that, in the limit, the voltage becomes the expected dc value (namely,  $90R_{load}/(R_G + R_{load}) = 10$  V). Such a plot at  $x = 0$ , the input, is shown in Fig. 4. Every step in voltage represents the arrival and generation of the reflected waves at the input. After five round-trip (200 ns), the voltage is within 0.10 percent of the steady-state value.

It is interesting to note that the voltage shown in Fig. 4 is oscillatory as it approaches its final value. The period of this ringing effect is 80 ns (twice the round-trip time) and hence its reciprocal is the natural resonant frequency of the circuit, namely, 12.5 MHz. Since  $v = 2 \times 10^8$  m/s, this means that the line is  $\lambda/4$  long at the resonant frequency. Thus we see that by connecting a dc source to a transmission line, high frequency oscillations are possible. In a PCB system, the emitted power from these high-frequency oscillations, if left unchecked, will result in interference to other devices, impairing the performance of the overall system.

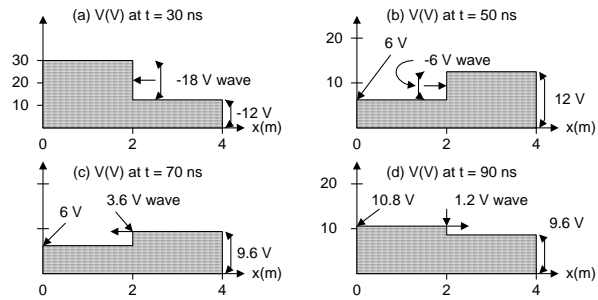


Fig. 3

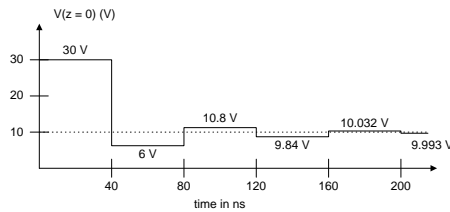


Fig. 4

## 2. Space-Time Representation of Signals

The space-time diagram is a graphical aid in determining the voltage and current as a function of either time or position along the line. Fig. 5 shows the diagram for the circuit in Example 3. The abscissa indicates position along the line and the ordinate represents the time scale,  $t = 0$  being the moment that the switch is closed. For reference, the values of  $\Gamma_G$  and  $\Gamma_{load}$  are given at the top of the diagram. The lines sloping downward and to the right represent forward traveling waves, while those sloping down and to the left represent reverse waves. The voltage and current values for the particular wave are shown above and below the sloping line. As explained, the load end creates reflections equal to  $\Gamma_{load}$  of the arriving wave. Generator reflections are equal to  $\Gamma_G$  times the value of the wave arriving at the generator end.

To illustrate, Fig. 5 will be used to determine the voltage and current at  $x = 2$  m. Each intersection of a sloping line with the interval  $x = 2$  m line represents the arrival of a wavefront. For  $t < 10$  ns, no intersection exists and hence both  $\mathbf{V}$  and  $\mathbf{I}$  are zero. For  $10 < t < 30$  ns, there is one intersection which means  $\mathbf{V} = 30$  V and  $\mathbf{I} = 0.30$  A. For  $t > 30$  ns, the voltage is the sum of all the forward and reverse waves that have passed the  $x = 2$  m location. For example, at  $t = 80$  ns,  $\mathbf{V} = 30 - 18 - 6 + 3.6 = 9.6$  V. The current may be determined in a similar manner except that current values associated with reverse waves must be subtracted from those associated with the forward waves. For example, at  $t = 80$  ns,  $\mathbf{I} = 0.30 - (-0.18) + (-0.06) + (-0.06) - (+0.036) = 0.384$  A. The diagram may also be used to determine voltage and current versus  $x$  for a fixed time by drawing a horizontal line corresponding to the particular value of time. The sum of voltages above the line corresponds to the voltage at that point on the line. The same applies to the current except that, as before, reverse-traveling current waves must be subtracted from forward-traveling current waves.


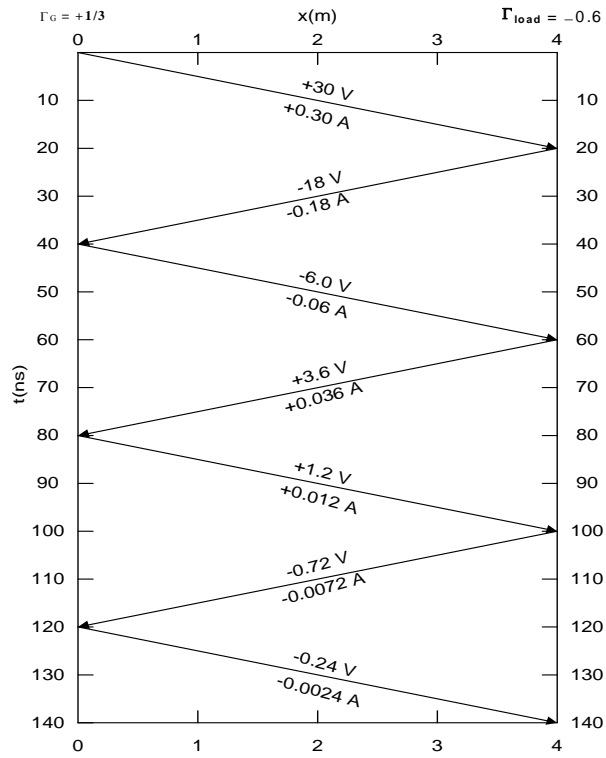


Fig. 5

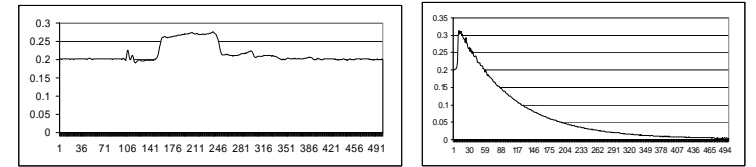
Expected responses (different TDR is used for these case)




a) Unmatched Transmission Line

(b) Unknown 1

(1 data point = 10ps)

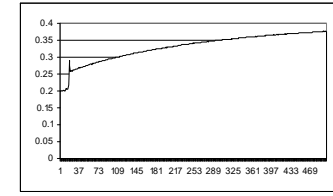


(c) Unknown 2

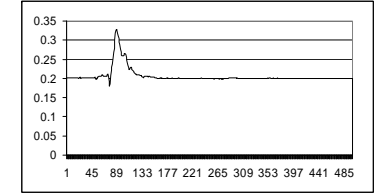

(d) Unknown 3

Pictures of devices

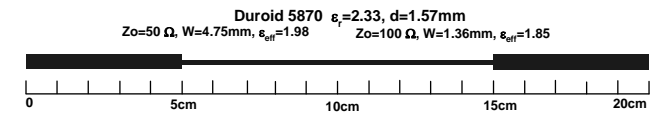

Test PCB



Unknown device 1



Unknown device 2



Unknown device 3




## 5. Laplace transform analysis of a TL terminated with a complex load impedance

10/27/10

In the previous section, we studied the reflection of a unit step function from the unmatched load which is purely resistive. The rise-time (waveform) of the reflected signal does not change if the unmatched load is resistive. In reality, however, the input/load impedances of the digital circuit contain a reactive element such as a parasitic capacitance and inductance. In this section, therefore, we will study the time-domain analysis of reflected signal from a complex load impedance. The analysis is based on Laplace transform. We express the input waveform and complex load impedance using Laplace transform and calculate the reflected voltage. By taking the inverse Laplace transform, we can derive the time-domain response. The waveform of the reflected signal shows the distinctive characteristics depending on the load type. This can be used for inferring the load type. In addition, we will show how to obtain the values of each element using different techniques.
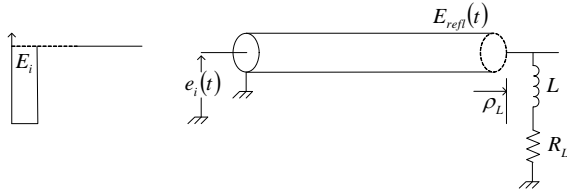
### 5-1. Unit step function as an input (Reflection case)

We have a L-R series load attached to a lossless TL which does not distort the waveform. The input signal is a unit step function. To simplify the analysis, we will neglect the delay due to a TL.



Using the Laplace transform, the load impedance is given by  $Z_L = R_L + sL$ .

The reflection coefficient at the load can be expressed as

$$\rho_L(s) = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{s + \frac{R_L - Z_0}{L}}{s + \frac{R_L + Z_0}{L}}$$

The input voltage is the unit step function and is given by

$$e_i(t) = u(t)$$

The Laplace transform of this is

$$E_i(s) = \frac{1}{s}$$

17

where Laplace transform of  $[u(t)] = \frac{1}{s}$

The reflected voltage from the load is given by

$$E_{refl}(s) = E_i(s) \rho_L(s) = \left( \frac{1}{s} \right) \left( \frac{s + \frac{R_L - Z_0}{L}}{s + \frac{R_L + Z_0}{L}} \right)$$

Now we use the inverse Laplace transform to get the time-domain response  $E_{refl}(t)$

We need to separate the above equation into simple terms which represent each response such as a unit step function  $u(t)$ . We can write the term as

$$\frac{s + A}{s(s + B)} = \frac{C_1}{s} + \frac{C_2}{(s + B)} = \frac{C_1(s + B) + C_2 s}{s(s + B)}$$

Therefore

$$C_1 + C_2 = 1$$

$$C_1 B = A$$

$$C_1 = \frac{A}{B} = \frac{R_L - Z_0}{R_L + Z_0}$$

$$C_2 = 1 - C_1 = \frac{2Z_0}{R_L + Z_0}$$

Now we take the inverse Laplace transform and obtain

$$\left[ \frac{R_L - Z_0}{(R_L + Z_0)} + \frac{2Z_0}{(R_L + Z_0)} e^{-\left(\frac{R_L + Z_0}{L}\right)t} \right] u(t)$$

$$\text{where } \frac{1}{s + B} \rightarrow e^{-Bt}$$

The final expression of the reflected signal is

$$E_{refl}(t) = \left[ \frac{R_L - Z_0}{(R_L + Z_0)} + \frac{2Z_0}{(R_L + Z_0)} e^{-\left(\frac{R_L + Z_0}{L}\right)t} \right] u(t)$$

The total voltage is the sum of incident and reflected at the load. Therefore, we have the load voltage of

$$E_{total}(t) = E_{inc} + E_{refl} = \left[ 1 + \frac{R_L - Z_0}{(R_L + Z_0)} + \frac{2Z_0}{(R_L + Z_0)} e^{-\left(\frac{R_L + Z_0}{L}\right)t} \right] u(t)$$

18

It is easy to see the peak voltage occurs at  $t=0$  and the value is given by

$$E_{total}(t=0) = \left[ \frac{2R_L + 2Z_0}{R_L + Z_0} \right] = 2$$

This is expected because the inductance is an open circuit at  $t=0$  and the total voltage becomes twice the incident voltage.

The final voltage is given by setting  $t \rightarrow \infty$ . The value is

$$E_{total}(t=\infty) = \left[ \frac{2R_L}{R_L + Z_0} \right]$$

The transient region is given by the exponential decay  $e^{-\left(\frac{R_L + Z_0}{L}\right)t}$ .

If we take a natural log of this response, we get a line as a function of time.

$$\log\left[e^{-\left(\frac{R_L + Z_0}{L}\right)t}\right] = -\left(\frac{R_L + Z_0}{L}\right)t = -mt$$

The above expression shows the slope of this line  $m$  is proportional to  $L$ . Because we can find  $R_L$  from the  $t = \infty$  data, we should be able to obtain the value of  $L$  from the slope  $m$ . This process can be used with the TDR response to obtain the values of  $L$  and  $R_L$ .

If the load is given by the other combinations of  $L$ ,  $C$  and  $R$ , we need to replace  $Z_L$  by

Parallel  $L$  and  $R$

$$Z_L = R_L // sL = sR_L L / (R_L + sL)$$

Series  $C$  and  $R$

$$Z_L = R_L + (1/sC)$$


Parallel  $C$  and  $R$

$$Z_L = R_L // sC = R_L / (1 + sCR_L)$$

The expected waveforms and responses are shown below. In all cases, the values of  $L$  and  $C$  can be estimated by taking a natural log of the time-domain responses. However, it is also clear that neither the initial peak voltage nor the final voltage can be used for estimating  $L$  and  $C$ . This limitation is due to the use of an ideal unit step function.

In the next section, we will study the finite rise-time case and show that the peak voltage value can be used for estimating the value of  $L$  when the inductance is present.
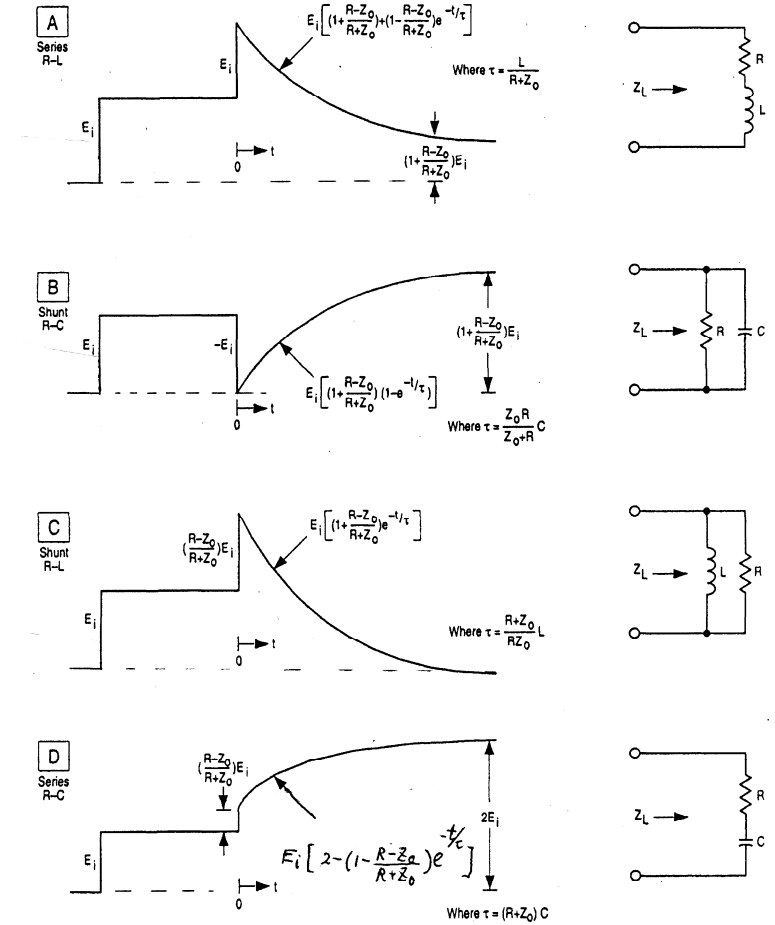
### Expected TDR responses from different complex loads



### Estimation of complex load values for the unit step function excitation

Assume we have a series L and R circuit and we get

$$E_{total}(t) = C_1 \left[ 1 + \frac{R_L - Z_0}{(R_L + Z_0)} + \frac{2Z_0}{(R_L + Z_0)} e^{-\left(\frac{R_L + Z_0}{L}\right)t} \right] u(t)$$


where  $C_1$  is a constant related to the initial peak voltage of TDR.

We can assume  $E_{total}$  is also our measured data. We can find  $R_L$  from either the initial or final condition. To find  $L$ , we set

$$e^{-\left(\frac{R_L + Z_0}{L}\right)t} = [(E_{total}(t) / C_1) - (1 + \frac{R_L - Z_0}{(R_L + Z_0)})] \left[ \frac{(R_L + Z_0)}{2Z_0} \right] = C_2$$

$$\ln(e^{-\left(\frac{R_L + Z_0}{L}\right)t}) = -\left(\frac{R_L + Z_0}{L}\right)t = -mt = \ln(C_2)$$

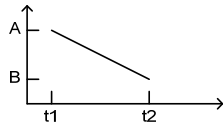where  $m$  is a slope of  $y=-mt$  line of the experimental data.  $C_2$  must be positive.  $C_2$  has a linear section and you can find the slope as  $m=(A-B)/(t_2-t_1)$ . Although  $E_{total}$  is your measured data, the constant term in  $C_2$  is not important. You can use your experimental data as  $C_2$  in the analysis as shown below.



Linear section of  $C_2$  is shown.

When we have  $R$  and  $C$ , we have  $(1-\exp(-mt))$  response. In this case you cannot take  $\ln(\text{experimental data})$  to get a slope. You need to change the data to get the form  $\exp(-mt)=C_x$  equation.

Assume we have a parallel  $R$  and  $C$  load.

$$E_{total}(t) = C_1 \left[ \left(1 + \frac{R_L - Z_0}{(R_L + Z_0)}\right) (1 - e^{-mt}) \right] u(t)$$

$$e^{-mt} = 1 - E_{total}(t) / [C_1 \left[ \left(1 + \frac{R_L - Z_0}{(R_L + Z_0)}\right) \right]] = C_3$$

where  $C_1$  is a constant related to the initial peak voltage of TDR. In this expression  $E_{total}$  is your measured data. Also  $C_3$  must be positive to use  $\ln()$  function.


Another approach is the "trial and error" or "supervised parameter estimation". Assume you already know  $C_1$  and  $R_L$  in the following equation and the only unknown is  $L$ .

$$E_{total}(t) = C_1 \left[ 1 + \frac{R_L - Z_0}{(R_L + Z_0)} + \frac{2Z_0}{(R_L + Z_0)} e^{-\left(\frac{R_L + Z_0}{L}\right)t} \right] u(t)$$

Set  $L$  to be a certain value then calculate  $E_{total}()$  and compare it with experimental data. Time  $t=0$  corresponds to the start of the reflected voltage. The initial voltage exists for  $t < 0$ , shown as  $E_i$ . If the tail is too long,  $L$  is too large. If the tail is too short,  $L$  is too small. You may use the "binary search" method to find the optimum value of  $L$ .
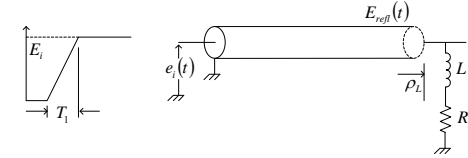
### 5-2. Finite rise-time input (Reflection case) (This is more realistic model.)

In 5-1, we studied the simple unit step function responses. The practical digital circuits, however, have a finite rise-time signal and complex load. In this section, we will use the Laplace transform technique to analyze both finite rise-time signal and reflection from a complex load. We assume the TL is lossless. The lossy TL case which will create dispersion (distortion of the waveform) will be analyzed later.



Let assume the input pulse rise-time (10-90%) is specified as  $t_r = 80\text{ps}$ . Using the straight line approximation, the total transient time is given by

$$T_1 \approx \frac{t_r}{0.8} = 100\text{ps}$$

The slope of the input signal (rise) is then  $m = \frac{E_i}{T_1}$ .


We use the same complex load given by  $Z_L = R_L + sL$

The reflection coefficient at the load can be expressed as

$$\rho_L(s) = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{s + \frac{R_L - Z_0}{L}}{s + \frac{R_L + Z_0}{L}}$$

The input voltage can be decomposed into two terms is given by
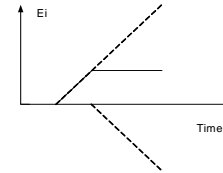
$$e_i(t) = m t u(t) - m (t - T_1) u(t - T_1)$$



We take Laplace transform of  $e_i(t)$  and obtain

$$E_i(s) = \frac{m}{s^2} (1 - e^{-T_1 s})$$

$e^{-T_1 s}$  : delay

$$\text{where } u(t) = \frac{1}{s}$$

$$tu(t) = \frac{1}{s^2}$$

The reflected voltage from the load is given by

$$E_{refl}(s) = E_i(s) \rho_L(s) = \left( \frac{m}{s^2} \right) (1 - e^{-\tau_1 s}) \left( \frac{s + \frac{R_L - Z_0}{L}}{s + \frac{R_L + Z_0}{L}} \right)$$

Now we use an inverse Laplace transform to get the time-domain response  $E_{refl}(t)$

$$E_{refl}(s) = \left( \frac{m}{s^2} \right) \left( \frac{s + \frac{R_L - Z_0}{L}}{s + \frac{R_L + Z_0}{L}} \right) - \left( \frac{m}{s^2} \right) e^{-\tau_1 s} \left( \frac{s + \frac{R_L - Z_0}{L}}{s + \frac{R_L + Z_0}{L}} \right)$$

We need to separate the above equation into simple terms which represent each response such as a unit step function  $u(t)$ . We can write the first term as

$$\frac{s + A}{s^2(s + B)} = \frac{C_1}{s} + \frac{C_2}{s^2} + \frac{C_3}{(s + B)} = \frac{C_1 s(s + B) + C_2(s + B) + C_3 s^2}{s^2(s + B)}$$

Therefore

$$C_1 + C_3 = 0$$

$$C_1 B + C_2 = 1$$

$$C_2 B = A$$

$$C_2 = \frac{A}{B} = \frac{R_L - Z_0}{R_L + Z_0}$$

$$C_1 = \frac{1 - C_2}{B} = \frac{2Z_0 L}{(R_L + Z_0)^2}$$

$$C_3 = -C_1$$

Take an inverse Laplace transform and obtain

1<sup>st</sup> term

$$\left[ \frac{2Z_0 L}{(R_L + Z_0)^2} + \left( \frac{R_L - Z_0}{R_L + Z_0} \right) t - \frac{2Z_0 L}{(R_L + Z_0)^2} e^{-\left(\frac{R_L + Z_0}{L}\right)t} \right] u(t)$$

$$\frac{1}{s + B} \rightarrow e^{-Bt}$$

We can obtain the 2<sup>nd</sup> term using the same method.

Then the final expression of the reflected voltage is

$$E_{refl}(t) = \left[ \frac{2Z_0 L}{(R_L + Z_0)^2} + \left( \frac{R_L - Z_0}{R_L + Z_0} \right) t - \frac{2Z_0 L}{(R_L + Z_0)^2} e^{-\left(\frac{R_L + Z_0}{L}\right)t} \right] m u(t)$$

$$- \left[ \frac{2Z_0 L}{(R_L + Z_0)^2} + \left( \frac{R_L - Z_0}{R_L + Z_0} \right) (t - T_1) - \frac{2Z_0 L}{(R_L + Z_0)^2} e^{-\left(\frac{R_L + Z_0}{L}\right)(t - T_1)} \right] m u(t - T_1)$$

The total voltage is the sum of incident and reflected at the load. Therefore, we have the load voltage of

$$E_{total}(t) = E_{inc} + E_{refl}$$

This should provide the complete voltage response.


It is often important to estimate the maximum reflected voltage. As we found in 5-1, the maximum value is  $2E_{inc}$  if the input is a unit step function.

\*\*\*\* This is not correct

To obtain the maximum reflected voltage, we take a derivative of  $E_{refl}(t)$  with respect to  $t$  and set it to zero. This gives us the condition that the maximum voltage occurs at

\*\*\*\*

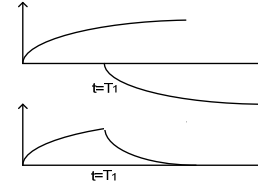To simplify, assume  $R_L = Z_0$  and plot  $E_{refl}(t)$ . We can show the peak occurs at  $t = T_1$ .



Therefore

$$E_{refl \max} = E_{refl}(t = T_1)$$

For a special case of  $R_L = Z_0$ , the maximum voltage becomes

$$E_{refl}(t = T_1) = \frac{mL}{2Z_0} \left[ 1 - e^{-\left(\frac{2Z_0}{L}\right)T_1} \right]$$

Although  $L$  is contained in two places, this expression can be used for estimating the inductance  $L$ .

If we approximate  $\exp()$  as  $e^x \sim 1 + x + x^2/2$  ( $e^x \sim 1 + x$  does not work in this case), we get

$$E_{refl}(t = T_1) \approx \frac{mL}{2Z_0} \left[ 1 - \left[ 1 - \left( \frac{2Z_0}{L} \right) T_1 + \left[ \left( \frac{2Z_0}{L} \right) T_1 \right]^2 / 2 \right] \right] = mT_1 \left[ 1 - \left( \frac{Z_0}{L} \right) T_1 \right]$$

Then the approximate value of  $L$  is  
 $L \approx Z_0 T_1 / [1 - E_{refl}(t = T_1) / mT_1]$

Another approach is to calculate the area of the reflected voltage which is the same as integration over the reflected voltage. If  $R_L = Z_0$ , the final value is the same as the incident voltage and the effect of the incident voltage can be neglected. However, if  $R_L \neq Z_0$ , the integration over the initial and final values must be carefully done.

Assume  $R_L = Z_0$ . The integration of the reflected voltage is given by

$$\int_0^{\infty} E_{refl}(t) dt = \int_0^{\infty} \frac{mL}{(2Z_0)} \left[ 1 - e^{-\left(\frac{2Z_0}{L}\right)t} \right] dt - \int_{T_1}^{\infty} \frac{mL}{(2Z_0)} \left[ 1 - e^{-\left(\frac{2Z_0}{L}\right)(t-T_1)} \right] dt = \frac{mLT_1}{2Z_0}$$

This should be set equal to the measured area under the reflected voltage. Then  $L$  can be estimated as

$$L = \frac{2Z_0}{mT_1} \int_0^{\infty} E_{refl\_measured}(t) dt$$

### 5.3 Estimation of the inductance $L$ (Examples using the next figure)

(a) Based on the peak value

$$T_1 \approx \frac{t_r}{0.8} = 100 ps \quad t_r: 10 \text{ to } 90\%, T_1: \text{total risetime}$$

We want to find the parasitic inductance of the load.  
 The peak reflected voltage is given by  $= 0.44V$

$$m = \frac{0.94}{100 ps} \quad 0.94V: \text{initial voltage}$$


$$\text{From } 0.44 = \frac{mL}{2Z_0} \left[ 1 - e^{-\left(\frac{2Z_0}{L}\right)T_1} \right], Z_0 = 50\Omega$$

We can find  $L$  to be

$$L = 6nH$$

If we use the approximation  $L \approx Z_0 T_1 / [1 - E_{refl}(t = T_1) / mT_1]$ , we get  $L \approx 10nH$  which is substantially different from the previous estimate. In this case the argument of the exp() is close to -1 and the approximation based on the 3 terms is not sufficient.

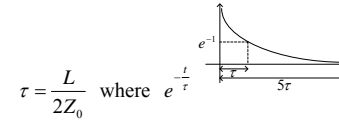(b) Based on  $e^{-1}$  value. If the time-domain response is close to the exponential function and the inductance can also be estimated from the decay time as shown below.



$$\tau = \frac{L}{2Z_0} \quad \text{where } e^{-\frac{t}{\tau}}$$

$$L = (\tau)(2Z_0)$$

If the decay time is  $5\tau \sim 0.3ns$ , then

$$L \approx (60 ps)(100) \approx 6nH$$

This value is close to an estimate based on the peak value.

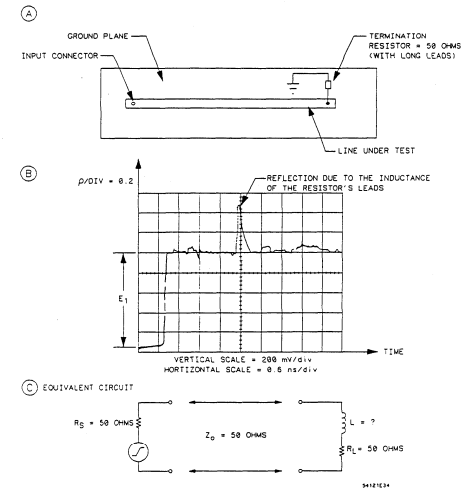


Figure E-10. Effects Due to Termination Resistor Leads

These two methods to estimate  $L$  have serious problems. For example, the max value of  $E_{refl}$  depends on the rise-time  $t_r$  in the first approach. If the rise time is close to  $1ns$ , then the peak voltage will be reduced to

$$E_{refl\_max} \sim 56mV$$

This is much less than  $0.44V$  for  $t_r = 80 ps$  and a small amount of noise will introduce an error in estimation. Similarly, it can be shown that the voltage waveform becomes far from an ideal exponential decay when the rise-time is increased.

### 5.4 Estimation of L based on the area (Transmission case)

Unlike a small capacitance, the small inductance measurement is much more difficult. The time-domain approach shown here can be used. In many cases it is difficult to find the accurate  $\exp(-1)$  time or slope  $m$  from the measured data due to a slow rise-time. Also these techniques are sensitive to measurement errors. In the following section, we will show the area under the reflected voltage can be used for estimating L.

The right figure shows the voltage observed at the unknown inductor. If there is no resistor, the final voltage is 0 (or the final current is  $\Delta V / R_s$ ). The initial current  $I(t=0) = 0$ . We can express the area under the voltage waveform is



$$V_{\text{inductor}} = L \frac{dI_{\text{inductor}}}{dt}$$

$$\int_0^{\infty} V_{\text{inductor}}(t) dt = L \int_0^{\infty} \frac{dI_{\text{inductor}}(t)}{dt} dt$$

$$\int_0^{\infty} V_{\text{inductor}}(t) dt = L[I(\infty) - I(0)]$$

$$\text{area} = L[I(\infty) - I(0)]$$
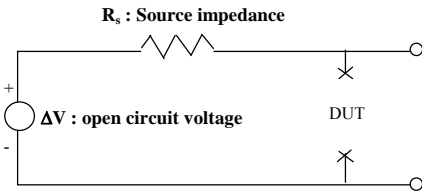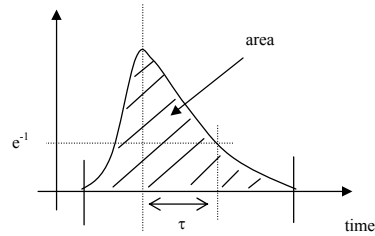
$$L = \frac{(\text{area})}{\Delta I} = \frac{(\text{area})(R_s)}{\Delta V}$$



$R_s$  = equivalent source impedance due to source  
 $\Delta V$  is the open circuit voltage.

### Example of Small Inductance Measurement.

The following figures show how to find the unknown inductance from the measured time-domain data. Unlike a small capacitor, measuring a small inductor with TDR is a challenging task. The time constant of series or parallel RL circuits has  $\exp(-t/L/R)$ . If the value of L is small, R cannot to too large to observe a time-domain response within a reasonable time.


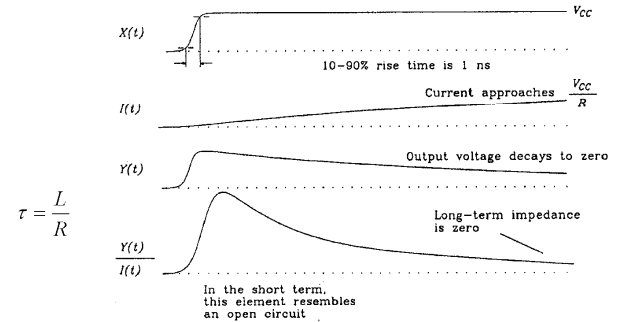
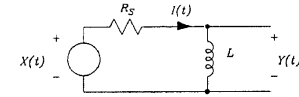


Figure 1.10 Instantaneous resistance of a perfect inductor.

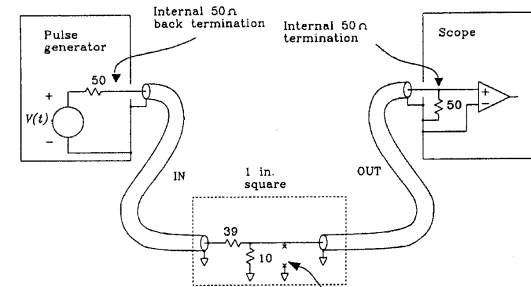

- All resistors 1/8 W
- Run coax probes in from opposite sides to reduce direct feed-through
- Ground out DUT test point to check for feed-through

Figure 1.11 A 7.6-Ω lab setup for measuring inductance.

System response

Open circuit voltage ~ 418mV

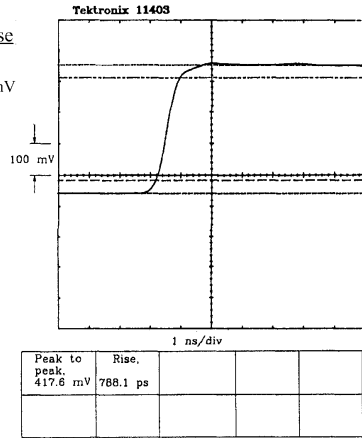


Figure 1.12 Open-circuit response of a 7.6-Ω inductance test setup.

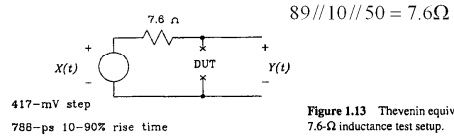


Figure 1.13 Thevenin equivalent of a 7.6-Ω inductance test setup.

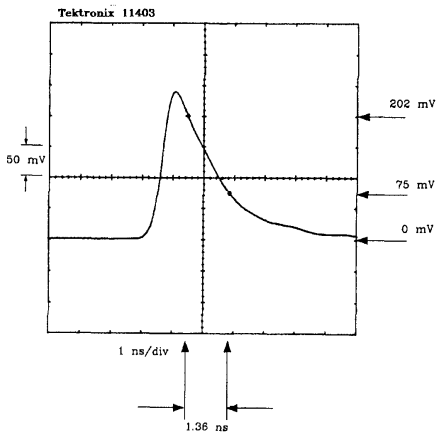


Figure 1.14 Decaying exponential response of a 7.6-Ω inductance test setup.

Based on the time constant

Find  $e^{-1}$  time

$$L = R\tau = (7.6)(1.36 \times 10^{-9}) = 10.3nH$$

R: must be small to get a large value of  $\tau=L/R$ .

System response without L: 0.8ns (rise time of the system)

System response with L: 1.36ns (inductor decay time)

L estimation from the area

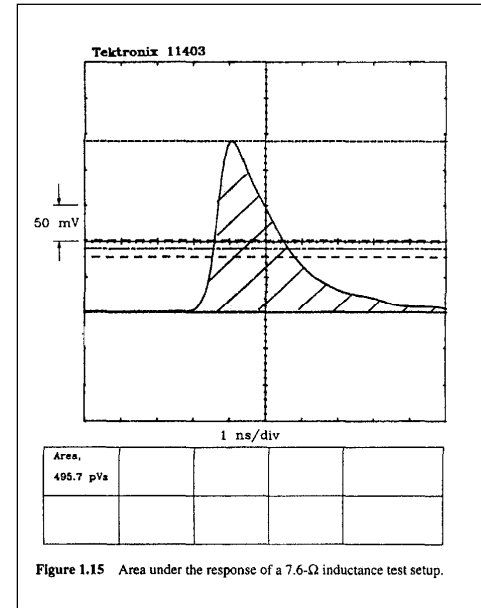


Figure 1.15 Area under the response of a 7.6-Ω inductance test setup.

$$R_s = (50+39) // 10 // 50 = 7.6 \text{ ohm}$$

- 50+39: toward source (pulse generator and series resistor)
- 10: to ground
- 50: toward scope (input impedance of the scope)

$$\int_0^{\infty} V_{inductor}(t) dt = L \int_0^{\infty} \left( \frac{dI}{dt} \right) dt$$

$$= L [I(\infty) - I(0)]$$

$$= L \Delta I$$

$$\int_0^{\infty} V_{inductor}(t) dt = Area$$

$$L = \frac{Area}{\Delta I} = \frac{Area \cdot R_s}{\Delta V}$$

$\Delta V$  : open circuit voltage  
 $R_s = 7.6 \Omega$

$$L = \frac{(495)(7.6)}{0.418} = 9nH$$

### 5.5 Small Capacitance Measurements

Unlike a small inductor, measuring a small capacitor with TDR is relatively easy. The time constant of series or parallel RC circuits has  $\exp(-t/RC)$  which can be significantly increased by choosing a large R value.

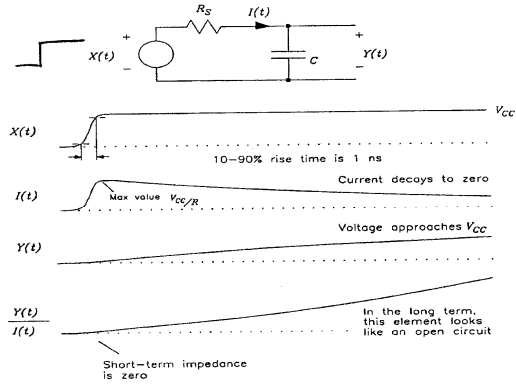


Figure 1.5 Step response of a perfect capacitor.

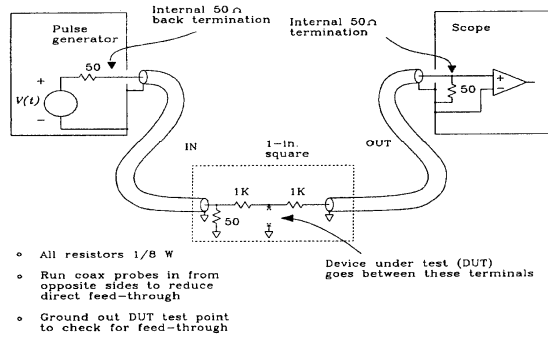


Figure 1.6 A 500-Ω lab setup for measuring capacitance.

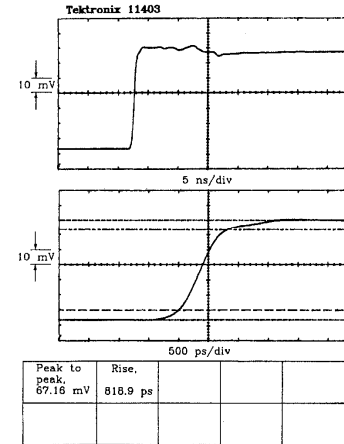


Figure 1.7 Open-circuit response of a 500-Ω capacitance test setup.


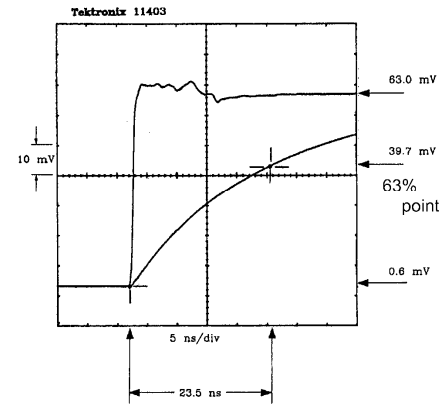


Figure 1.9 Finding a time constant using the 63% method.

$$1025 // 1050 = 503\Omega$$

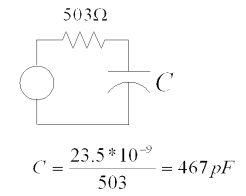



### Laplace Transform Theorem

$$X(s) = \int_0^{\infty} x(t)e^{-st} dt$$

$$x(t) = \frac{1}{2\pi} \int_{\sigma-j\infty}^{\sigma+j\infty} X(s)e^{st} ds$$

Name	Transform Pair
1. Linearity	$ax(t) + by(t) \leftrightarrow aX(s) + bY(s)$
2. Scale change	$x(at) \leftrightarrow \frac{1}{a}X\left(\frac{s}{a}\right) \quad a > 0$
3. Time delay	$x(t - t_0) \leftrightarrow X(s)e^{-st_0} \quad t_0 > 0$
4. s-Shift	$e^{-at}x(t) \leftrightarrow X(s + a)$
5. Multiplication by $t^n$	$t^n x(t) \leftrightarrow (-1)^n \frac{d^n X(s)}{ds^n} \quad n = 1, 2, \dots$
6. Time differentiation	$\frac{d^n x(t)}{dt^n} \leftrightarrow s^n X(s) - \sum_{i=0}^{n-1} s^{n-1-i} x^{(i)}(0^-)$ where $x^{(i)}(t) = \frac{d^i x(t)}{dt^i}$
7. Time integration	$y(t) = \int_{0^-}^t x(\lambda) d\lambda + y(0^-) \leftrightarrow \frac{X(s)}{s} + \frac{y(0^-)}{s}$
8. Convolution	$x(t) * y(t) \leftrightarrow X(s)Y(s)$
The final two theorems present equal expressions rather than transform pairs. Also, these two theorems are valid only if the conditions stated in Chapter 7 are satisfied.	
9. Final value	$\lim_{t \rightarrow \infty} x(t) = \lim_{s \rightarrow 0} sX(s)$
10. Initial value	$\lim_{t \rightarrow 0^+} x(t) = \lim_{s \rightarrow \infty} sX(s)$

Table C.4 Laplace Transform Pairs

$x(t)$	$X(s)$
1. $\delta(t)$	1
2. $u(t)$	$\frac{1}{s}$
3. $\frac{t^n}{n!} u(t)$	$\frac{1}{s^{n+1}}$
4. $e^{-at} u(t)$	$\frac{1}{s+a}$
5. $\frac{t^n e^{-at}}{n!} u(t)$	$\frac{1}{(s+a)^{n+1}}$
6. $\sin(\omega_0 t) u(t)$	$\frac{\omega_0}{s^2 + \omega_0^2}$
7. $\cos(\omega_0 t) u(t)$	$\frac{s}{s^2 + \omega_0^2}$
8. $t \sin(\omega_0 t) u(t)$	$\frac{2\omega_0 s}{(s^2 + \omega_0^2)^2}$
9. $t \cos(\omega_0 t) u(t)$	$\frac{(s^2 - \omega_0^2)}{(s^2 + \omega_0^2)^2}$
10. $e^{-at} \sin(\omega_0 t) u(t)$	$\frac{\omega_0}{(s+a)^2 + \omega_0^2}$
11. $e^{-at} \cos(\omega_0 t) u(t)$	$\frac{s+a}{(s+a)^2 + \omega_0^2}$
12. $2Ce^{-at} \cos(\omega_0 t) u(t) + 2De^{-at} \sin(\omega_0 t) u(t)$	$(C + jD)/(s + a + j\omega_0) + (C - jD)/(s + a - j\omega_0)$
13. $Ee^{-at} \cos(\omega_0 t) u(t) + ((F - Ea)/\omega_0)e^{-at} \sin(\omega_0 t) u(t)$	$\frac{Es + F}{s^2 + es + f} \quad \omega_0 = \sqrt{f - a^2} \quad a = e/2$