

# Physics 115

## General Physics II


### Session 23

### Series and parallel R

### Real Batteries
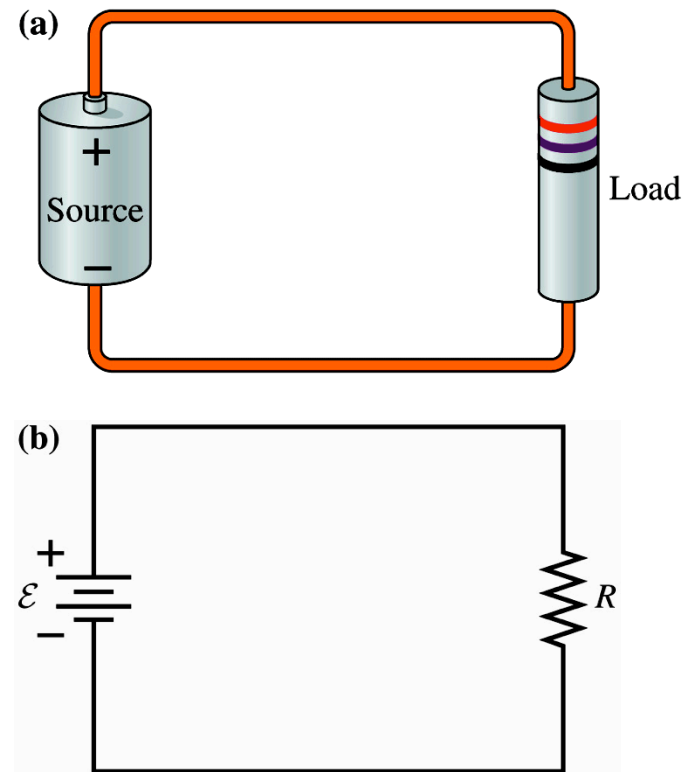
### Meters

- R. J. Wilkes
- Email: [phy115a@u.washington.edu](mailto:phy115a@u.washington.edu)
- Home page: <http://courses.washington.edu/phy115a/>




# Lecture Schedule


<b>12-May</b>	Mon	23	DC Circuits & Meters	21.5-21.8
<b>13-May</b>	Tues	24	DC Circuits	21.5-21.8
<b>15-May</b>	Thurs	25	RC circuits	21.6-21.7
<b>16-May</b>	Fri	26	Circuits - Neurons	
<b>19-May</b>	Mon	27	Magnetism	22.1
<b>20-May</b>	Tues	28	Magnetic Force	22.2-22.5
<b>22-May</b>	Thurs	29	Magnetic Fields	22.6-22.7
<b>22-May</b>	Fri	30	Induced EMF, Applications	23.1-23.3
<b>26-May</b>	<b>holiday</b>		<b>NO CLASS</b>	
<b>27-May</b>	Tues	31	Energy, RL circuits	23.4-23.8
<b>29-May</b>	Thurs	32	Transformer	23.9-23.10
<b>30-May</b>	<b>Fri</b>		<b>EXAM 3 - Chapters 21,22,23</b>	
<b>2-Jun</b>	Mon	33	AC circuits	24.1-24.3
<b>3-Jun</b>	Tues	34	AC circuits	24.4-24.5
<b>5-Jun</b>	Thurs	35	Resonance, Applications	24.6
<b>6-Jun</b>	Fri	36	Last class - review	
<b>June 9</b>	<b>FINAL EXAM</b>			<b>Comprehensive</b>
	Mon	2:30-4:20 p.m. Monday, June 9, 2014		<b>Today</b>
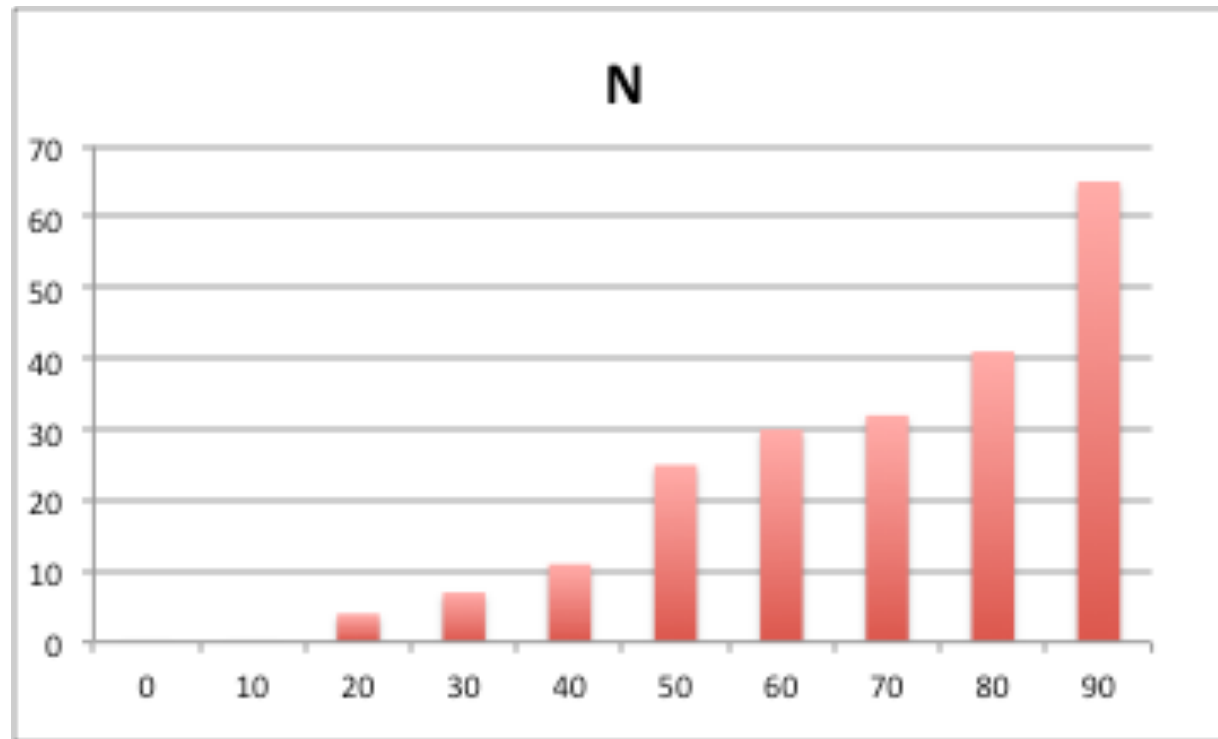
# Announcements

- Exam 2 results (posted on WebAssign and Catalyst Gradebook)
  - Average = 76, standard deviation = 19



Questions are worth points shown

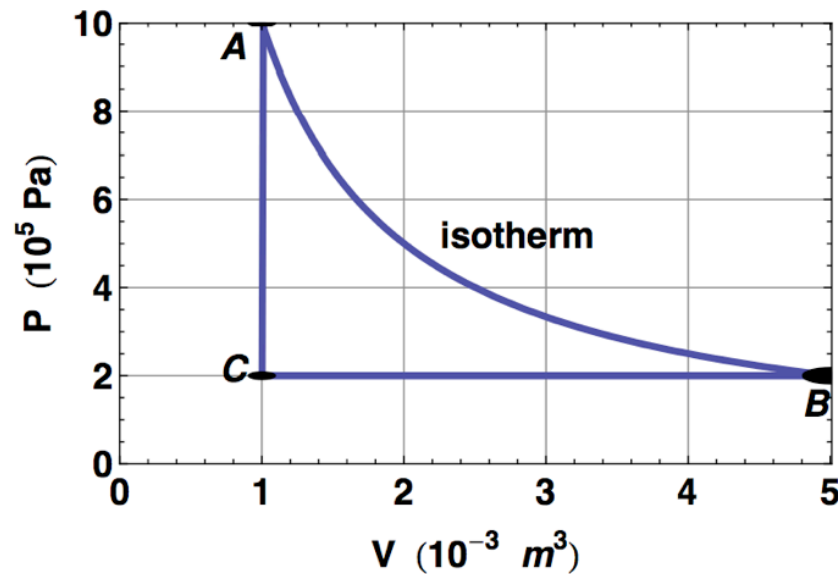

For questions 1-5: Working fluid for the P-V diagram above is an ideal monatomic gas.

For this system  $Nk = 2$  SI units.  $PV = NkT$

The area under the Isotherm between  $V = 1$  and  $V = 5 \cdot 10^{-3} \text{ m}^3$  is approx. 1600 J (or N-m).

Temperatures are:  $T_A$ ,  $T_B$ ,  $T_C$

1. (8 pts.) What is the temperature,  $T_A$  (K) at point A?

- A) 200
- B) 100
- C) 400
- D) 500
- E) 1000

**Ans: D.**  $T = PV/Nk = (10^6 \text{ Pa})(10^{-3} \text{ m}^3)/2 = 500 \text{ K}$

2. (4 pts.) What is the temperature,  $T_B$  at point B?

A)  $T_A$

B)  $T_A / 2$

C)  $T_A / 10$

D)  $T_A / 5$

E)  $T_A / 2.5$

**Ans: A. Isothermal connects A and B**

3. (6 pts) During the process A to B is work ( $W_{AB}$ ) done by the gas or on the gas?

A) By

B) On

C) No work is done

**Ans: A. Gas is expanding, work is done BY gas**

4. (6 pts) During the process A to B, does heat ( $Q_{AB}$ ) flow into the gas or out of the gas?

A. Into

B. Out of

C. No heat flow

**Ans: A. Work is done BY gas, so must add heat to keep  $U$  ( $\sim T$ ) constant.**

5. (6 pts) During the process B to C, is work ( $W_{BC}$ ) done by the gas or on the gas?

A. By

B. On

C. No work done

**Ans: B. Compression at constant  $P$ , so work done ON gas = area under B-C curve**

6. What is the efficiency of a heat engine that exhausts 1200 J of heat in the process of doing 250 J of work ?

- A. 75 %
- B. 33 %
- C. 47 %
- D. 66 %
- E. 17 %

**Ans: E.**  $Q_H = Q_C + W = 1200\text{J} + 250\text{J}$ ;  $\epsilon = 1 - (Q_C / Q_H) = 1 - (1200\text{J}/1450\text{J}) = 0.17$

7. With the pressure held constant at 170 kPa, 50 mol of an ideal monatomic gas expands from an initial volume of 1.5 m<sup>3</sup> to a final volume of 2.9 m<sup>3</sup>.

How much work was done by the gas during the expansion?

- A. 189 kJ
- B. 200
- C. 67
- D. 238
- E. 100

**Ans: D.**  $W = P\Delta V = 170\text{kPa} (2.9 - 1.5 \text{ m}^3) = 238 \text{ kJ}$

8. An air conditioner which is an ideal Carnot engine operates between an indoor temperature of 20°C and an outdoor temperature of 39°C. How much energy (work) must it provide to remove 2000 J of heat from the inside of the house?

- A) 105 J
- B) 130 J
- C) 780 J
- D) 520 J
- E) 340 J

**Ans: B.** Carnot efficiency  $= (1 - T_c / T_h) = (1 - Q_c / Q_h) \rightarrow Q_h = Q_c (T_h / T_c)$   
 $= 2000(312/293) = 2129.7 \text{ J}$  so require  $W = Q_h - Q_c = 129.7 \text{ J}$

9. Find the change in Entropy when 1 kg of water is boiled away to steam .  
(both water and steam are at 100 °C )

- A. 9.71 kJ/Kelvin
- B. 6.06
- C. 1.94
- D. 5.62
- E. 4.56

**Ans: B.**  $\Delta Q = mL = 1\text{kg} (2.26 \times 10^6 \text{ J/kg})$ ;  $\Delta S = \Delta Q / T = 2.26 \times 10^6 \text{ J} / 373\text{K} = 6.06 \text{ kJ/K}$

10. What is the magnitude of the electric field produced at a distance of 520 m by a charge of 7 Coulombs ?

- A. 0.38 Megavolts/meter
- B. 1.73
- C. 0.23
- D. 1.94
- E. 6.37

**Ans: C.**  $E = k Q / R^2 = (8.99 \times 10^9 \text{ N.m}^2/\text{C}^2)(7\text{C}) / (520 \text{ m})^2 = 0.233 \text{ MV/m}$


11. A box in the form of a Tetrahedron contains electric charge. The electric fluxes through the four sides of the box are as follows :

$$\text{Flux1} = -113 \text{ N. m}^2/\text{C} ;$$

$$\text{Flux2} = +144 \text{ N. m}^2/\text{C};$$

$$\text{Flux3} = +26 \text{ N. m}^2/\text{C};$$
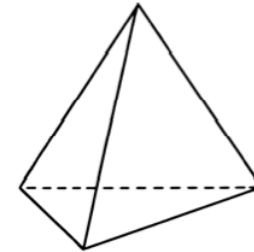
$$\text{Flux4} = -12 \text{ N. m}^2/\text{C}$$



Find the electric charge inside this box.

A. 0.398 nano Coulombs

B. 0.144

C. 0.74

D. 0.796

E. -0.74

**Ans: A.  $\Sigma \Phi = 45 \text{ N. m}^2/\text{C} = Q/\epsilon_0$  ;  $Q = 45 \text{ N. m}^2/\text{C} (8.85 \times 10^{-12} \text{ C}^2/\text{N.m}^2) = 0.398 \times 10^{-9} \text{ C}$**



For questions 12-13: An isolated parallel-plate capacitor has plates with an area of  $0.017 \text{ m}^2$  and separation of  $0.87 \text{ mm}$ . Initially, the space between the plates is filled with a dielectric whose dielectric constant is  $2.0$ .

12. What is the potential difference between the plates when the charge on the capacitor plates is  $\pm 4.7 \text{ } \mu\text{C}$ ?

- A)  $13.6 \text{ kV}$
- B)  $27.2 \text{ kV}$
- C)  $54.4 \text{ kV}$
- D) none of the above

**Ans: A**

$$\begin{aligned} C &= \kappa(\epsilon_0 A / d) \\ &= 2(8.85 \times 10^{-12} \text{ F/m})(0.017 \text{ m}^2) / 0.00087 \text{ m} \\ &= 344 \text{ pF} \\ V &= Q / C = (4.7 \times 10^{-6} \text{ C}) / (344 \times 10^{-12} \text{ F}) = 13.6 \text{ kV} \end{aligned}$$

13. (4 pts.) Would your previous answer increase, decrease, or stay the same, if we remove the dielectric material, leaving the gap empty space (so, the dielectric constant is reduced to  $1.0$ ), all else staying the same?

- A) stay the same
- B) increase
- C) decrease

**Ans: B. increase, because  $V$  is inversely proportional to  $\kappa$ :  $V = Q/C = Q/(\kappa C_0)$ .**

14. Find the electric energy density between the plates of a 1.0 F parallel plate capacitor. The potential difference between the plates is 100 V and the plate separation is 1 mm . There is a vacuum between the plates.

- A.  $0.067 \text{ J/m}^3$
- B. 0.172
- C. 0.057
- D. 0.044
- E. 0.095

**Ans: D.**  $-E = \Delta V / \Delta s = (100\text{V} / 0.001\text{m}) = 100\text{kV/m}$ ;  $u = \frac{1}{2}\epsilon_0 E^2 = \frac{1}{2} (8.85 \times 10^{-12})(10^5)^2 \text{ J/m}^3$


15. An electron accelerates through a potential difference of 3000 V from rest . Find its final velocity .

- A. 0.42 (  $\times 10^8 \text{ m/s}$  )
- B. 0.32
- C. 1.3
- D. 0.76
- E. 0.15

**Ans: B.**  $KE = \Delta U$ ;  $\frac{1}{2}mv^2 = q\Delta V$ ;  $v^2 = 2q\Delta V/m$

$v^2 = 2(1.6 \times 10^{-19} \text{ C})3000\text{V} / (9.11 \times 10^{-31}\text{kg}) = 1054 \times 10^{12}$ ;  $v = 32 \times 10^6 \text{ m/s}$

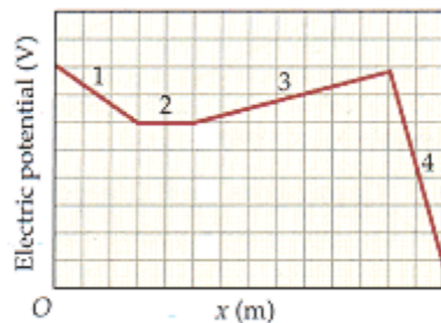For questions 16 -18: As a positive test charge moves along the  $x$  axis from  $x = 0$  to  $x = 1.4$  m, the electric potential it experiences is shown in the figure, below. (The horizontal axis is marked in increments of 0.1 m and the vertical axis is marked in increments of 0.5 V.)



16. (4 pts.) For which part of its path is the electrostatic force on the charge zero?

- A. segment 1
- B. segment 2
- C. segment 3
- D. segment 4
- E. none of the above

**Ans: B ( $E=0=\text{slope of plot; slope}=0$  for segment 2)**

17. (4 pts.) For which part of its path does the electrostatic force point in the  $-x$  direction?

- A. segment 1
- B. segment 2
- C. segment 3
- D. segment 4
- E. none of the above

**Ans: C ( $E = \text{negative; slope of 3} = \text{negative}$ )**

18. (4 pts.) For which part of its path is the electrostatic force largest in magnitude?

- A. segment 1
- B. segment 2
- C. segment 3
- D. segment 4
- E. none of the above

**Ans: D (slope=steepest)**

$$P = V^2 / R$$

Example: bright and dim bulbs

1. How much **current** is “drawn” by a 100 W light bulb connected to a 120 V outlet?


$$I = \frac{P}{\Delta V_R} = \frac{(100 \text{ W})}{(120 \text{ V})} = 0.833 \text{ A}$$

2. How much **power** is used by a 60 W light bulb rated at 120 V if it is operated at 100 V, using a dimmer control? (Assume its resistance stays the same.)

$$\Delta V = \frac{P}{I} = \frac{P}{\Delta V / R} \quad \text{so} \quad R = \frac{(\Delta V)^2}{P} = \frac{(120 \text{ V})^2}{(60 \text{ W})} = 240 \, \Omega \quad \text{(from specifications: 120V bulb)}$$

$$P = (\Delta V)^2 / R = (100 \text{ V})^2 / (240 \, \Omega) = 42 \text{ W} \quad \text{(100V, as used here)}$$

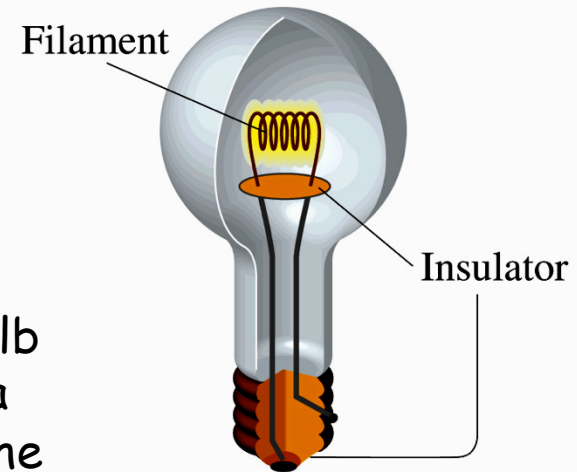(Actually, the resistance at this lower operating V will be less than the R calculated here, because the filament temperature will be lower.)




# Bulbs in Series

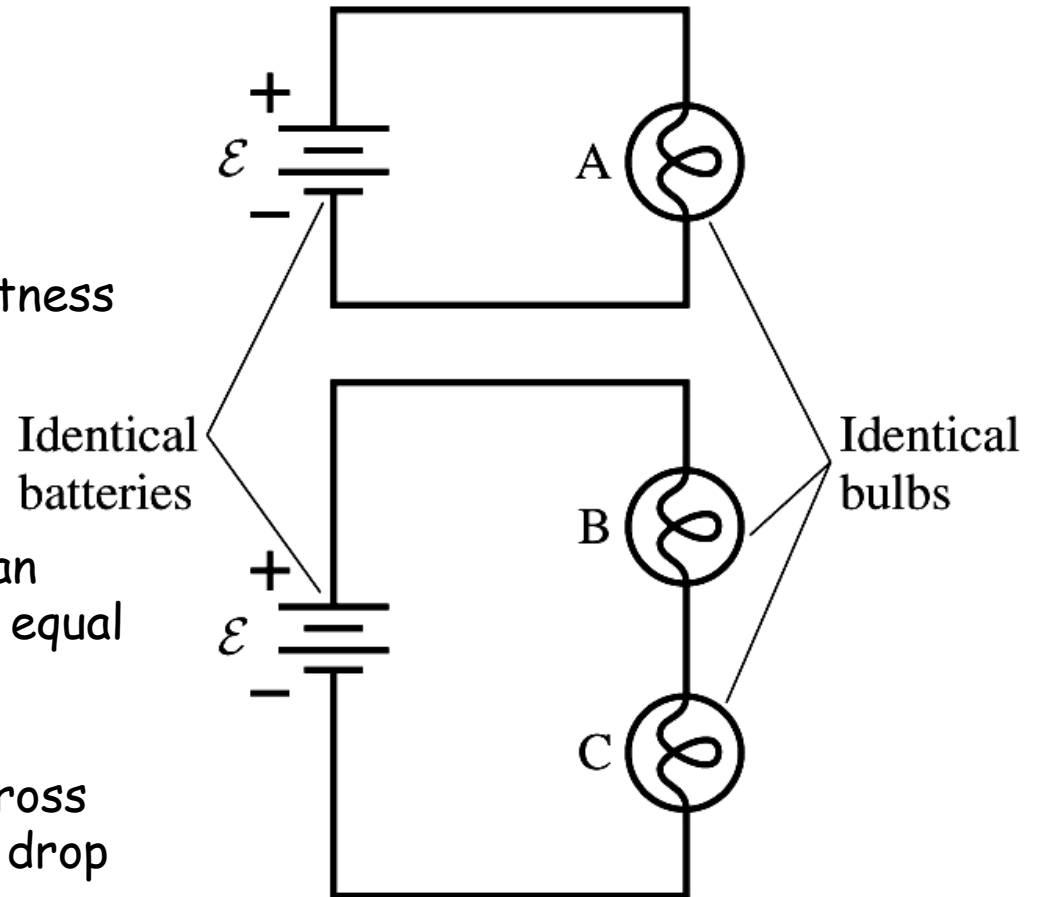**Question:** How does the brightness of bulb A compare with that of bulbs B and C?

**Answer:** Bulb A is brighter than bulb B and bulb C, which are of equal brightness.


**Reason:** The potential drop across bulb A is  $\mathcal{E}$ , while the potential drop across B and across C is  $\mathcal{E}/2$ .



# Bulbs in Parallel


Initially, bulbs A and B have the same brightness and C is out. What happens to the brightness of the bulbs when the switch is closed?

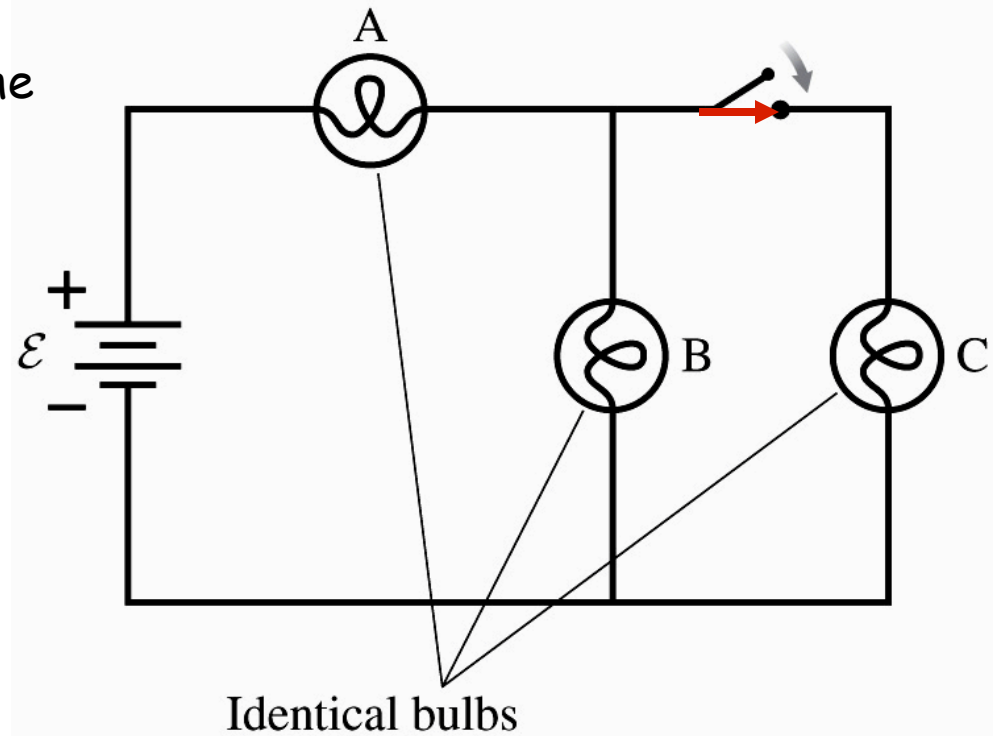1. Bulb A gets brighter (because the overall current increases);
2. Bulb B gets dimmer (because current is diverted to Bulb C);
3. Bulb C glows with the same brightness as B (because they split the current equally).


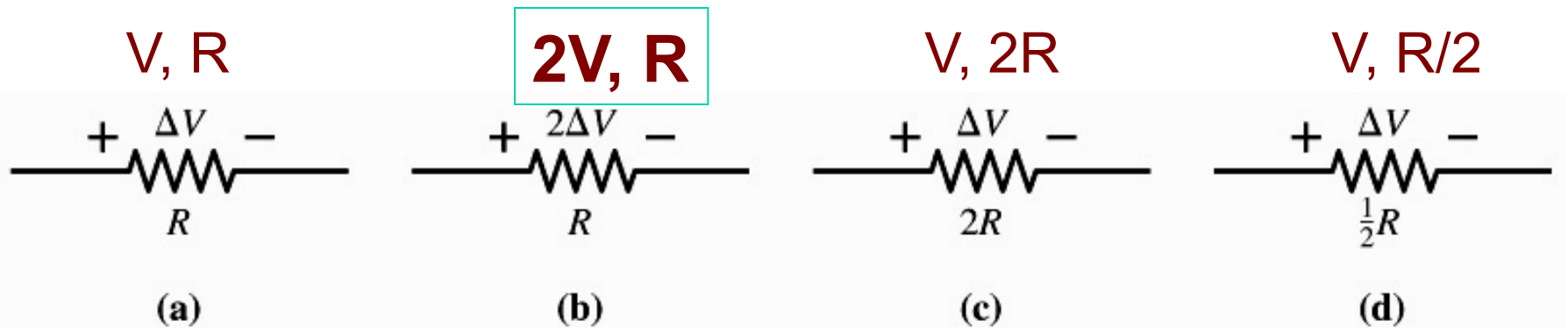
## Clicker Question 15

Which resistor dissipates the **most** power?



$$P \propto V^2 / R$$

So power compared to case A is:  $B=4A$ ,  $C=A/2$ ,  $D=2A$

## Series circuits applications


## Real vs Ideal Batteries: Internal Resistance

**Ideal** batteries maintain  $\mathcal{E}$  regardless of load, but

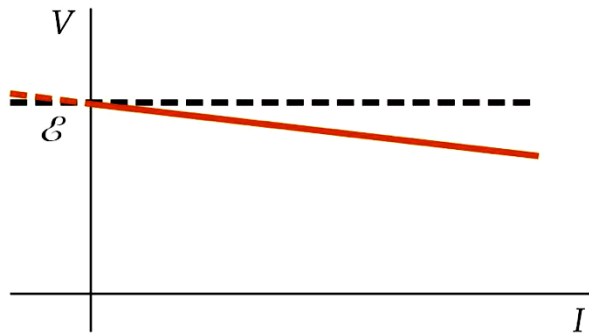**Real** batteries have **internal resistance**

We model a real battery as ( ideal battery + resistor  $r$  )

so  $\mathcal{E}$  on terminals comes **after** a voltage drop  $V = I r$  :




$$V_a = V_b + \mathcal{E} - I r$$

$$V_a - V_b = \mathcal{E} - I r$$

$$I R = V_a - V_b = \mathcal{E} - I r$$

$$I = \frac{\mathcal{E}}{R + r}$$

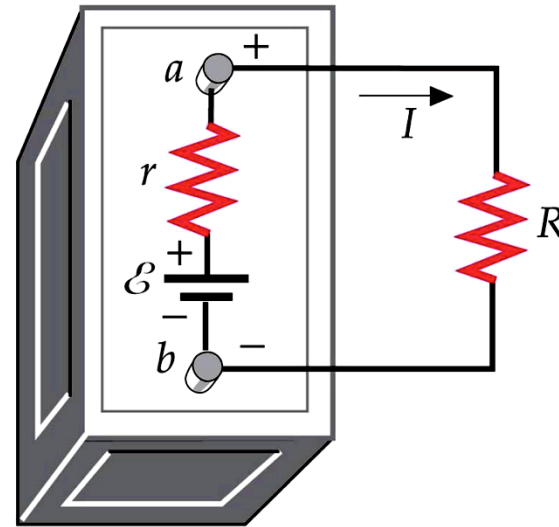

Current\*time = charge

1 ampere-sec = 1 C

Large batteries are rated in A-hrs

$$1 \text{ A h} = 3600 \text{ C}$$

$$E_{\text{stored}} = Q \mathcal{E}$$

Typical car batteries are rated 50 A-hr or more



# Bad way to measure $r$ : Short Circuits

"Short circuit" = zero  $R$  path for  $I$ .

What if you "short out" a battery, i.e., connect an ideal ( $R=0$ ) wire across its terminals?

The potential difference across its terminals becomes zero, so


$$I_{\text{short}} = \mathcal{E} / r$$

All of the battery's EMF is now dropped across its internal resistance,  $r$ .

$I_{\text{short}}$  is the maximum possible current that the battery can supply

It is a measure of the internal resistance  $r$  of the battery:

$$r = \mathcal{E} / I_{\text{short}}$$

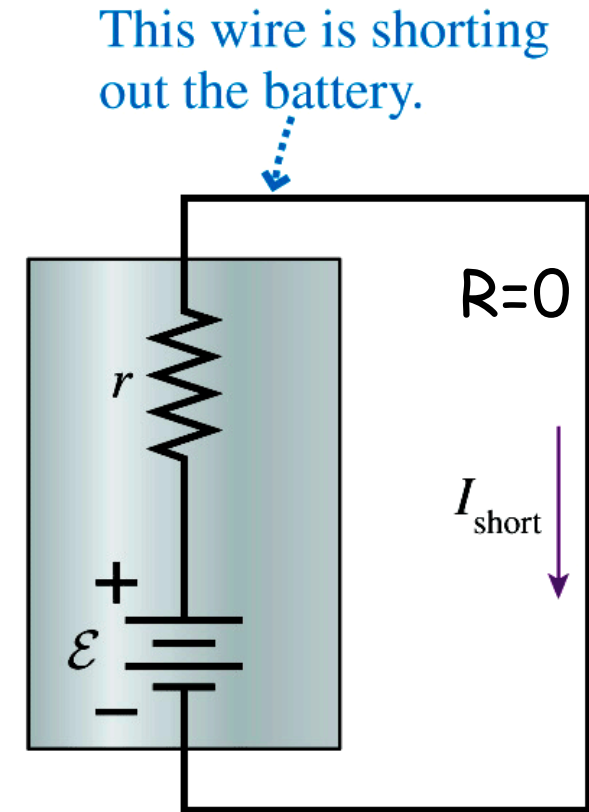

## Example: A Short-Circuited Car Battery


What is the short-circuit current of a 12 V car battery with an internal resistance of  $0.020\ \Omega$ ?

What happens to the power supplied by the battery when it is shorted?

$$I_{\text{short}} = \frac{\mathcal{E}}{r} = \frac{(12\ \text{V})}{(0.020\ \Omega)} = 600\ \text{A}$$

$$P = I^2 r = (600\ \text{A})^2 (0.020\ \Omega) = 7,200\ \text{W}$$

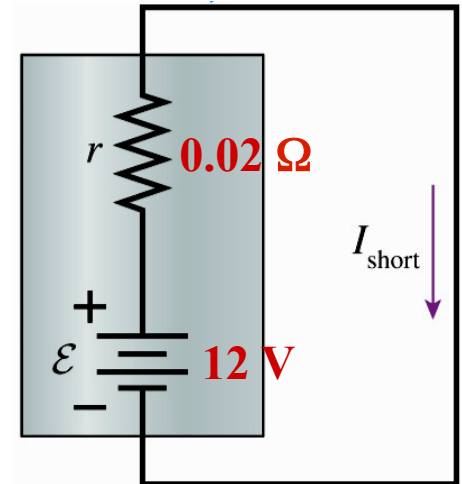**All** of this power would be dissipated inside the battery, making it likely to explode.  
Do not short out your car's battery!




# Better way to measure internal resistance

- We can determine the effective  $r$  in a battery by comparing “open-circuit voltage” (when  $I = 0$ ) to the voltage we measure when some **known current** is drawn
  - **Measure voltage** across terminals a-b, with nothing connected:  $V_0$
  - Attach some load and measure the current flowing, then also measure the voltage across the battery terminals,  $V_I$
  - Then  $V_0 = \mathcal{E}$ , and  $V_I = \mathcal{E} - I r$
  - **So  $r = (\mathcal{E} - V_I) / I$**
- Example: 12 V car battery
  - Open-circuit, we measure  $V_0 = 12.0 \text{ V}$
  - With 2 amps current flowing,  $V_I = 8.0 \text{ V}$
  - Then  $r = (12 - 8) / 2 = 2 \text{ ohms}$
  - What will battery terminal voltage be for  $I=5\text{A}$ ?

**$V_{I=20\text{A}} = \mathcal{E} - I r = 12\text{V} - 5\text{A}(2 \text{ ohms}) = 2 \text{ V}$**

This battery is not very useful !

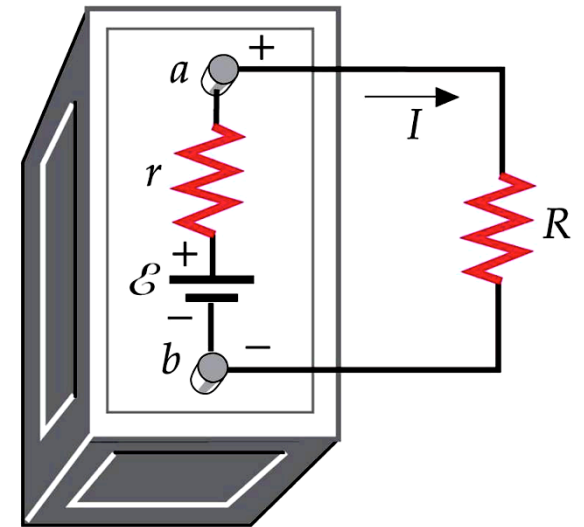

## Example: Lighting Up a Flashlight

A  $6\ \Omega$  flashlight bulb is powered by a  $3\ \text{V}$  battery with internal resistance of  $1\ \Omega$ . (Assume ideal wires.)

What is the power dissipation of the bulb in this circuit?

What is the terminal voltage of the battery when bulb is on?

$$I = \frac{E}{R + r} = \frac{(3\ \text{V})}{(6\ \Omega) + (1\ \Omega)} = 0.43\ \text{A}$$

$$P_R = I^2 R = (0.43\ \text{A})^2 (6\ \Omega) = 1.1\ \text{W}$$


$$P_r = I^2 r = (0.43\ \text{A})^2 (1\ \Omega) = 0.185\ \text{W}$$

About 15% of the total **power** consumed goes into heating the battery rather than lighting the bulb.

$$\Delta V_{\text{bat}} = E - Ir = (3\ \text{V}) - (0.43\ \text{A})(1\ \Omega) = 2.57\ \text{V}$$

# Ammeters

(a)

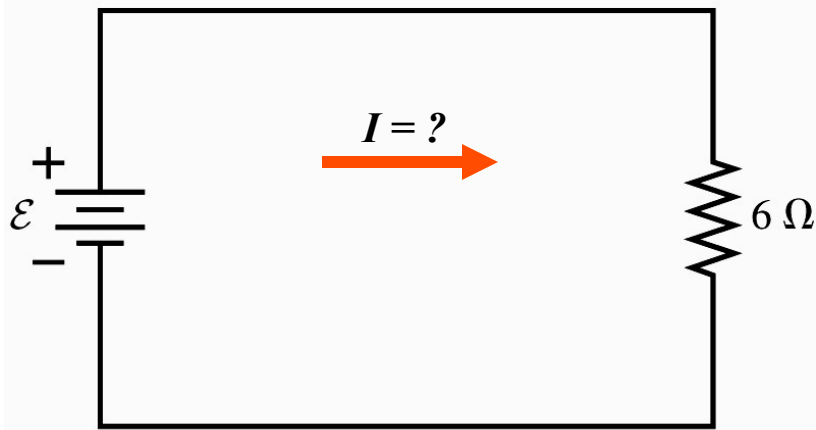


**Question:** How can you measure the **current** in a circuit?

**Ideal Ammeter:** To have a minimum effect on the current being measured, the ammeter must have **zero resistance**, so that there is zero potential difference across the ammeter. Electronic ammeters can give good approximations to this condition.

**Note:** “Clip on” ammeters that measure AC current without breaking the circuit are commercially available. They use magnetic induction (...later).

(b)

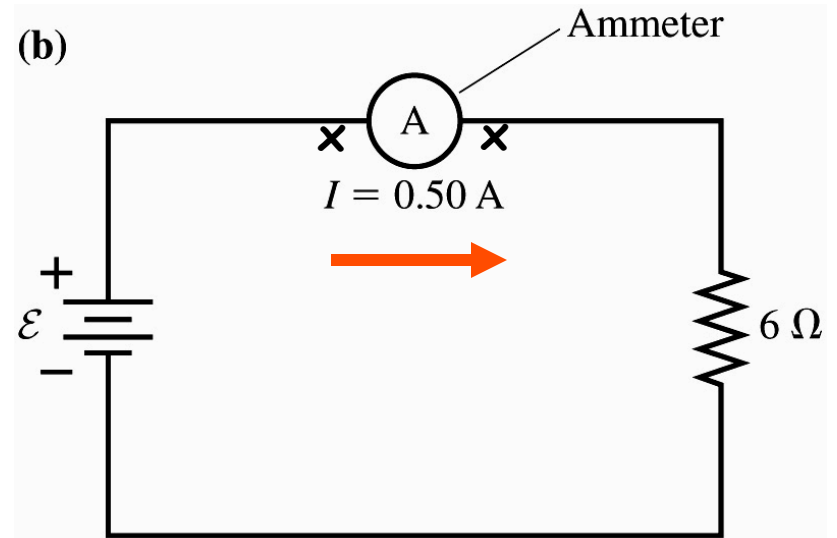


**Answer:** You must **break the circuit** and **insert** an ammeter into the current.

# Voltmeters

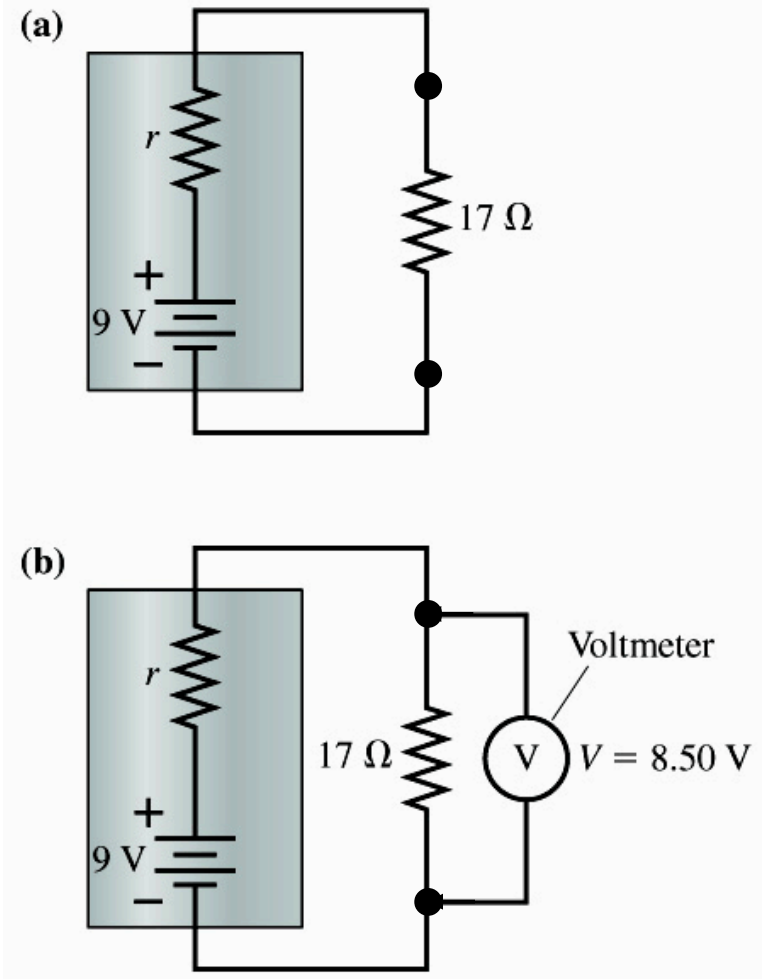**Question:** How do you measure the **potential difference** between two points in a circuit?

**Answer:** connect one lead of a **voltmeter** to each point.


**Ideal Voltmeter:** To have a minimum effect of the circuit being measured, the connected voltmeter must have **infinite resistance**, so that no current is diverted through the voltmeter. Electronic voltmeters can give good approximations to this condition, but electro-mechanical voltmeters may not.



## So - What is a voltmeter or ammeter?
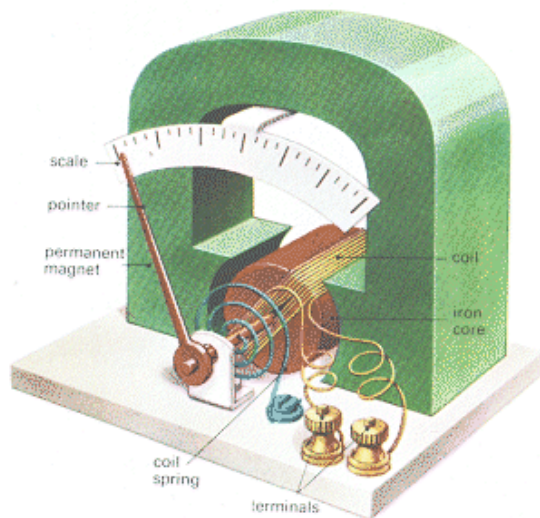
### 1. Old fashioned electro-mechanical meters (obsolete but still used)

- “Galvanometer” :
  - Coil in a magnetic field rotates in proportion to  $I$  in coil
  - We'll learn about how this works in a few days
  - Generic sensing device for 19<sup>th</sup> and early 20<sup>th</sup> C.
- Calibrate its deflection vs  $I$  : you have an **ammeter**
- To measure volts: use ammeter to measure  $I$  through a known large  $R$ 
  - Large  $R$ , so  $I$  drawn by meter is very small – must not significantly affect circuit being measured !
  - Then  $V$  across meter terminals =  $I R$ , neglecting  $R$  of meter itself
- Then mark the meter face with  $V$ 's corresponding to  $I$  values: **voltmeter**





# What is a voltmeter or ammeter?

- Modern digital meters
  - “Analog to digital converter” (ADC) chips produce computer-readable digits proportional to voltage across their inputs
  - If you want to measure  $I$ , put a small  $R$  across the ADC and measure  $V$ 
    - Small  $R$  because you must not significantly affect current being measured
  - “Digital multimeter” = device that can measure  $I$ ,  $V$ , or  $R$ , in one package

