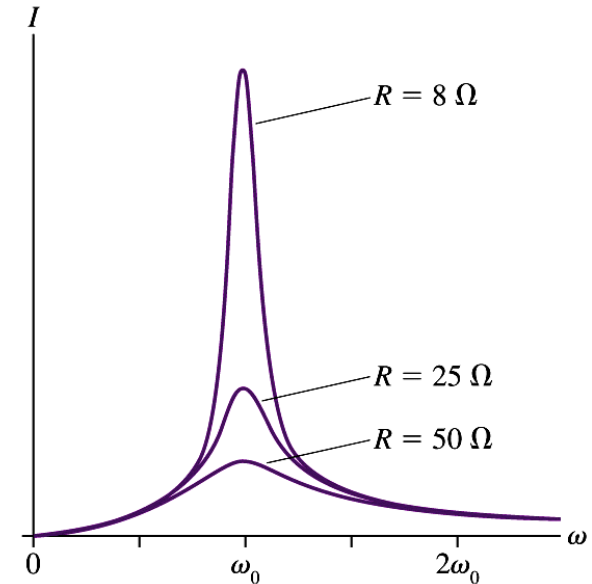


Physics 115

General Physics II

Session 34

Inductors, Capacitors, and RLC circuits



- **R. J. Wilkes**
- Email: phy115a@u.washington.edu
- Home page: <http://courses.washington.edu/phy115a/>

Lecture Schedule

12-May	Mon	23	DC Circuits & Meters	21.5-21.8
13-May	Tues	24	DC Circuits	21.5-21.8
15-May	Thurs	25	RC circuits	21.6-21.7
16-May	Fri	26	Circuits - Neurons	
19-May	Mon	27	Magnetism	22.1
20-May	Tues	28	Magnetic Force	22.2-22.5
22-May	Thurs	29	Magnetic Fields	22.6-22.7
22-May	Fri	30	Induced EMF, Applications	23.1-23.3
26-May	<i>holiday</i>		NO CLASS	
27-May	Tues	31	Energy, RL circuits	23.4-23.8
29-May	Thurs	32	Transformer	23.9-23.10
30-May	Fri		EXAM 3 - Chapters 21,22,23	
2-Jun	Mon	33	AC circuits	24.1-24.3
3-Jun	Tues	34	AC circuits	24.4-24.5
5-Jun	Thurs	35	Resonance, Applications	24.6
6-Jun	Fri	36	Last class - review	
June 9	FINAL EXAM			Comprehens
	2:30-4:20 p.m.			
	Mon	Monday, June 9, 2014		

Today

Announcements

Final exam is **2:30 pm, Monday 6/9, here**

- 2 hrs allowed for exam (really: 1 to 1.5 hr), comprehensive, but with extra items on material covered after exam 3
- Usual arrangements
- If you took midterms with section B please do **NOT** do that for final – everyone takes it with our group on Monday
- Final exam will contain ONLY Ch. 24 topics covered in class
- I will be away all next week
 - Final exam will be hosted by Dr. Scott Davis
 - If you need to see me, do so this week...
 - Exam scores and grade data will be posted before the end of next week, final grades before Tuesday 6/17
- TA Songci Li will have office hour **MONDAY** 12:30-1:30, B-442 PAB
- Homework set 9 is due **Friday** 6/6 11:59pm


Announcements

“How best to study for final? ”

- Review and work to understand what you did not get right when you did HW problems, quizzes, or mid-term exam questions.
- Final Exam will not go into tricky details or fine points! Focus on main ideas
- A few practice questions for ch. 24 will be posted tonight, reviewed Friday in class

Inductors can make sparks

Electromagnet circuit

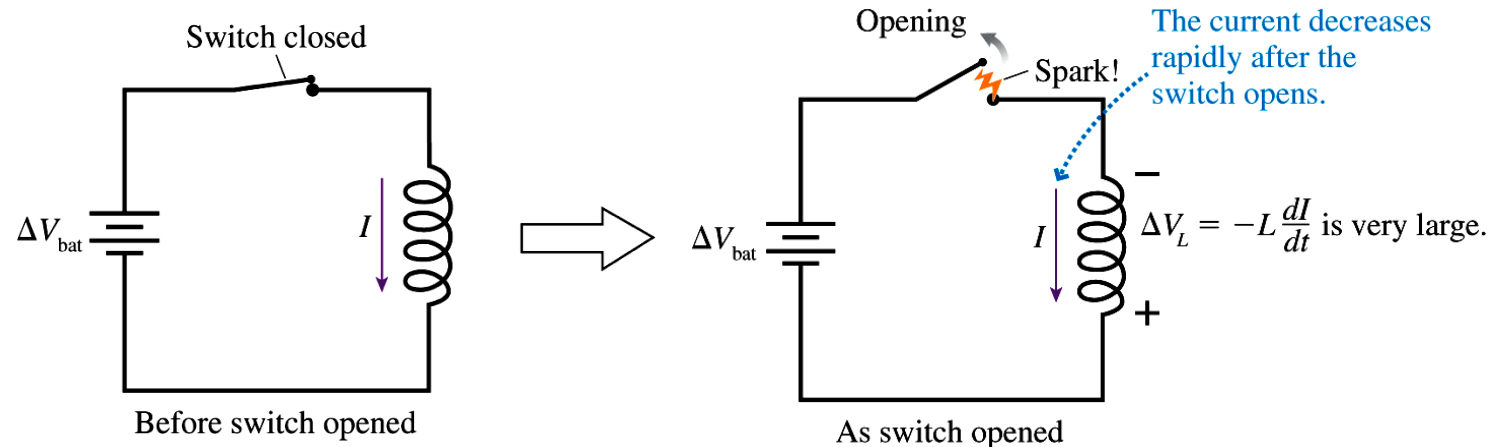



If we **quickly** interrupt DC current flow through an inductor, the back-EMF may cause a very large voltage ($L \frac{dI}{dt}$) across its terminals. The induced V typically causes an arc (spark) across the switch or broken wire that is breaking the current.

Example: large electric motors act like inductors - a simple on/off switch would pull a spark when opened

Sparks can damage switches or cause fires, so we use special switch arrangements in such circuits



Make-Before-Break Switches

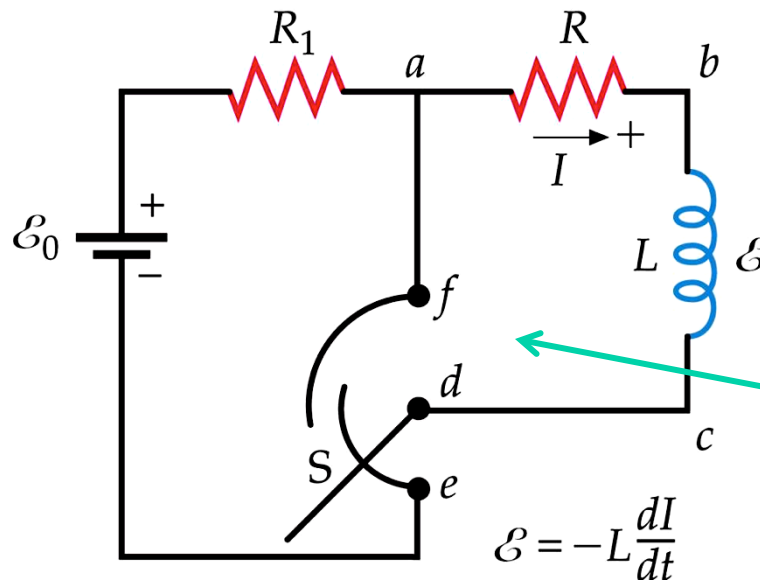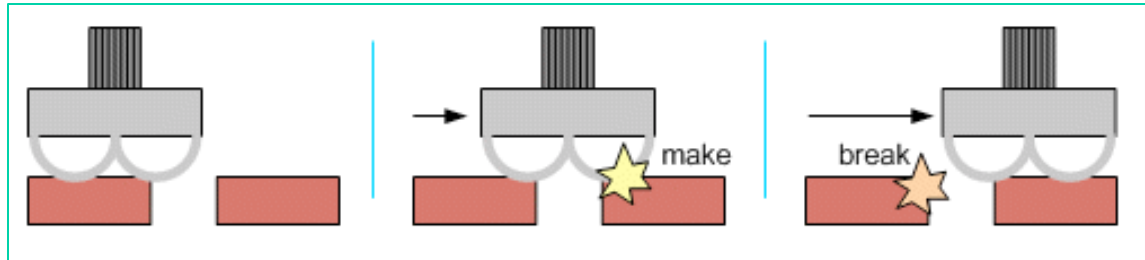

Sliding contacts: d-f is closed **before** d-e opens

Special “make-before-break” switches are used for inductive circuits: the inductor is shorted across a resistor **before** the switch actually opens the circuit. **R** dissipates the current generated by back-EMF, and **R_1** keeps the EMF source from being shorted out.

Example: Large Voltage across an Inductor

A 1.0 A current passes through a 10 mH inductor coil.

What potential difference is induced across the coil if the current drops to zero in 5 μs ?

$$\frac{dI}{dt} = \frac{\Delta I}{\Delta t} = \frac{(-1.0 \text{ A})}{(5.0 \times 10^{-6} \text{ s})} = -2.0 \times 10^5 \text{ A/s}$$


$$\Delta V_L = -L \frac{dI}{dt} = -(0.010 \text{ H})(-2.0 \times 10^5 \text{ A/s}) = 2000 \text{ V}$$

Big jolt from a small current and inductance! Where does the energy for this come from...?

Example: Inductive reactance

A 10 H inductor is connected to a 1000 Hz oscillator with a peak emf of 5.0 V.

What is the RMS current in the inductor?

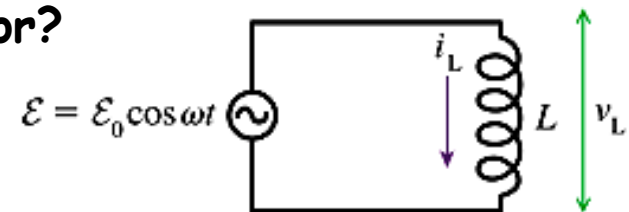

$$X_L(1000 \text{ Hz}) = 2\pi fL = 2\pi(1000 \text{ s}^{-1})(10 \text{ H}) = 6.28 \times 10^4 \Omega$$

$$I_{L(PEAK)} = \frac{V_{PEAK}}{X_L} = \frac{(5.0 \text{ V})}{(6.28 \times 10^4 \Omega)} = 8 \times 10^{-5} \text{ A} \quad (80 \mu\text{A})$$

$$I_{RMS} = \frac{I_{PEAK}}{\sqrt{2}} = 0.707 I_{PEAK} = 56 \mu\text{A}$$


Remember:
Reactance does not *dissipate* energy like a resistor: energy is *stored* in electromagnetic fields

Capacitors and springs


AC voltage and current in reactance are related like position and velocity in a spring+mass system: when one is max the other is zero

AC current through a capacitor *leads* the capacitor voltage by $\pi/2$ rad or 90° .

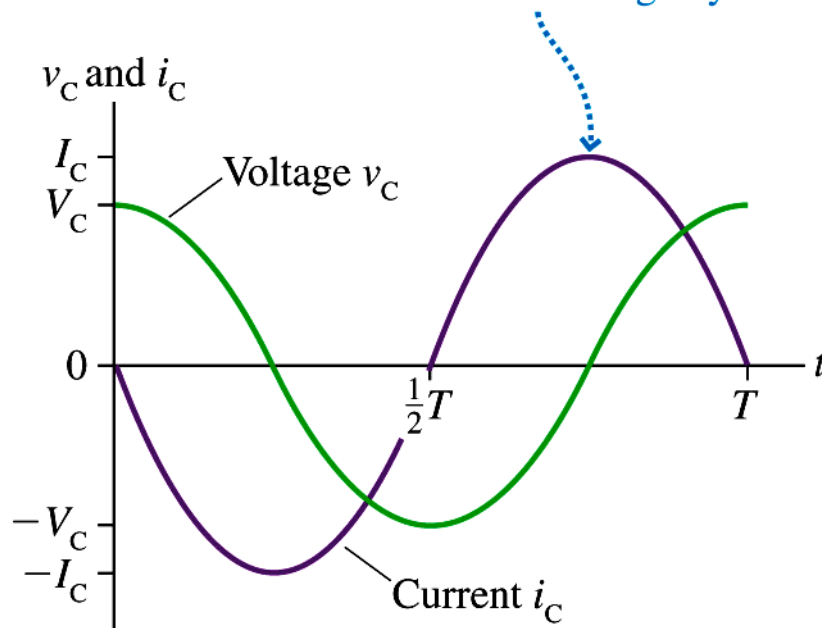- (a) i_C peaks $\frac{1}{4}T$ before v_C peaks. We say that the current *leads* the voltage by 90° .



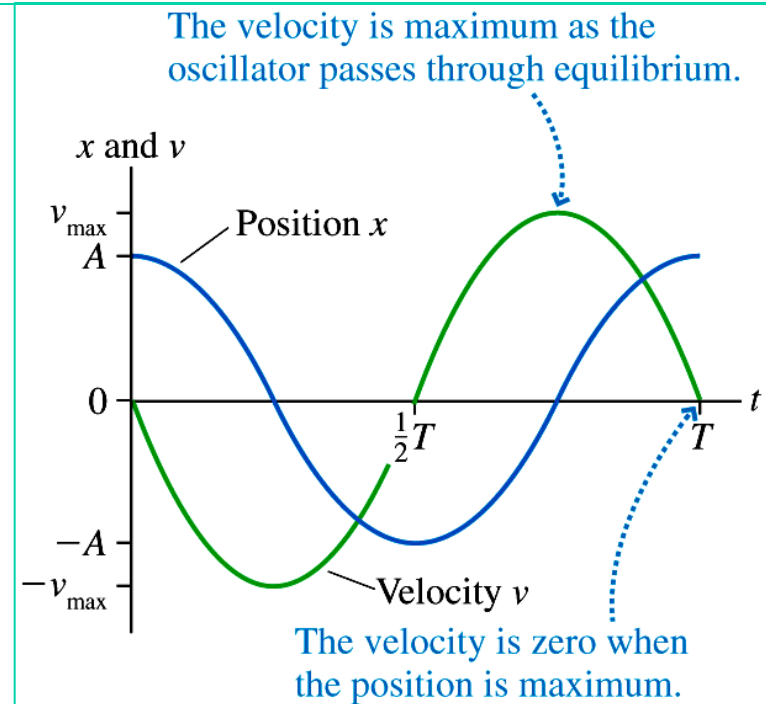This is just like the relationship of the position and velocity for a mass + spring, or a pendulum.



LC circuits - resonance

For an LC circuit, suppose we put charge Q on the capacitor initially.

Once the switch closes,

charge flows from C through L (E field decreases, B field increases) and back again: oscillation of current flow (AC).

(if we really had no R , it would go on forever)

"It can be shown" that for this situation,

Q varies sinusoidally:

$$Q(t) = Q_{PEAK} \cos(\omega t)$$


Calculus fact: for this $Q(t)$,

$$I(t) = -\omega Q_{PEAK} \sin(\omega t)$$

$$\text{where } \omega = \frac{1}{\sqrt{LC}} = 2\pi f \rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

$$(\omega = \text{rad} / \text{s})$$

$$(f = 1 / \text{s} = \text{Hz})$$

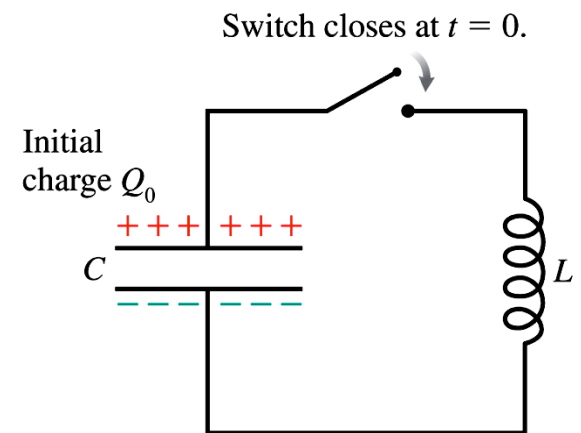

Oscillation frequency depends only on L and C
This is called the resonant frequency for the LC combination

Example:

An AM Radio tuning circuit

You have a 10mH inductor. What capacitor do you need with it to make **resonant circuit** with a frequency of 920 kHz? (This frequency is near the center of the AM radio band.)

$$\omega = 2\pi f = 2\pi(9.20 \times 10^5 \text{ s}^{-1}) = 5.78 \times 10^6 \text{ s}^{-1}$$

$$C = \frac{1}{\omega^2 L} = \frac{1}{(5.78 \times 10^6 \text{ s}^{-1})^2 (1.0 \times 10^{-2} \text{ H})} = 3.0 \times 10^{-11} \text{ F} = 30 \text{ pF}$$

Such circuits were used to tune in on desired stations in old radios: now tuners are built into complex microchips (integrated circuits) for radio receivers

The Series RLC Circuit

Now add a **resistor** in series with the inductor and capacitor.


The same current i passes through all of the components.

Fact: The C and L reactances create currents with $\pm 90^\circ$ phase shifts, so their contributions end up **180° out of phase** - tending to **cancel** each other. So the net reactance is $X = (X_L - X_C)$

$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

$$\sqrt{R^2 + (X_L - X_C)^2} = Z \quad Z = \text{"Impedance"} : \text{resistance and/or reactance}$$
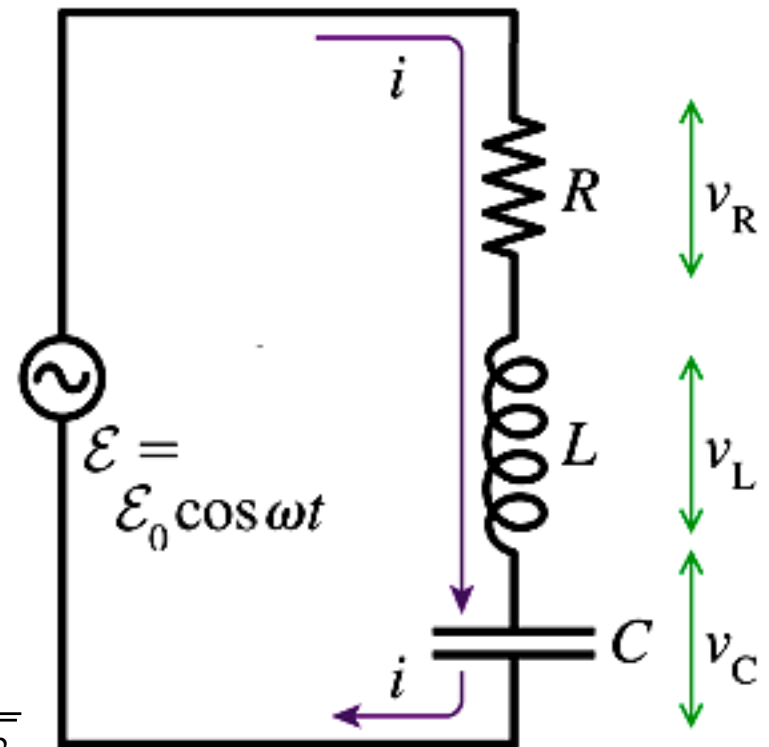
$$\mathcal{E}_0^2 = V_R^2 + (V_L - V_C)^2 = [R^2 + (X_L - X_C)^2] I^2$$



Impedance and resonance for RLC

We define the *impedance* Z of the circuit as:

$$\begin{aligned} Z &\equiv \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{R^2 + (\omega L - 1/\omega C)^2} \end{aligned}$$

Then $I = \mathcal{E} / Z$ (Peak, or RMS - here we mean peak values)

If circuit includes no C or L , then Z is just the resistance.

If frequency f is just such that $X_L = X_C$, we get *resonance*: *minimum possible Z* .

Then the circuit “looks like” only the resistor. Current is *maximum*.

Notice: if there *are* reactances in addition to R , they *do not contribute to RMS power dissipation* - *but* the circuit has to handle the reactive currents they produce (eg, wire sizes may need to be larger)

Series RLC Resonance


$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} = \frac{\mathcal{E}_0}{Z(\omega)}$$

The current I will be a maximum when $\omega L = 1/\omega C$.
This defines the **resonant frequency** ω_0 :

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Note (“cultural comment, not on test”):
Resonance is an important phenomenon in physics! (Example: Tacoma Narrows Bridge*)
Off-resonance, the current is given by
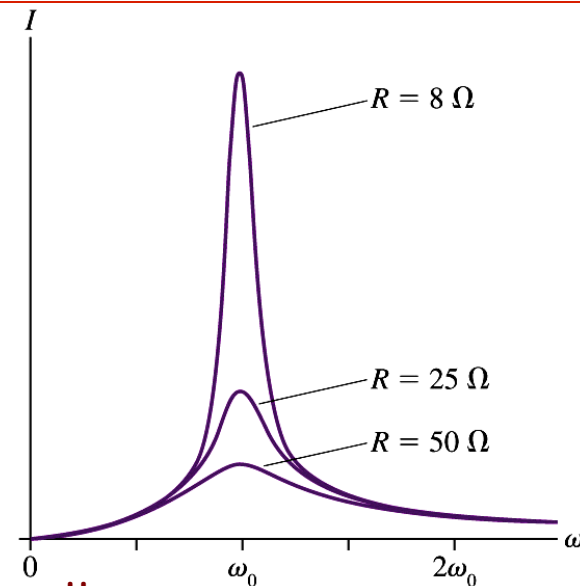
$$I = \frac{E_0}{\sqrt{R^2 + (L\omega)^2 \left[1 - \left(\frac{\omega_0}{\omega} \right)^2 \right]^2}}$$



The resonance is **sharper** if the resistance is smaller.
(analogy: mass + spring *with friction*: greater friction diminishes the amplitude of motion rapidly.)

quiz

- Which of the following is **TRUE** when a circuit with R , L , C in series is at its **resonant frequency**?
 - A. Net impedance = 0
 - B. Capacitive reactance = Inductive reactance**
 - C. EMF source "sees" only reactance, not R
 - D. The capacitor explodes
 - E. None of the above

