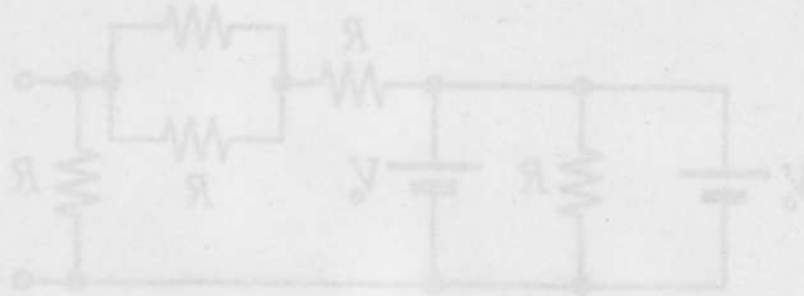


Physics 334, Winter Quarter 2012, Examination #1

Name SOLUTIONS V1.0

- 1 /25
 2 /25
 3 /25
 4 /25



TOTAL /100

Exam notes: The exam is closed-book. You may use a calculator, but not smart phones, iPads or laptops. You may not use your own equation sheet. Check that you have a total of 5 pages, including this page. You can make reasonable assumptions based on standard component tolerances of 5%, which may save you some time. You may use scratch paper or the back of the exam, but that won't be graded. Sloppy or disorganized work may be downgraded. Answers without showing work may be downgraded.

Possibly useful information and equations:

Ohm's Law: $V = IR$ Generalized Ohm's Law: $V = IZ$

Thévenin-equivalent circuits, conceptually (voltage-source and series resistor):

$V_{th} = V_{out}$ (open-circuit) and $R_{th} = V_{th}/I_{sc}$ (current through short-circuit)

Norton-equivalent circuits, conceptually (current source and parallel resistor):

$I_n = I_{out}$ (short circuit) and $R_n = V_{oc}$ (voltage open-circuit)/ I_n

Impedance/reactance equations:


Resistor: $Z=R$ Capacitor: $Z = -i/(\omega C)$ Inductor: $Z = i\omega L$

Other equations: $\omega = 2\pi f$ $e^{ia} = \cos a + i \sin a$ Power(t) = V(t) I(t)

For sine & cosine: $V_{rms} = V_{peak}/\sqrt{2}$ $\omega(3db) = \text{is } 1/2 \text{ power angular frequency (or } 1/\sqrt{2} \text{ voltage)}$

Capacitors: $Q = C V$ $I = C (dV/dt)$

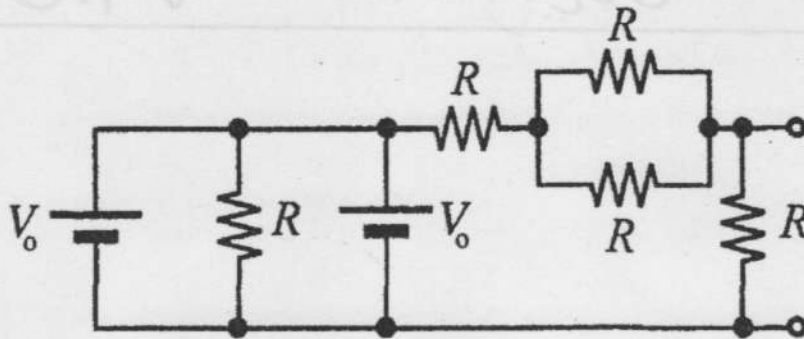
1. (25 points total) Thévenin and Norton equivalent circuits.
 Consider the circuit shown below, consisting of two identical and ideal voltage sources and five identical resistors.




a. (4 points) In 10 words or less, what is meant by "ideal" in "ideal voltage sources"?

THE VOLTAGE ACROSS THE DEVICE IS CONSTANT REGARDLESS OF CURRENT.

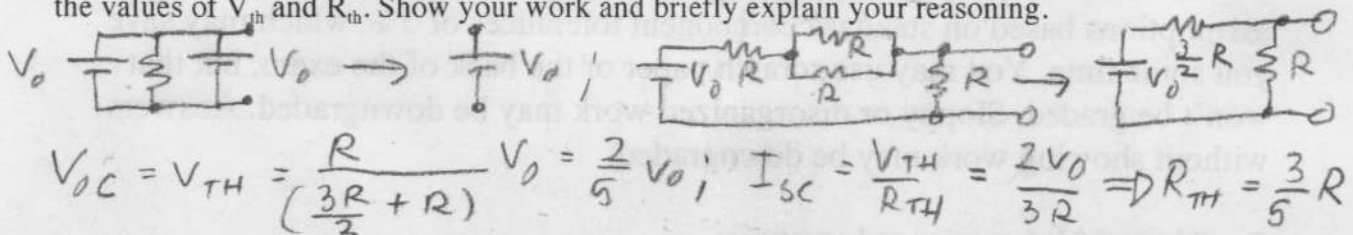
b. (7 points) Neatly and clearly sketch below the Thévenin equivalent circuit and determine the values of V_{th} and R_{th} . Show your work and briefly explain your reasoning.



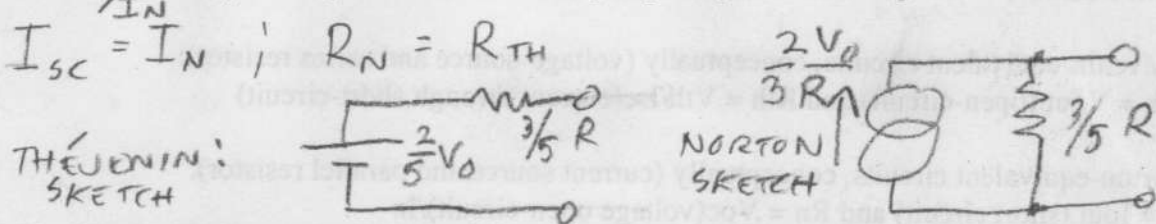
c. (7 points) Neatly and clearly sketch below the Norton equivalent circuit and determine the values of V_N and R_N . Show your work and briefly explain your reasoning.



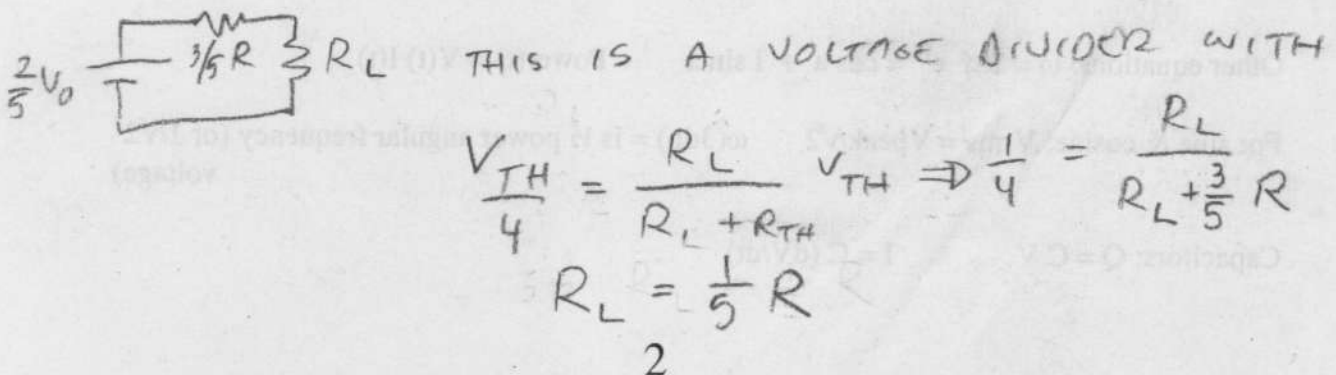d. (7 points) An unknown resistor load is connected across the output and a voltage $V_{th}/4$ is measured across the load. What is the load resistance expressed in terms of R ? Show your work and briefly explain your reasoning. USING THÉVENIN!



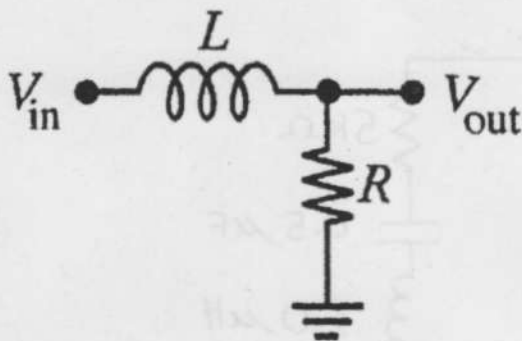2. (25 points total) Filters. Consider the circuit shown below. Assume $L = 15 \text{ mH}$ and $R = 120 \Omega$. Also assume the circuit is driven by an AC voltage source with RMS voltage $V_{in,RMS} = 10 \text{ V}$.



a. (4 points) Does this circuit behave like a high-pass, low-pass, band-pass or notch filter? Briefly explain your reasoning.

As $\omega \rightarrow 0$, $Z_L = i\omega L \rightarrow 0$ AND ALL V_{in} IS ACROSS R ; $V_{out} \approx V_{in}$
 As $\omega \rightarrow \infty$, $Z_L \rightarrow \infty$ AND NO V_{in} ACROSS R ; $V_{out} \rightarrow 0$

b. (7 points) Write an expression (or expressions) in terms of the given variables for the "3dB" angular frequency ω_{3dB} . If there's more than one value of ω_{3dB} , identify all such values.

Show your work and briefly explain. $Z = i\omega L + R$; $I = V_{in} / Z$


$$V_{out} = IR = R V_{in} / Z \quad |V_{out}|^2 / |V_{in}|^2 = R^2 / |Z|^2 = \frac{R^2}{R^2 + \omega^2 L^2}$$

For $\frac{|V_{out}|^2}{|V_{in}|^2} = \frac{1}{2}$, $\frac{R^2}{R^2 + \omega_{3dB}^2 L^2} = \frac{1}{2}$ $\omega_{3dB} = \frac{R}{L}$

c. (7 points) Calculate the value(s) of f_{3dB} for this particular circuit. Show your work.

$$f_{3dB} = \frac{\omega_{3dB}}{2\pi} = \frac{R}{2\pi L} = \frac{120 \Omega}{2\pi \cdot 15 \times 10^{-3} \text{ H}} = 1.3 \text{ kHz}$$

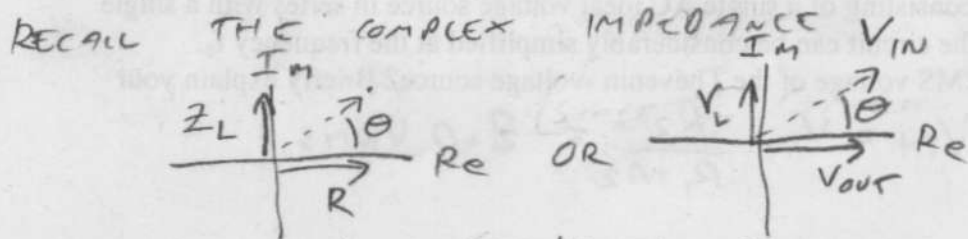d. (7 points) Suppose the input frequency is 950 Hz. Determine the phase difference in degrees between V_{out} and V_{in} . If the two quantities are not in phase, be sure to state clearly whether V_{out} lags or leads V_{in} . Show your work and briefly explain your reasoning.




$$\cos \theta = \frac{|V_{out}|}{|V_{in}|} = \frac{|Z_{out}|}{|Z_{in}|} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$

$$= \frac{120 \Omega}{\sqrt{(120 \Omega)^2 + (2\pi \cdot 950 \text{ Hz})^2 (15 \text{ mH})^2}} = 0.80$$

$\theta \approx 40^\circ$ AND V_{out} LAGS V_{in}

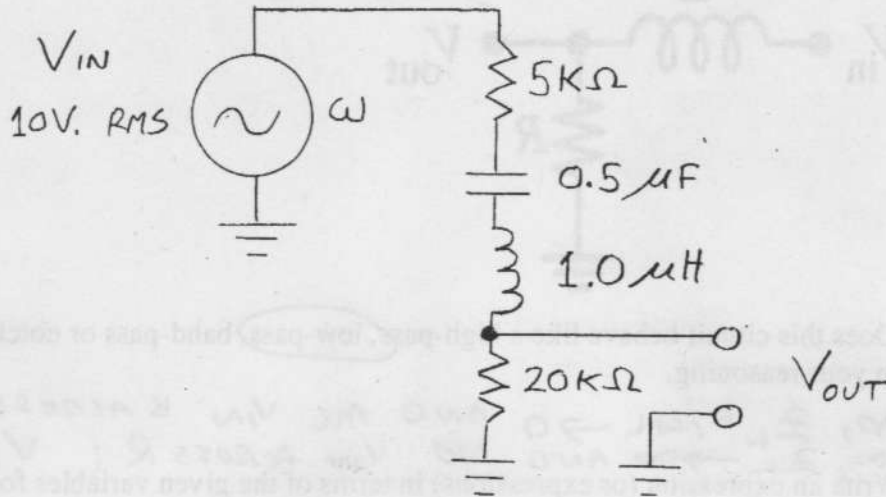3. (25 points) Thévenin-equivalent circuit and resonance.
 Consider the circuit shown below. Notice this circuit is driven by an AC voltage source with RMS voltage V_{in} (RMS) = 10 V at angular frequency ω .



a. (4 points) At what source-frequency f_0 is the RMS current supplied by the voltage source at a maximum? Briefly explain your reasoning.

$f_0 = \frac{1}{2\pi\sqrt{LC}} \approx 230\text{kHz}$
 AT THE RESONANT FREQUENCY THE SERIES L & C HAVE THEIR LOWEST IMPEDANCE AND HENCE HIGHEST CURRENT.

b. (7 points) What's the value of the RMS current supplied by the voltage-source at frequency f_0 ? Briefly explain your reasoning.

AT f_0 $Z = 5\text{k}\Omega + 20\text{k}\Omega$; AT RESONANCE THE SERIES L & C CONTRIBUTE NO IMPEDANCE
 $I = 25\text{k}\Omega / 10\text{V} = 0.40\text{mA RMS}$

c. (7 points) What's the RMS output voltage at frequency f_0 ? Briefly explain your reasoning.

OUTPUT IS VOLTAGE ACROSS $20\text{k}\Omega$ RESISTOR
 $V_{OUT} = 20\text{k}\Omega \cdot 0.40\text{mA} = 8.0\text{V RMS}$

d. (7 points) Suppose you replace this circuit, operating at frequency f_0 , by a Thévenin-equivalent circuit consisting of a single AC ideal voltage source in series with a single impedance. Hint: the circuit can be considerably simplified at the frequency f_0 .

i. What's the RMS voltage of the Thévenin -voltage source? Briefly explain your reasoning.


$$V_{TH} = V_{IN} \frac{R_2}{R_1 + R_2} = 8.0\text{V RMS}$$

ii. What's the value of the Thévenin-equivalent series impedance? Briefly explain your reasoning.

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{5\text{k}\Omega \cdot 20\text{k}\Omega}{5\text{k}\Omega + 20\text{k}\Omega} = 4\text{k}\Omega$$

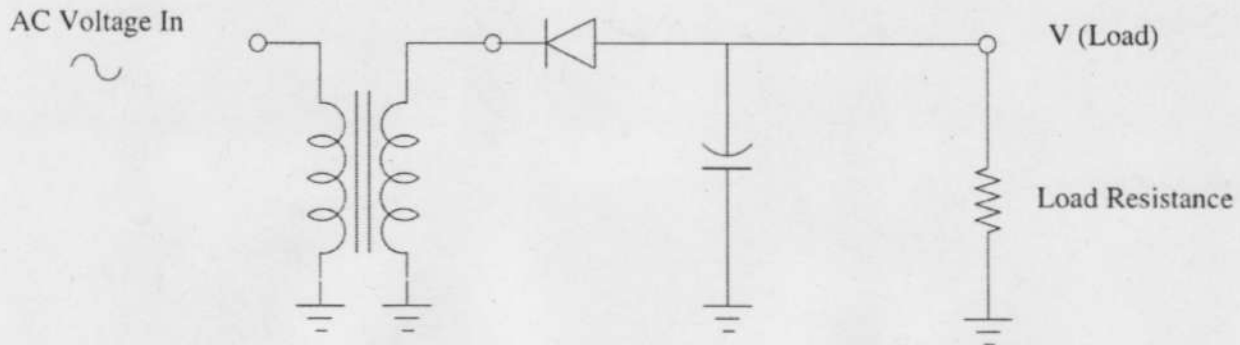4. (25 points) Diodes and power supplies.

Consider the power-supply circuit shown below. The output is taken at the point labeled V(Load). Assume for now the Load Resistance is very very large.



a. (4 points) With the assumptions above, is this design an AC- or DC-voltage supply?

IT'S A CLASSIC DC SUPPLY AS SEEN IN LAB.

b. (6 points) If it's an AC supply, carefully and neatly sketch the output waveform. If it's a DC supply, is this a positive, negative, or 0 volt (ground) supply?

NEGATIVE: THE DIODE IS REVERSED FROM WHAT YOU SAW IN LAB.

c. (7 points) Assume the AC Voltage In applied to the transformer primary is 120 V AC(RMS), the standard US line voltage. Assuming further that the transformer turns-ratio is 12:1 (meaning the transformer's secondary voltage is $\times 12$ smaller than the primary input voltage). What V(Load) output do you expect for very large load resistance: either carefully and neatly sketch the output waveform or otherwise explain as appropriate.

$$V_{\text{TRANS}} = 10 \text{ V (RMS)}; V_{\text{TRANS}} (\text{PEAK}) = \sqrt{2} 10 \text{ V}$$

ACCOUNTING FOR THE DIODE DROP (SAY, 0.6 V);

$$V(\text{LOAD}) \approx -\sqrt{2} 10 \text{ V} + 0.6 \text{ V} \approx -13.4 \text{ V}$$

d. (8 points) Now assume a finite load resistance of 10 k Ω . What value of capacitance should you choose so that the output voltage droops less than 1 V from the maximum value? You can assume the frequency of the AC Voltage In is 60 Hz.

$$C = \frac{I_{\text{PEAK}} \Delta t}{\Delta V}$$

$$= \frac{1.3 \text{ mA} (16 \text{ ms})}{1 \text{ V}}$$

$$\approx 21 \mu\text{F MINIMUM}$$

$$\Delta t = \frac{1}{60 \text{ Hz}} \left(\frac{1}{2} \text{ WAVE RECTIFIER} \right)$$

$$\approx 16 \text{ ms}$$

$$I_{\text{PEAK}} = \frac{13.4 \text{ V}}{10 \text{ k}\Omega} \approx 1.3 \text{ mA}$$