

PHYS 334

WINTER QUARTER

2012


HOMEWORK 1 SOLUTIONS

VER 1.0.


I. (MODIFIED EXERCISE 1.5). CAPACITORS & INDUCTORS STORE ENERGY. RAPIDLY RELEASING THAT ENERGY PROVIDES LARGE BURSTS OF POWER

FOR EXAMPLE:


STEP 1: CHARGE PARALLEL CAPACITORS

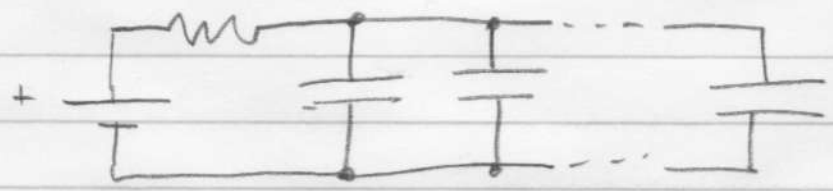

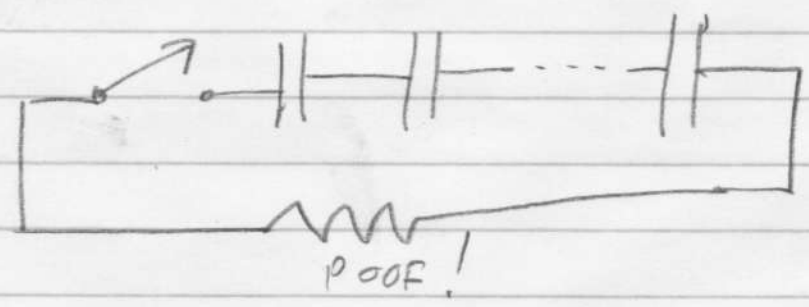STEP 2: REARRANGE (OR SWITCH) THOSE CHARGED CAPACITORS INTO SERIES, THEREBY FRYING THE RESISTOR.



2. (a) "OUTPUT LOADING"

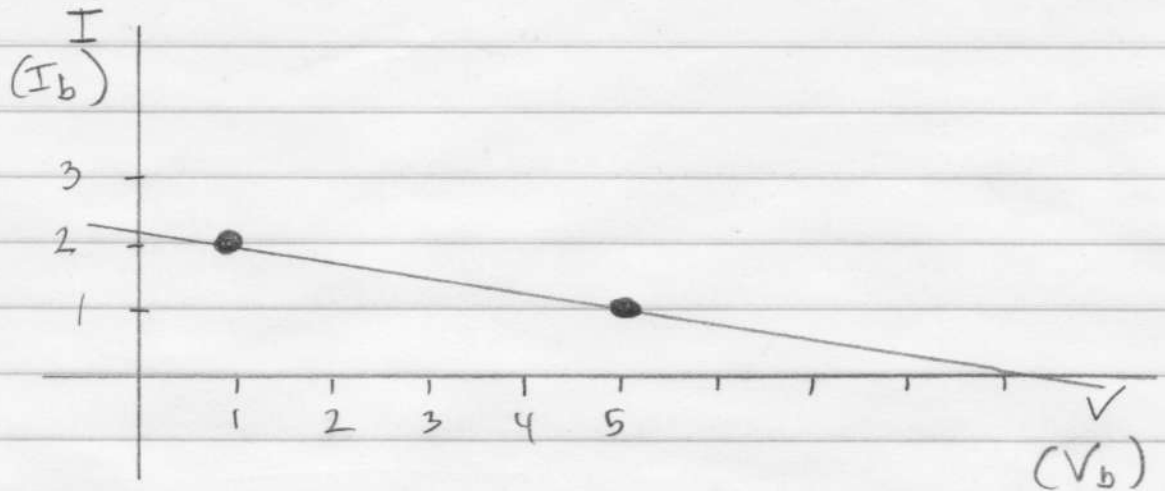

(b) THE VOLTAGE INTERCEPT IS V_{TH} : $9V_b$,
 THE SHORT-CIRCUIT CURRENT IS $\approx 2.25 I_b$,
 THE THÉVENIN RESISTANCE IS V_{TH}/I_{SC}
 $\approx \frac{9}{2.25} \frac{V_b}{I_b}$

THE NORTON RESISTANCE IS THE
 THÉVENIN RESISTANCE

$$(3) a. \quad V_C = 12V - 2mA \cdot 1k\Omega = 10V$$

$$V_E = (2mA + 20\mu A) \times 1k\Omega \approx 2.0V.$$

b. SINCE $20\mu A \ll I_d$, THE VOLTAGE AT B IS THAT OF THE UNLOADED DIVIDER-CHAIN OUTPUT, HENCE $V_B = 12V \frac{R_2}{R_1 + R_2}$. ALSO $V_B = 2V + 0.6V$, HENCE

$$(1) \quad 12V \frac{R_2}{R_1 + R_2} = 2.6V$$

RECALL THAT $V_B - V_E = 0.6V$, HENCE $R_{BE} = 0$. WE CAN THEREFORE USE OHM'S LAW TO FIND THE CURRENT INTO B:

$$(2) \quad 20\mu A = \frac{12V \frac{R_2}{R_1 + R_2} - 0.6V}{\frac{R_1 R_2}{R_1 + R_2} + 1k\Omega}$$

WHEREAS $\frac{R_1 R_2}{R_1 + R_2}$ IS THE THÉVENIN RESISTANCE OF THE DIVIDER CHAIN.

SOLVING FOR R_1 & R_2 :

$$R_1 \approx 450k\Omega,$$

$$R_2 \approx 125k\Omega$$