

# Physics 334, Winter Quarter 2012

## Homework Assignment 1

**Due Tuesday January 10 in class or in my mail box before the end of class.**

1. Exercise 1.5 in the textbook with this twist: If the circuit is allowed to include capacitors and inductors, find a counter-example circuit to the problem premise and explain your reasoning.
2. You are given a “black box” with two terminals and proceed to measure its “I-V” curve, finding the following two points on the curve:  $(2I_b, V_b)$  and  $(I_b, 5V_b)$ . (a) Accurately sketch the “I-V” curve. (b) From this curve, find the Thévenin voltage and resistance  $V_{Th}$  and  $R_{Th}$ , as well as the Norton current and resistance  $I_N$  and  $R_N$ .
3. A “black box” with 3 terminals labeled E, B and C is shown in the circuit below. Assume terminal B is magically always 0.6 V more positive than terminal E, and  $I_d$  is very large compared to the current flowing into terminal B. (FYI, this black box is an NPN bipolar transistor.) (a) Find  $V_C$  and  $V_E$ . (easy to do) (b) Find  $R_1$  and  $R_2$ . Hints: “Assume terminal B is always 0.6 V more positive than terminal E, ...” implies what “dynamic” resistance between terminals B and E? And why does it help that  $I_d$  is relatively large?

