
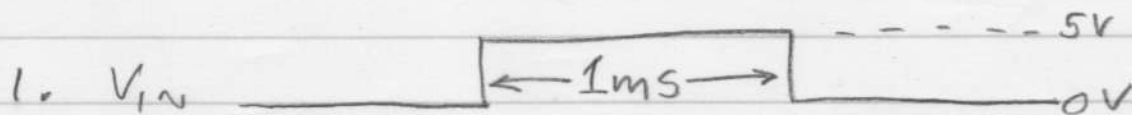


PHYS 334 WINTER QUARTER  
HOMEWORK 3 SOLUTIONS


2012  
V. 1.0

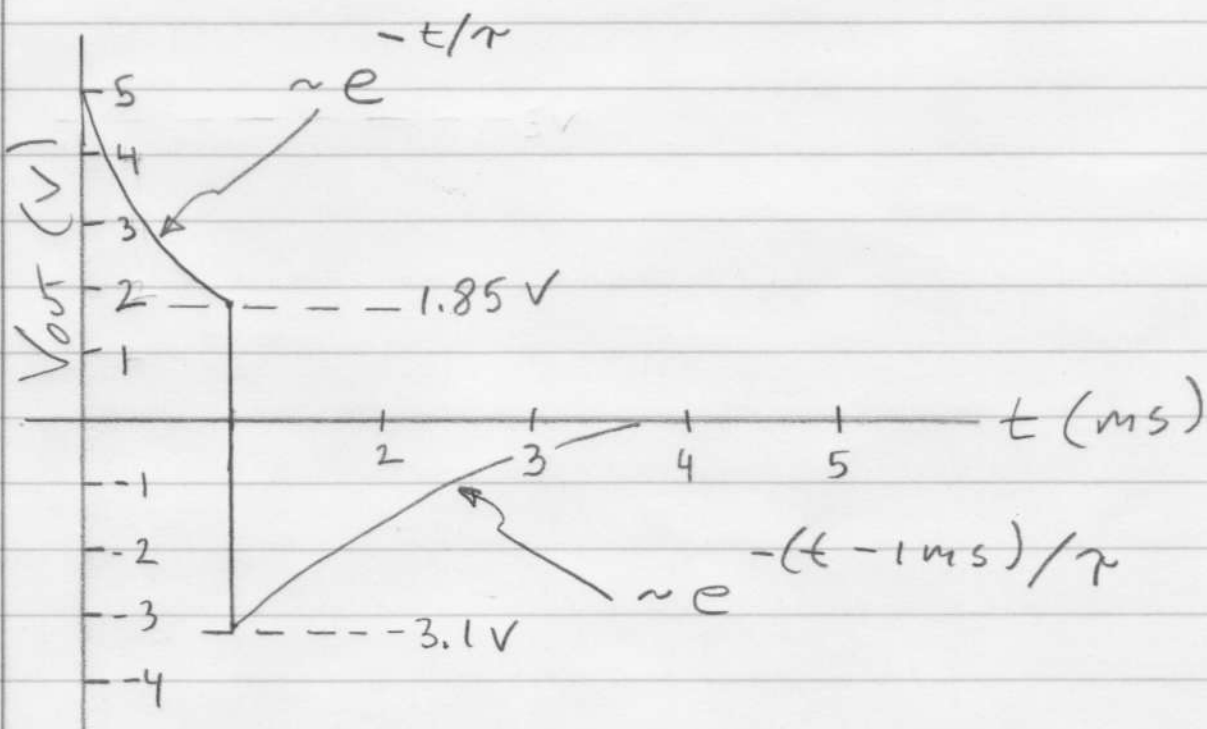

$$T = RC = 1000 \Omega \times 1 \text{ mF} = 1 \text{ ms.}$$



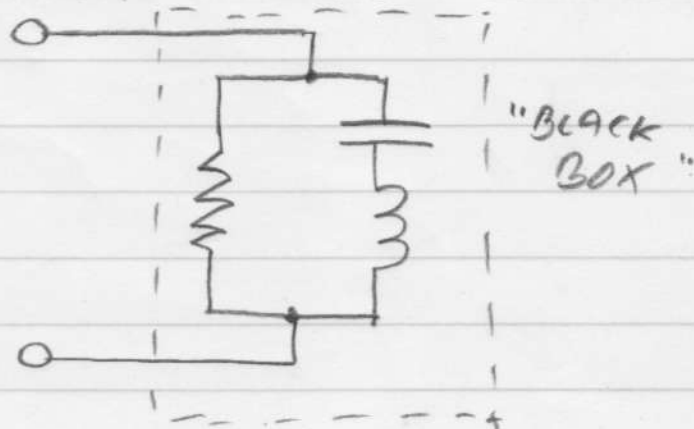2. THE ONLY POSSIBLE CONFIGURATION  
SATISFYING CONSTRAINT 1 & 3 IS



THE IMPEDANCE "LOOKING INTO" THE TWO TERMINALS IS

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{i\omega L - i/\omega C}$$

$$= \frac{1}{R} + \frac{1}{i\omega L (1 - \omega_0^2/\omega^2)} \quad ; \quad \omega_0^2 = \frac{1}{LC}$$

$$\frac{1}{L} = \sqrt{\frac{1}{|Z|^2} - \frac{1}{R^2}} \omega \left\{ 1 - \frac{\omega_0^2}{\omega^2} \right\}$$

AT  $\omega (60\text{Hz}) \equiv \omega_{60}$ ,  $V_{\text{RMS}} = 1\text{V}$

AND  $I_{\text{RMS}} = 1/100\text{A}$

HENCE  $|Z| = V_{\text{RMS}}/I_{\text{RMS}} = 100\Omega$  (AT  $\omega_{60}$ )

$= \frac{1}{10} R$  ( $R = 1000\Omega$  FROM  
CONSTRAINT 1)

NOTICE  $\omega_{60}/\omega_0 = 3/50$

HENCE  $L \approx \frac{\omega/\omega_0^2 |Z|}{(1000 \cdot 2\pi/\text{SEC})^2} \times 100\Omega$

$$= \frac{60 \cdot 2\pi/\text{SEC}}{(1000 \cdot 2\pi/\text{SEC})^2} \times 100\Omega$$

$$\approx 1\text{mH}$$

$$C = \frac{1}{L\omega_0^2} = \frac{1}{\omega|Z|} = \frac{1}{60 \cdot \frac{2\pi}{5\text{EC}} \cdot 100\Omega}$$

$$\approx 30 \text{ mF}$$

3.  $Z = 1000\Omega (1+i) = 1000\Omega\sqrt{2} e^{i\pi/4}$

$$V(t) = V_0 e^{i(\omega t + \theta)}$$

$\theta$  IS THE ARBITRARY PHASE

$$I(t) = V(t)/Z = \frac{V_0 e^{i(\omega t + \theta)}}{1000\Omega\sqrt{2} e^{i\pi/4}}$$

$$\langle P \rangle = \frac{1}{2} \text{Re } V I^*$$

$$= \frac{1}{2} \text{Re } V_0 e^{i(\omega t + \theta)} \frac{V_0 e^{-i(\omega t + \theta)}}{1000\Omega\sqrt{2} e^{-i\pi/4}}$$

$$= \frac{1}{2} \frac{|V_0|^2}{1000R\sqrt{2}} \text{Re } e^{i\pi/4}$$

$$= \frac{1}{2} \frac{|V_0|^2}{1000\Omega R\sqrt{2}} \frac{\sqrt{2}}{2}$$

$$= \frac{1}{4} \frac{|10\text{V}|^2}{1000\Omega} = 25 \text{ mW}$$