

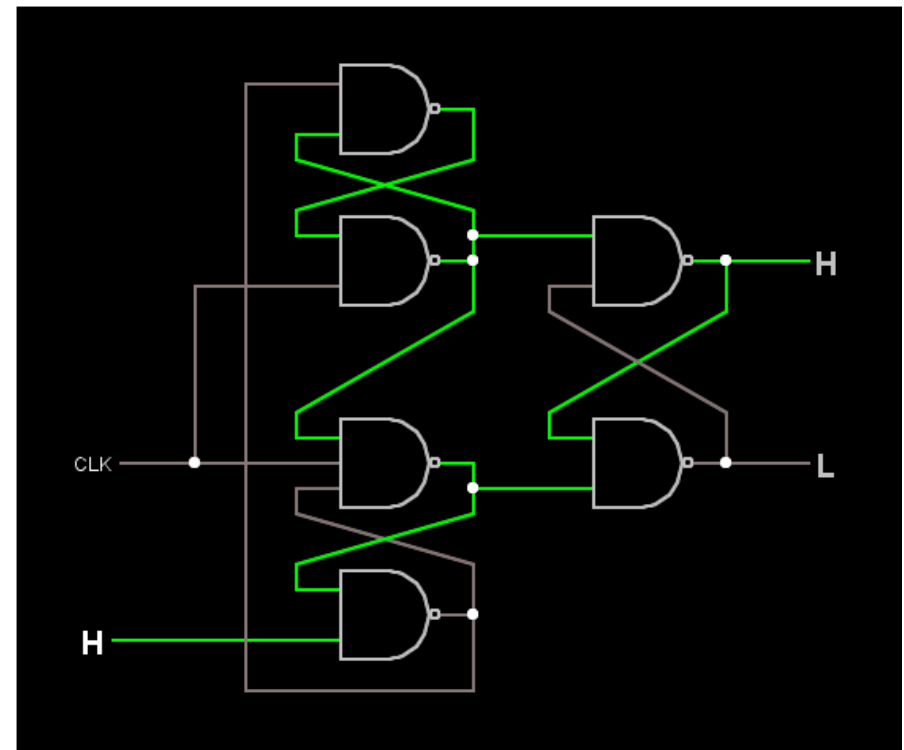
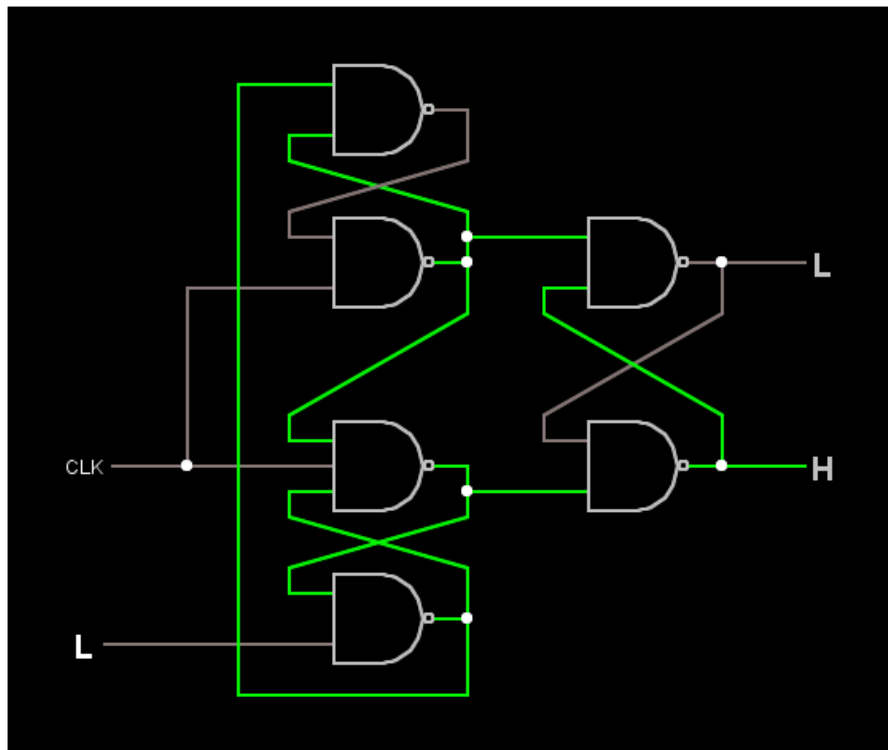


Edge-triggered flip-flop

 

For both H and L inputs **and** CLK=LOW, right latch is kept in memory state


CLK → HI allows data to pass

 

Even if data input (D) changes state after CLK goes HI, it does not propagate.

COMPUTER FIRST STEPS


REGISTERS + GATES

 

BASIC IDEA OF DIGITAL
COMPUTER !!

FUNDAMENTAL NOTION: "STATE MACHINE"

SILLY EXAMPLE (FROM M&H)

 

STATES = CIRCLES


CAUSES = ARROWS

EACH STATE REMAINS
UNTIL CLOCK
(END OF TERM)
OR OTHER INTERRUPT
(INSULT TEACHER)

Figure 8.61. State diagram: going to school.

STATE DIAGRAM AS DESIGN TOOL

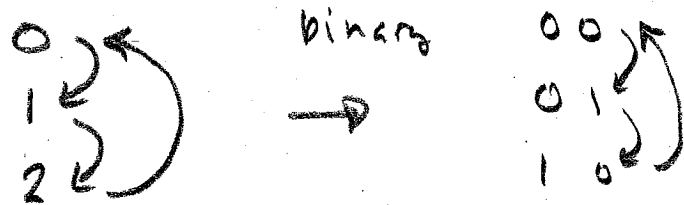
EXAMPLE: "DIVIDE-BY-3" SYNCHRONOUS COUNTER.



NEED 2 BITS


BUT 2 bits $\Rightarrow$ 4 STATES

LET 11 STATE GO TO
10 STATE

 

STATE DIAGRAM FOR $\div 3$
COUNTER.


÷ 3 CONT.

 

COMBINATIONAL PROBLEM:

GIVEN POSSIBLE OUTPUTS
WANT GATES TO PRESENT
NEXT STATE TO INPUTS

Q_s are INPUTS / D_s are OUTPUTS

 

Q_1	Q_0	D_1	D_0
0	0	0	1
0	1	1	0
1	0	0	0
1	1	1	0

÷ 3 CONT

K-MAPS (FOR PRACTICE)

D_0

$Q_1 \backslash Q_0$	0	1
0	1	0
1	0	0

D_1

$Q_1 \backslash Q_0$	0	1
0	0	1
1	0	1


Q_0

so $D_0 = \overline{Q_0} \overline{Q_1}$ (NOR)
 $= \overline{(Q_0 + Q_1)}$

$D_1 = Q_0$

ONLY NEED
ONE GATE

EXERCISE: DRAW
TIMING DIAGRAM

 

A BIT MORE COMPLICATED? J-K FLOP FROM D-FLOP.

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\bar{Q}_n$


EXPAND
→ TRUTH →
TABLE

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


$Q_n \backslash J, K$	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$\bar{Q}_n \cdot J$ (points to the 1s in the $Q_n=0$ row)
 $Q_n \cdot \bar{K}$ (points to the 1s in the $Q_n=1$ row)
 
$$Q_{n+1} = \bar{Q}_n \cdot J + Q_n \cdot \bar{K}$$




 NOTICE: BECAUSE D-FLOPS HAVE BOTH Q , $\bar{Q}$ OUTPUTS, WE CAN USE TO ADVANTAGE



EXERCISE: MAKE WITH NANDS ONLY

HERE'S THE SAME THING USING
4-INPUT MUX

 

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

COUNTER CHIPS (NO ONE BUILDS COUNTERS FROM SCRATCH)

BCD - "BINARY-CODED DECIMAL"


(ONLY COMPUTER GEEKS READ HEX,
REST OF US READ BASE 10)

BCD → EACH DIGIT IS 0 - 9

0000 ... 1001 → CARRY

IDEA :

"7-SEGMENT"
DISPLAYS →

 


LS 390 (BCD) vs LS 393 (HEX)

CLOCK $\rightarrow$

SN54/74LS393 LOGIC DIAGRAM (one half shown)

RESET LINE $\rightarrow$

 


J, k in toggle (HI) STATE (LS Floats HI)

'393 HEX COUNTER - RIPPLE OR SYNCHRONOUS?

2 CLOCKS

SN54/74LS390 LOGIC DIAGRAM (one half shown)

For $\div 10$

 

J = 0, k = 1
 $\Rightarrow Q_3 = 0$
 $\Rightarrow$ CP1 EN

'390 BCD COUNTER: $\div 2 + \div 5$

Q_3	Q_2	Q_1
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

COUNTER CHIPS, CONTINUED

FEATURES

- SIZE - 4, 8, 12, 16 $\rightarrow$ 24 BITS
(SOME BITS INTERNAL)
- TYPE - RIPPLE OR SYNCHRONOUS
'390 '160


- UP/DOWN SELECTION?
'191, '193




- LOAD & CLEAR

LOAD - SETS COUNTER TO PREDEFINED
START VALUE

CLEAR - SETS COUNTER TO ZERO

 


COUNTERS DESIGNED TO EXPAND

 

← SYNCHRONOUS CLOCKING

$\overline{C_{in}}$ = ENABLE - when asserted (here LO)
ALLOWS CLOCK TO ADVANCE

 $\overline{C_{out}}$ = ASSERTED WHEN ALL BITS ARE 1
ABOUT TO ROLLOVER?



⇒ $\overline{C_{out}}$ ON

$\overline{C_{out}}$ OFF (NOW)

COUNTER RESET/CLEAR OPERATION

RESET or CLEAR CAN BE

- SYNCHRONOUS — CLEAR
IS ASSERTED, BUT ACTION WAITS
FOR CLOCK EDGE
- "JAM" (ASYNCH.) — CLEAR
HAPPENS IMMEDIATELY

SYNCH. TYPES


'163 (4 bit)
'264 (8 bit)

BOTH!
'569

JAM TYPES


'161 (4 bit)
'393 (8 bit)

EXAMPLE — DIVIDE BY 5

 

LOAD OPTION ALLOWS COUNTERS
TO START AT NUMBERS OTHER THAN
ZERO. (AGAIN, SYNCH & JAM TYPES)

EXAMPLE: MODULO-N COUNTER

 

COUNTER COUNTS
DOWN (T_0 asserted at 00_{16})

