

COUNTERS, CONTINUED

USE COUNTERS AS A DESIGN TOOL
TO MEASURE SOME QUANTITY

1. Make a counter
2. Add gates / Flips to start & stop
3. MAKE CIRCUITRY TO CONVERT
Quantity of interest into a pulse
4. USE COUNTER TO MEASURE
LENGTH OF PULSE

EXAMPLE - DIGITAL VOLT METER (M & H)

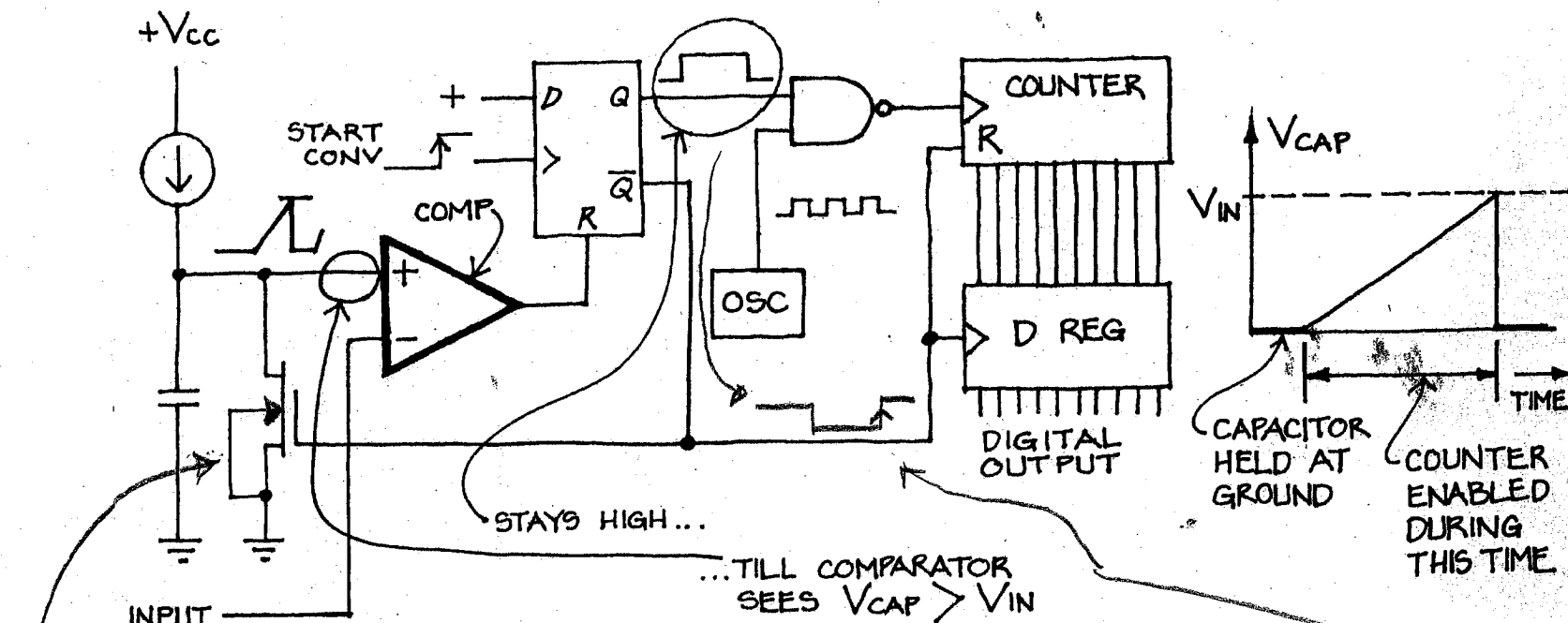


Figure N15.14: Example 1: measure period to measure voltage


MEASURED VOLTAGE GOES HERE

TRANSISTOR NORMALLY ON - SHORTS OUT CAPACITOR

$\bar{Q} \rightarrow \underline{LO}$ turns PBT OFF, VOLTAGE ON CAP RISES LINEARLY,

RISEING EDGE LATCHES COUNT AND RESETS COUNTER

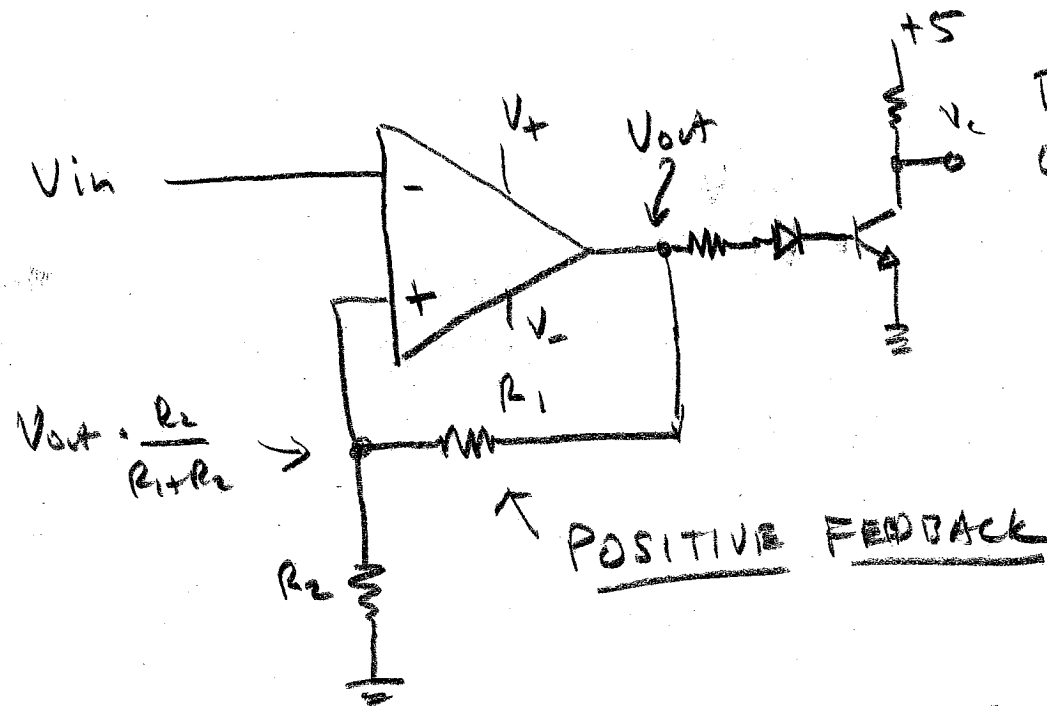NOTE : A COMPARATOR IS AN OP-AMP
DESIGNED TO HAVE A TWO-STATE OUTPUT,
ONLY DETERMINES IF $V_+ > V_-$ or $V_+ < V_-$



BECAUSE GAIN OF
OPAMP IS SO HIGH

$V_{out} = V_-$ IF

$$V_{in} > V_- = \frac{R_1}{R_1 + R_2}$$

TRANSISTOR OFF

$$\Rightarrow V_c = +5$$

WHEN $V_{in} < V_- = \frac{R_1}{R_1 + R_2}$

V_{out} SWINGS TO V_+

TURNING TRANSISTOR

ON, $V_c \rightarrow \approx 0$

NOTE THRESHOLDS DIFFER
GOING LOW \rightarrow HIGH, $V_+ = \frac{R_1}{R_1 + R_2}$

HIGH \rightarrow LOW $V_- = \frac{R_1}{R_1 + R_2}$

HYSTERESIS

SIMILAR CIRCUIT USED TO MEASURE
CAPACITANCE. RECALL 555 TIMER


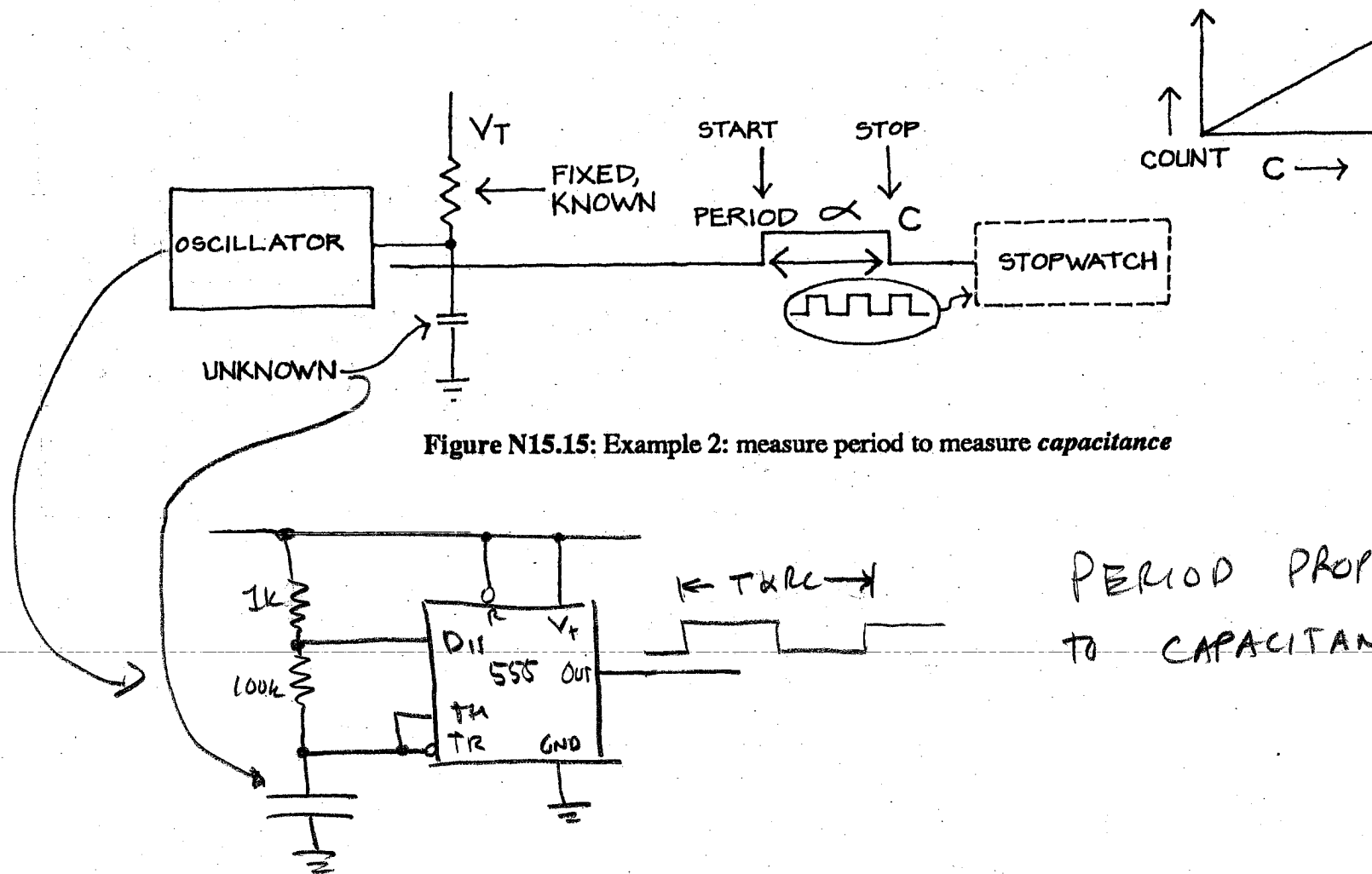


Figure N15.15: Example 2: measure period to measure *capacitance*

PERIOD PROPORTIONAL
TO CAPACITANCE



BASIC SEQUENCE OF COUNTING:

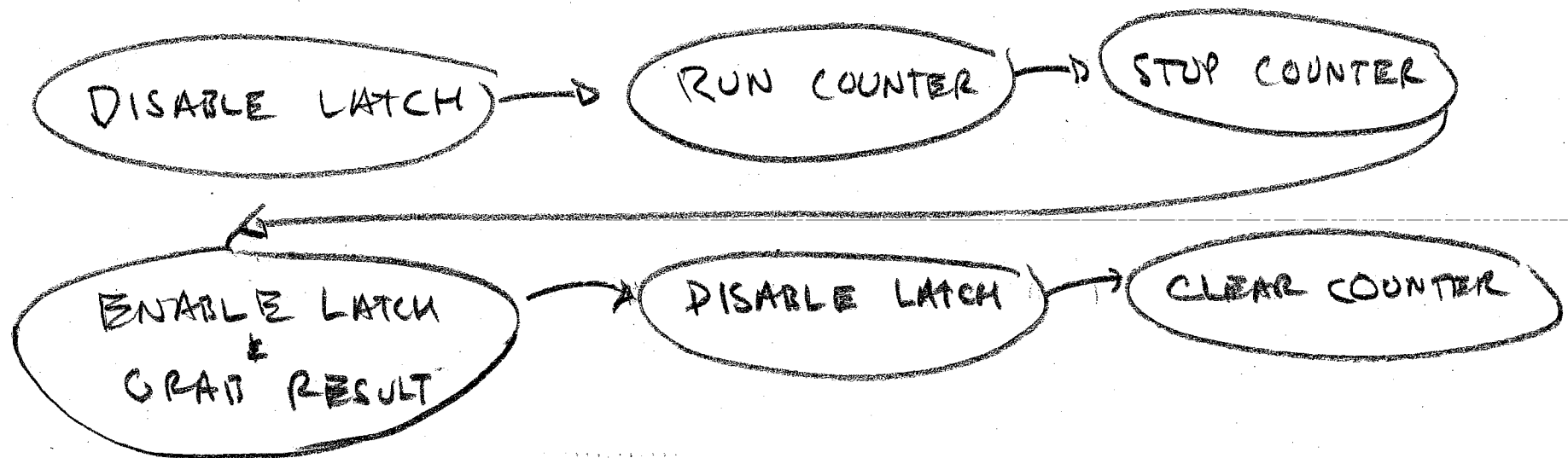

TIMING OF ENABLE PINS & CLOCK EDGES IS CRITICAL.

- PAY ATTENTION TO POS (F) or NEG (L) EDGE TRIGGERS
- PAY ATTENTION TO POSITIVE OR NEGATIVE ASSERTIONS
- PAY ATTENTION TO PROPAGATION DELAYS

EXAMPLE PROBLEM — PULSE SYNCHRONIZER

  

SAME PROBLEM - ANOTHER CONTEXT

$\div 13$ COUNTER

 


Figure X15.1: A poor way to convert natural binary counter to $+13$

 


Figure X15.2: Poor $+13$ design: false 14th state between 12 and 0

 


Figure X15.3: Synchronous $+13$ from $+16$ counter


 


Figure X15.4: Proper count modification: using synchronous Clear*

$\div 13$ COUNTS $\rightarrow 0, 1, 2, \dots, 12$

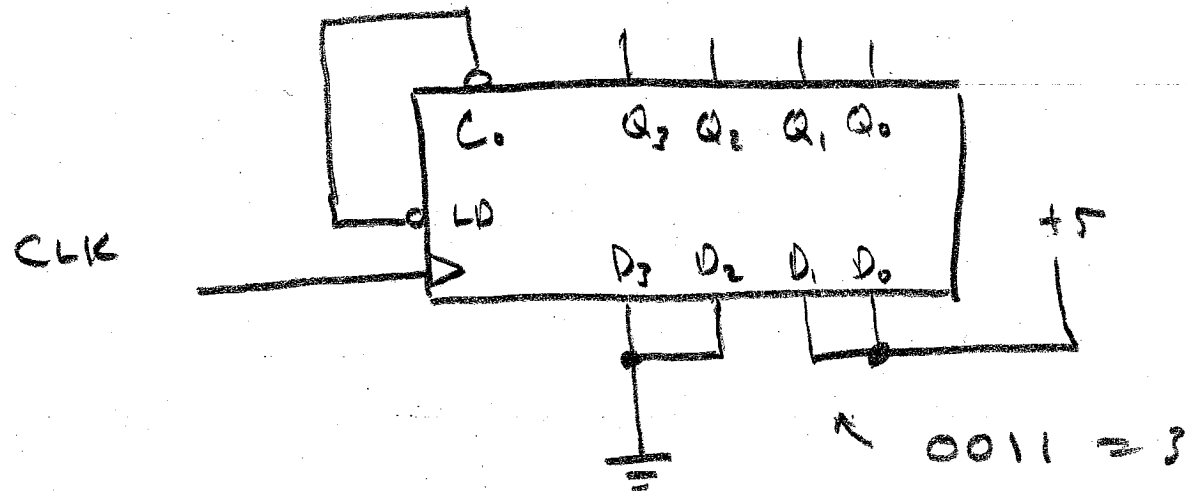ANOTHER WAY TO DO IT - USE SYNCHRONOUS
LOAD




This counts from 3, 4, ..., 15 } 13 states

- But
- Peculiar numbers (if you care)
 - could count Down (but reversed)


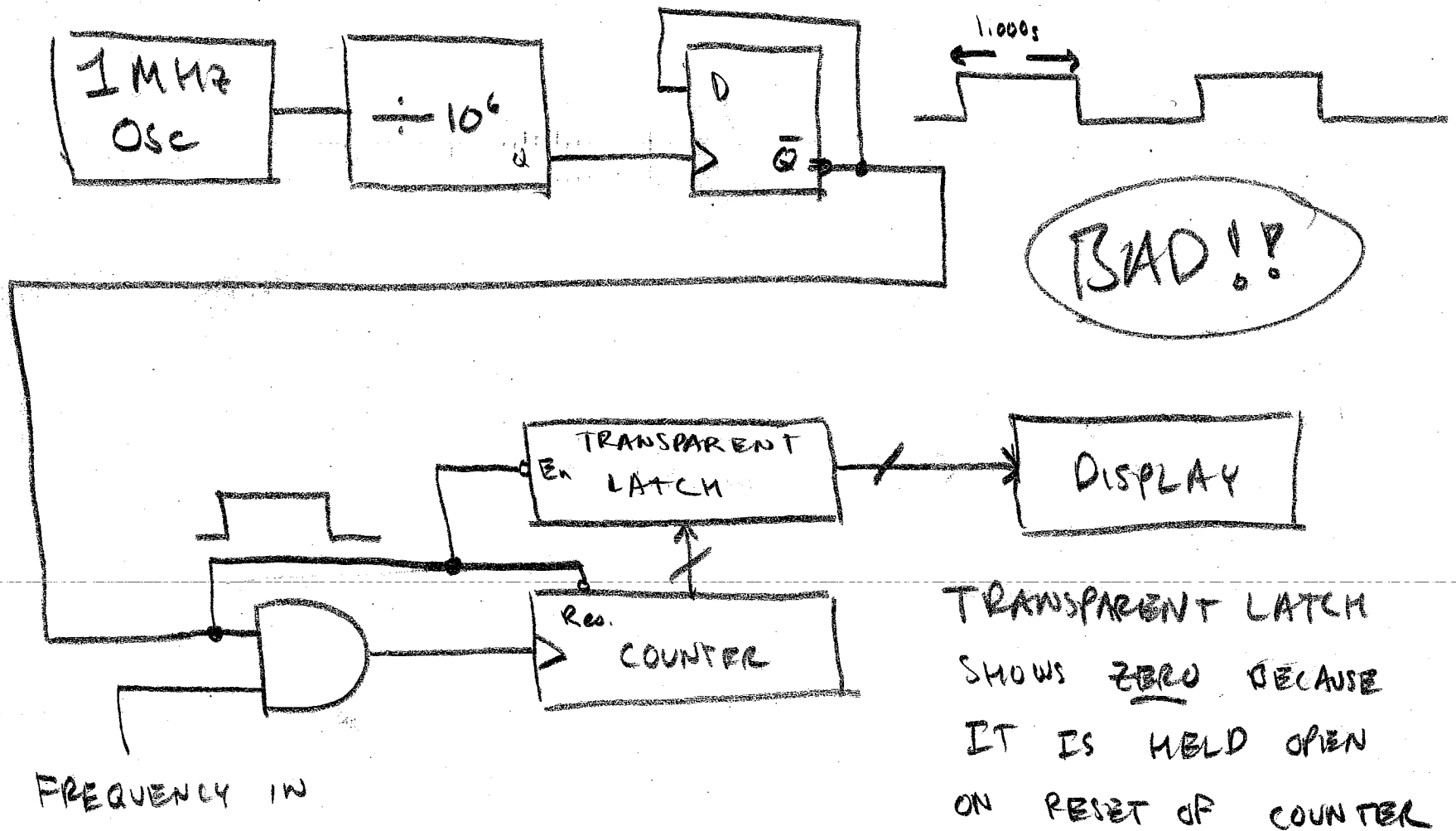
EXAMPLE, GOOD & BAD - FREQUENCY COUNTER

IDEA: FREQUENCY = CYCLES/SECOND.

TURN ON COUNTER FOR 1.000 seconds, count CYCLES



SOLUTION: USE EDGE TRIGGERED REGISTER

  

= CLOCK INPUT TO REGISTER

SLIGHT DELAY

IN RESET

ALLOWS EDGE



TRIGGERED REGISTER

TO GRAB COUNTS

TIMING TRICKINESS - COUNTER IS STILL
COUNTING WHEN REGISTER IS TRIGGERED.


THIS COULD VIOLATE SETUP TIMES OF
REGISTER & CAUSE BAD VALUE TO BE RECORDED

SOLUTION - STOP COUNTER FIRST!

  


A NEW CONCEPT: THE BUS

 
PROBLEM — NOT ENOUGH WIRES, OR,
YOU WANT TO HAVE AN INPUT
CHOOSE AMONG VARIOUS OUTPUTS,



ONE POSSIBILITY - OR GATES

 


WHY CAN'T THIS HAPPEN?

 

BRIEF DICRESSION . . .

NEVER DO THIS

 

SLIGHT PHASE DIFFERENCE OR VOLUME DIFFERENCE
CAUSES AMP A TO BECOME LOAD of AMP B

POWER AMPS HAVE LOW OUTPUT Z.


RESULT :

FRIED AMPLIFIERS


~~~~~

EXTRA OR GATE SOLVES PROBLEM, BUT  
IS CUMBERSOME.


SOLUTION: 3 STATE OUTPUTS

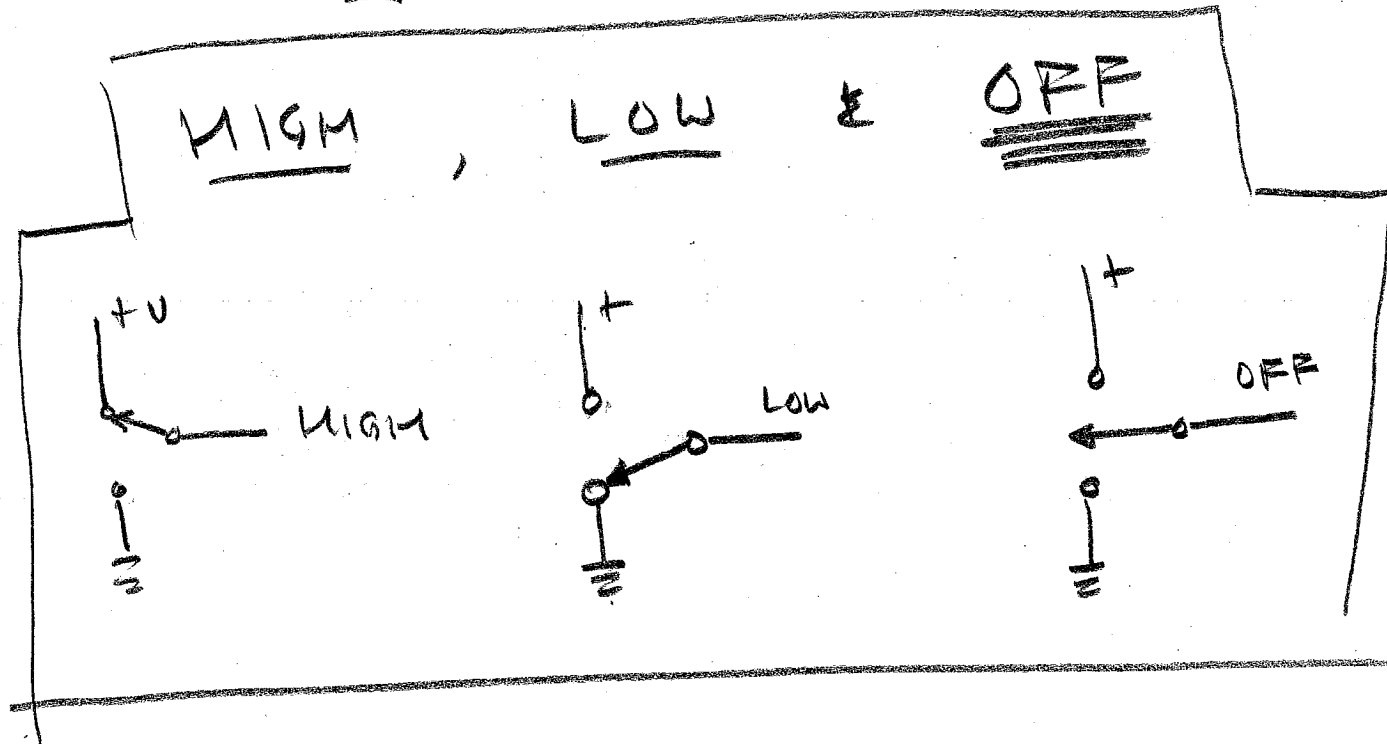

SYMBOL : 3-STATE BUFFER

 


### 3 - STATE OUTPUTS - HOW THEY WORK

 


- IF ENABLE IS LOW, BOTH NANDS ARE HIGH, BOTH MOSFETS ARE OFF
- IF ENABLE IS HIGH, MOSFET CORRESPONDING TO IN IS ON → OUTPUT EITHER LOW OR HIGH



WITH 3-STATE OUTPUTS, CAN DO THIS

 

 MANY COUNTERS & REGISTER  
CHIPS USE 3-STATE OUTPUTS




E.G.  
74HC574

MAY BE LABELED { OE = "OUTPUT ENABLE"  
CS = "CHIP SELECT"

 
# ANOTHER LESS COMMON SOLUTION

"WIRED-OR" OR "OPEN COLLECTOR" OR "DRAIN"



OK IF MORE THAN 1 ON - ANY ON PULLS OUT LOW.

USUALLY DRAWN

 


NOTE

- PULLUP RESISTOR
- \* SYMBOL NEAR OUTPUT



**Bright Red MSQC4111C**  
**High Efficiency Red MSQC4911C**  
**Green MSQC4411C**  
TR/QTS/030800-001

## PACKAGE DIMENSIONS

 

### NOTES:

- Dimensions are in mm (inches)
- Tolerances are +/- 0.25 (0.010) unless otherwise stated.

## FEATURES

- Bright Bold Segments
- Common Anode/Cathode
- Low Power Consumption
- Low Current Capability
- Neutral Segments
- Grey Face
- Epoxy Encapsulated PCB
- High Performance
- High Reliability

## APPLICATIONS


- Appliances
- Automotive
- Instrumentation
- Process Control

## MODELS AVAILABLE


| Part Number | Colour              | Description                              |
|-------------|---------------------|------------------------------------------|
| MSQC4111C   | Bright Red          | Four Digit, 12/24 hour Clock Display, CA |
| MSQC4411C   | Green               | Four Digit, 12/24 hour Clock Display, CA |
| MSQC4911C   | High Efficiency Red | Four Digit, 12/24 hour Clock Display, CA |
|             |                     |                                          |
|             |                     |                                          |
|             |                     |                                          |
|             |                     |                                          |
|             |                     |                                          |

(For other colour/polarity options, contact your local area Sales Manager)

 **PIN ORIENTATION, SEGMENT IDENTIFICATION, AND PRODUCT MARKING**



**SCHEMATICS**

 

## CD4017BC • CD4022BC

### Decade Counter/Divider with 10 Decoded Outputs • Divide-by-8 Counter/Divider with 8 Decoded Outputs

#### General Description

The CD4017BC is a 5-stage divide-by-10 Johnson counter with 10 decoded outputs and a carry out bit.

The CD4022BC is a 4-stage divide-by-8 Johnson counter with 8 decoded outputs and a carry-out bit.

These counters are cleared to their zero count by a logical "1" on their reset line. These counters are advanced on the positive edge of the clock signal when the clock enable signal is in the logical "0" state.

The configuration of the CD4017BC and CD4022BC permits medium speed operation and assures a hazard free counting sequence. The 10/8 decoded outputs are normally in the logical "0" state and go to the logical "1" state only at their respective time slot. Each decoded output remains high for 1 full clock cycle. The carry-out signal completes a full cycle for every 10/8 clock input cycles and is used as a ripple carry signal to any succeeding stages.

#### Features

- Wide supply voltage range: 3.0V to 15V
- High noise immunity: 0.45  $V_{DD}$  (typ.)
- Low power Fan out of 2 driving 74L  
TTL compatibility: or 1 driving 74LS
- Medium speed operation: 5.0 MHz (typ.)  
with 10V  $V_{DD}$
- Low power: 10  $\mu$ W (typ.)
- Fully static operation

#### Applications

- Automotive
- Instrumentation
- Medical electronics
- Alarm systems
- Industrial electronics
- Remote metering


#### Ordering Code:

| Order Number | Package Number | Package Description                                                          |
|--------------|----------------|------------------------------------------------------------------------------|
| CD4017BCM    | M16A           | 16-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-012, 0.150" Narrow |
| CD4017BCSJ   | M16D           | 16-Lead Small Outline Package (SOP), EIAJ TYPE II, 5.3mm Wide                |
| CD4017BCN    | N16E           | 16-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300" Wide       |
| CD4022BCM    | M16A           | 16-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-012, 0.150" Narrow |
| CD4022BCN    | N16E           | 16-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300" Wide       |


Devices also available in Tape and Reel. Specify by appending the suffix letter "X" to the ordering code.


 
#### Connection Diagrams

Pin Assignments for DIP, SOIC and SOP  
CD4017B



 
Pin Assignments for DIP and SOIC  
CD4022B



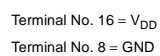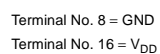

## Timing Diagrams

CD4017B

 

CD4022B

