

Physics 335, Spring Quarter 2011, Examination

Name SOLUTIONS VI.2

1 /35

2 /35

3 /30

TOTAL /100

Please check that you have a total of 7 exam pages, including this page.

This exam is closed-book. There's a summary of PIC instructions on the following page.

PIC16F84A

TABLE 7-2: PIC16CXXX INSTRUCTION SET

Mnemonic, Operands	Description	Cycles	14-Bit Opcode				Status Affected	Notes	
			MSb		LSb				
BYTE-ORIENTED FILE REGISTER OPERATIONS									
ADDWF	t, d	Add W and f	1	00	0111	dfff	ffff	C,DC,Z	1,2
ANDWF	t, d	AND W with f	1	00	0101	dfff	ffff	Z	1,2
CLRF	f	Clear f	1	00	0001	1fff	ffff	Z	2
CLRWF	-	Clear W	1	00	0001	0xxx	xxxx	Z	
COMF	t, d	Complement f	1	00	1001	dfff	ffff	Z	1,2
DECf	t, d	Decrement f	1	00	0011	dfff	ffff	Z	1,2
DECFSZ	t, d	Decrement f, Skip if 0	1 (2)	00	1011	dfff	ffff		1,2,3
INCF	t, d	Increment f	1	00	1010	dfff	ffff	Z	1,2
INCFSZ	t, d	Increment f, Skip if 0	1 (2)	00	1111	dfff	ffff		1,2,3
IORWF	t, d	Inclusive OR W with f	1	00	0100	dfff	ffff	Z	1,2
MOVF	t, d	Move f	1	00	1000	dfff	ffff	Z	1,2
MOVWF	f	Move W to f	1	00	0000	1fff	ffff		
NOP	-	No Operation	1	00	0000	0xx0	0000		
RLF	t, d	Rotate Left f through Carry	1	00	1101	dfff	ffff	C	1,2
RRF	t, d	Rotate Right f through Carry	1	00	1100	dfff	ffff	C	1,2
SUBWF	t, d	Subtract W from f	1	00	0010	dfff	ffff	C,DC,Z	1,2
SWAPF	t, d	Swap nibbles in f	1	00	1110	dfff	ffff		1,2
XORWF	t, d	Exclusive OR W with f	1	00	0110	dfff	ffff	Z	1,2
BIT-ORIENTED FILE REGISTER OPERATIONS									
BCF	t, b	Bit Clear f	1	01	00bb	bfff	ffff		1,2
BSF	t, b	Bit Set f	1	01	01bb	bfff	ffff		1,2
BTFSC	t, b	Bit Test f, Skip if Clear	1 (2)	01	10bb	bfff	ffff		3
BTFSS	t, b	Bit Test f, Skip if Set	1 (2)	01	11bb	bfff	ffff		3
LITERAL AND CONTROL OPERATIONS									
ADDLW	k	Add literal and W	1	11	111x	kkkk	kkkk	C,DC,Z	
ANDLW	k	AND literal with W	1	11	1001	kkkk	kkkk	Z	
CALL	k	Call subroutine	2	10	0xxx	kkkk	kkkk		
CLRWDT	-	Clear Watchdog Timer	1	00	0000	0110	0100	$\overline{TO,PD}$	
GOTO	k	Go to address	2	10	1xxx	kkkk	kkkk		
IORLW	k	Inclusive OR literal with W	1	11	1000	kkkk	kkkk	Z	
MOVLW	k	Move literal to W	1	11	00xx	kkkk	kkkk		
RETFIE	-	Return from interrupt	2	00	0000	0000	1001		
RETLW	k	Return with literal in W	2	11	01xx	kkkk	kkkk		
RETURN	-	Return from Subroutine	2	00	0000	0000	1000		
SLEEP	-	Go into standby mode	1	00	0000	0110	0011	$\overline{TO,PD}$	
SUBLW	k	Subtract W from literal	1	11	110x	kkkk	kkkk	C,DC,Z	
XORLW	k	Exclusive OR literal with W	1	11	1010	kkkk	kkkk	Z	

1. (35 points) PIC 16F84A programming.

Find the value of w-register after execution of the following snippets of code.

You can assume the 16f84a.inc definitions are loaded. Put your answer in hexadecimal form in the box.

```
movlw B'00001111' ;move literal to w
```

w (hex) = H'0F' [= B'0000 1111']

```
movlw H'06' ;move literal to w  
andlw H'04' ;Boolean literal and to w
```

w (hex) = H'04' [= B'0000 0100']

```
movlw H'06' ;move literal to w  
movwf H'0E' ; move w to file register  
bsf H'0E', H'03' ;bit set  
movf H'0E', w ;move file register
```


w (hex) = H'0E' [= B'0000 1110']

```
movlw H'06' ;move literal to w  
movwf H'0E' ; move w to file register  
bsf H'0E', D'00' ;bit set  
movf H'0E', f ;move file register
```


w (hex) = H'06' [= B'0000 0110']

NOTICE IT'S A TRICK QUESTION - THIS INSTRUCTION DOESN'T MODIFY W,

 2. (35 points) Counters. Recall in lab we used a 74LS90 configured as shown just below as a decade counter. Also recall that the connection between output Q_A and input CKB was made because this counter has two independent counters, a divide-by-two counter (clocked at CKA with output Q_A) and a divide-by-five counter (clocked at CKB with outputs Q_B , Q_C and Q_D).



 Now, from this point on, consider the 74LS90 wired as shown below. Assume un-shown inputs don't disable counting.



A. In 10 words or less, what's the "wedge" at CKA and CKB indicate?


The wedge indicates ... *EDGE-TRIGGERED INPUT.*

B. In 10 words or less, what's the "open ball" at CKA and CKB indicate?

The open ball indicates ... *TRIGGER ON FALLING EDGE.*

(problem 2, continued)

 C. Complete the timing diagram below. Notice Q_A through Q_D start "low".




D. In 10 words or less, describe a simple wiring modifications to this circuit, that, without adding any additional gates or parts, produces a symmetric duty-factor decade counter.

You simply ... CONNECT Q_D TO CLKA AND USE Q_A AS THE OUTPUT;
OR YOU CAN CONNECT Q_C TO CLKA AND USE Q_A AS OUTPUT.


3. (30 points) Digital circuits: short answers.

A. Single gate: what's the value of Q?

$$Q = \overline{A}$$

 

 B. Two open-collector logic gates are wired as shown.




What's the value of Q?

$$Q = \text{LOW} \{ \text{OR "F" OR "0" OR 0V.} \}$$


C. Fill in the truth table (positive logic)

A	B	Q
0	0	1 {or "T", etc.}
0	1	0
1	0	0
1	1	1

 

D. Fill in the truth table, assuming A, B = 1, 1 is followed by 1, 0 then 0, 1 etc. (positive logic)

A	B	X	Y
1	1	0	0
1	0	0	1
0	1	1	0
1	0	0	1

 

E. D-latch: Fill in the timing diagram for Q with CLK and D as shown. Notice that Q starts low. Assume un-shown inputs don't inhibit clocking the chip.

