
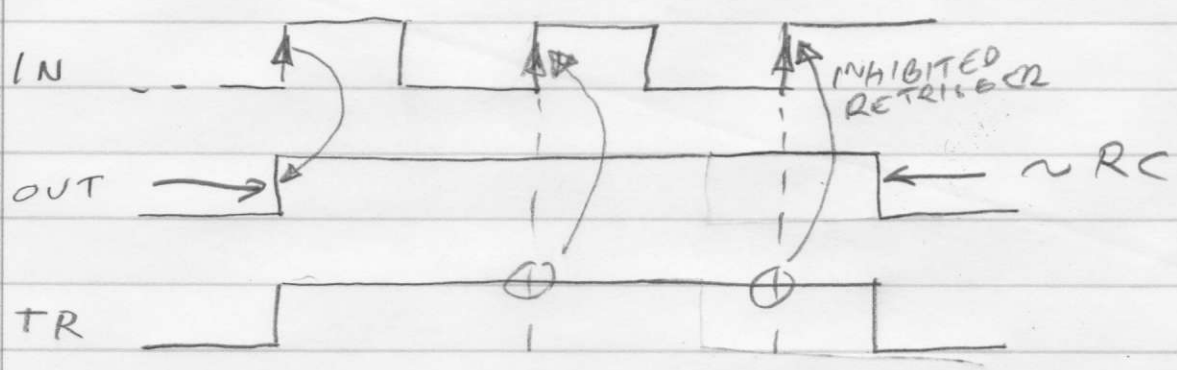


PHYS 335 - SPRING QUARTER 2013
HOMEWORK 3 SOLUTIONS VI.0

1. SEE HLH TEXT P. 518 AT UPPER LEFT.

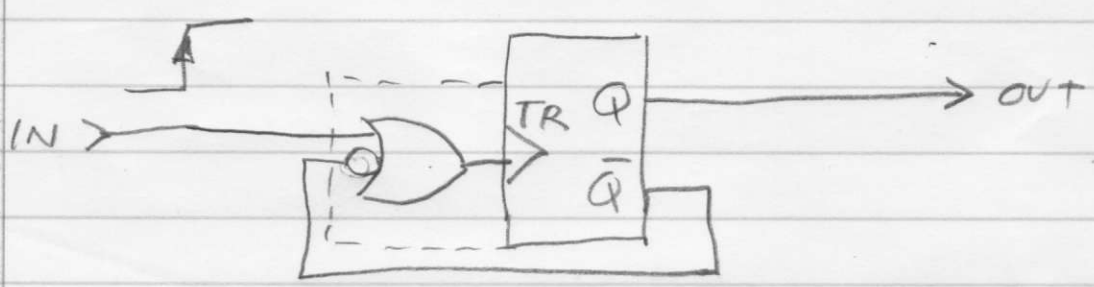

2. LOOK AT A DATASHEET FOR THE OUTPUT PULSE WIDTH VS. TIMING CAPACITANCE. NOTICE AS $C \rightarrow 0$, THE OUTPUT PULSE WIDTH APPROACHES A CONSTANT. THIS IS DUE TO THE "STRAY" CAPACITANCE AT THAT PIN, APPROXIMATELY, THE LIMITING PULSE WIDTH IS ~ 100 NS.

FOR MORE FUN: FIGURE OUT THE VALUE OF THE "STRAY" CAPACITANCE AND ASK YOURSELF WHETHER THIS VALUE IS REASONABLE

3. AGAIN, LOOK AT A DATASHEET.
NOTICE THERE'S AN INTERNAL $10k\Omega$
RESISTOR. USING $10k\Omega$ TIMING CURVES
FROM THE DATASHEET AND EYEBALLING
 $C \rightarrow 0$, THE PULSE-WIDTH IS
AGAIN IN THE NEIGHBORHOOD
OF $100ns$.