


PHYS 335 - SPRING QUARTER 2013

①

HOMEWORK 5 SOLUTIONS

V1.0

1) 0 10V

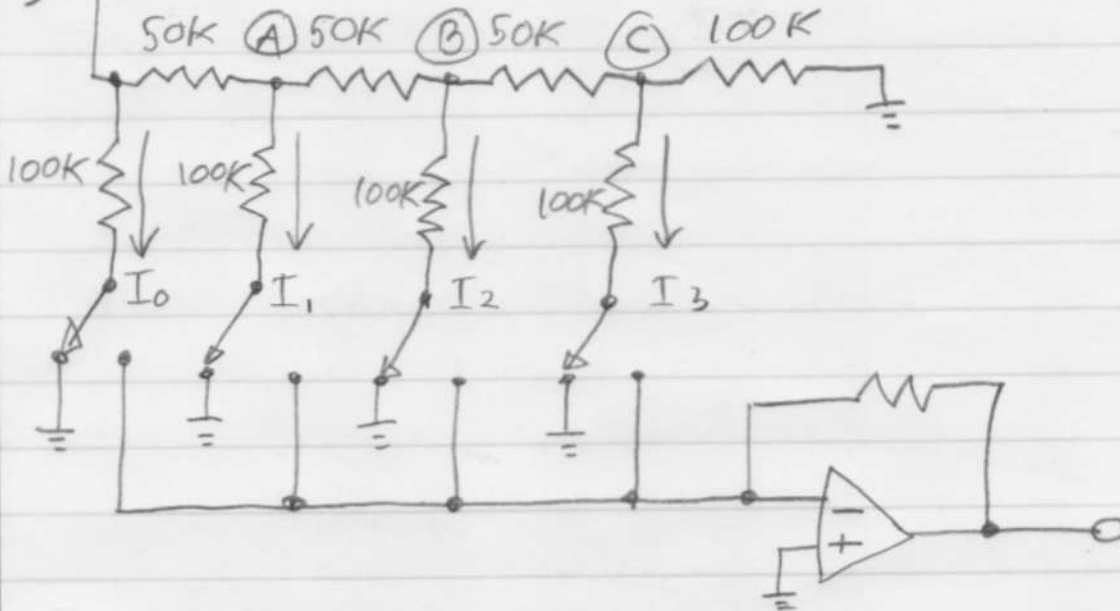

EITHER SWITCH POSITION IS A GROUND - REAL OR VIRTUAL. THEREFORE CURRENTS DON'T DEPEND ON SWITCH POSITIONS. NOTICE CURRENT ENTERING NODE (C) FROM THE LEFT; IT DIVIDES EQUALLY THROUGH TWO 100K RESISTORS. AS FOR NODE (B), THE RESISTANCE "LOOKING" RIGHT IS 100K (THAT IS, $50K + 100K \parallel 100K = 100K$). HENCE CURRENT ENTERING (B) SPLITS EVENLY. THE SAME HOLDS FOR NODE (A). HENCE, AT EACH NODE, CURRENT SPLITS EQUALLY.

THE CURRENT I_0 IS $\frac{10V}{100K\Omega} = 100\mu A$,
 HENCE $I_1 = 50\mu A$, $I_2 = 25\mu A$, AND
 $I_3 = I_4 = 12.5\mu A$.

2) FOR $V_{REF} = 10V$ WITH 16 "STEPS", EACH STEP IS $10V/16 = 0.625 V/COUNT$,

$7.21V / 0.625 V/COUNT \approx 11.5$ COUNTS,
HENCE, THE 4 MSBs ARE 1011.

THE SECOND ADC SEES INPUT

$$7.21V - 11 \text{ COUNTS} \times 0.625 V/COUNT = 0.335V.$$

NOTICE THE "STEP SIZE" (LEAST COUNT) IS X16 SMALLER THAN THAT OF THE FIRST ADC: $(10V/16) / 16V/COUNT = 0.039 V/COUNT$,

SO, AGAIN

$$0.335V / 0.039 V/COUNT \approx 8.6 \text{ COUNTS}$$

HENCE, THE FOUR LSBs ARE 1000

AND THE COMPLETE 8-BIT OUTPUT IS
1011 1000

(YOU CAN QUIBBLE ABOUT WHETHER TO ASSIGN COUNT THRESHOLDS AT THE BOTTOM, TOP, OR MIDDLE OF A STEP.)