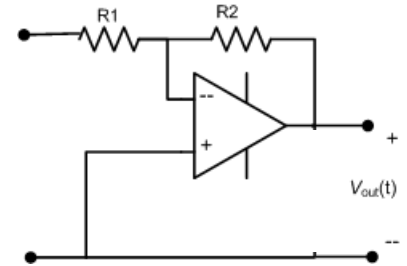


Quiz 2 Practice

This was quiz 2 on October 21, 2009

Note: Throughout this quiz, you may leave your answers in terms of R_1 , R_2 , R_x and L , or you may use $R_1 = 4 \Omega$, $R_2 = 10 \Omega$, $R_3 = 6 \Omega$, $L = 2 \text{ H}$. [A table of Laplace transforms was provided on the original quiz but has been omitted from this practice sheet.]

You know from EE 215 that, for an inverting op-amp circuit, $\frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1}$.




a) Show that you can make an integrating circuit by replacing one of the resistors with an inductor. Steps to follow: State which resistor is replaced by the inductor, provide the transfer function for this circuit; write the Laplace transform pair that shows it is an integrator.

This is an inverting amplifier circuit, which as shown has a gain of $-R_2/R_1$. Replace R_1 with an inductor, and work in impedances: $Z_L = Ls$, and $Z_{R_2} = R_2$. The transfer function $V_{out}(s)/V_{in}(s) = -R_2/Ls$. The appropriate Laplace transform pair is

$$\int f(t)dt = \frac{F(s)}{s}, \text{ where } F(s) = -R_2/L. \text{ Therefore it is an integrator. It is also a}$$

circuit with a unit impulse response that is a unit step; they are equivalent.

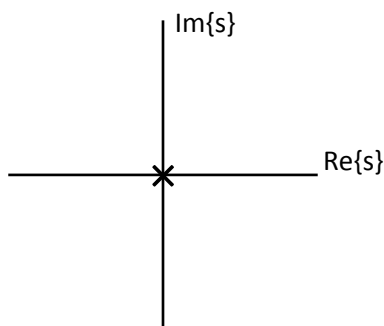b) Mark any poles or zeros on the complex plane, and state whether the integrator is BIBO stable, unstable, or conditionally stable. Use the circuit's response to a unit impulse and its response to a unit step to support your choice.



There is one pole at $0,0$ and no zeros, so the integrator is conditionally stable. When the input is a unit impulse, the output is a step with amplitude R_2/L , which is finite. On the other hand, the response to a unit step is the function $-(R_2/L)t$, which tends toward infinity as time increases. Therefore, whether the output is bounded depends on the input.

c) Show that you can insert a resistor R_x in the inductor-integrator circuit to make it more stable. It might not be as good at integrating, but that is OK. Steps to follow: draw the new circuit, provide its transfer function, mark a new pole-zero plot, and state whether it is now BIBO stable or conditionally stable.

To make the circuit stable we need to add a constant term in the denominator of the transfer function.

That would make the denominator $Ls + R_x$. To get this sum we want the resistor in series with the inductor.


The new transfer function is now

$$V_{out}/V_{in} = (-R_2/L)/(s + R_x/L)$$

It has one pole at $-R_x/L$, and no zeros.

Its impulse response is $v(t) = (-R_2/L) \cdot \exp(-t \cdot R_x/L) \cdot u(t)$, which integrates to $-R_2/R_x$. If we integrate the absolute value we get $+R_2/R_x$, which is bounded so it is bounded-input, bounded output (BIBO) stable.

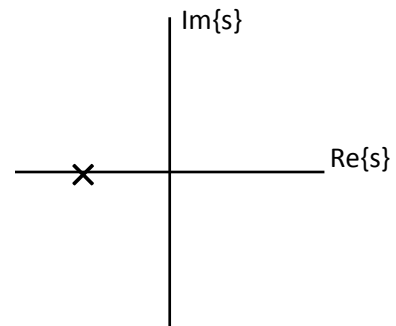I have omitted the figure, but it has R_x and L in series where R_1 was before, and R_2 is unchanged.



$f(t)$	$F(s)$
$t^n u(t)$	$\frac{n!}{s^{n+1}}$
$\frac{d}{dt} f(t)$	$sF(s)$
$\int f(t) dt$	$\frac{F(s)}{s}$
$f(t-a)u(t-a)$	$e^{-as}F(s)$
$\int_{-\infty}^{+\infty} f(\lambda)g(t-\lambda)d\lambda$	$F(s)G(s)$